

Ohms Law.

What does it mean...

$E = I \times R$ (Voltage = Current multiplied by Resistance)

$R = E / I$ (Resistance = Voltage divided by Current)

$I = E / R$ (Current = Voltage Divided by Resistance)

What is a WATT **$P=EI$** ~The measure unit of power used in a circuit. for instance 3 lights in a circuit all using 60w bulbs would be 180w on that circuit.

Power is defined as **$P = V \times I$** .

Substituting in Ohm's Law for V and I:

$$\mathbf{V = I \times R}$$

$$P = V \times I$$

$$V = R \times I$$

∴

$$P = R \times I \times I = I^2 R$$

$$\mathbf{P = I^2 R}$$

$$\mathbf{P = V \times I}$$

$$I = \frac{V}{R}$$

∴

$$P = V \times \frac{V}{R} = \frac{V^2}{R}$$

$$\mathbf{P = \frac{V^2}{R}}$$

This is proportional to the amount of voltage and amount of current flow through that circuit.

Volts E	Amps I	Ohms R	Watts P
153	.056		
	.065	470	
24			124
	.00975		.035
		6.8	.86
460		72	

Volts E	Amps I	Ohms R	Watts P
48	1.2		
	154	.8	
277			760
	.0043		.0625
		130	.0225
96		2.2	

An electric Iron is connected to 120v and has a current draw of 8A. How much power is used by the iron?

Calculate the solution in Watts

$P=EI$ $P=120 \times 8$ $P=960W$

An electric hair dryer has a power rating of 1000W. How much current will it draw when connected to 120V?

$$I = P/E \quad I = 1000/120 \quad I = 8.33A$$

The quantity to be found here is amperage or current. The known quantities are power and Voltage. Use the following equation

$$R = P/I^2$$

$$R = \frac{1440}{12 \times 12}$$

$$R = \frac{1440}{144}$$

$$R = 10$$