ID: MC123456789

Digital Logic Design (CS302)

Question No 01

Simplify the stated 5 Variable Boolean Expression using the Karnaugh Map method.

$$F(A, B, C, D, E) = \sum (1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31)$$

With the following **Don't Care**Conditions

$$F(A, B, C, D, E) = \sum (2, 6, 10, 14, 18, 22, 26, 30)$$

Solution:

BC/DE	00	0	1	10
		1	1	
00	0	1	3	2
01	4	5	7	6
11	12	1	1	14
		3	5	
10	8	9	1	10
			1	
BC/DE	00	0	1	10
		1	1	
00	16	1	1	18
		7	9	
01	20	2	2	22
		1	3	
11	28	2	3	30
		9	1	
10	24	2	2	26
		5	7	

A=1

A=0

BC/DE	00	0	1	10
		1	1	
00	0	1	1	Χ
01	0	1	1	Х
11	0	1	1	Х
10	0	1	1	Х
BC/DE	00	0	1	10
BC/DE	00	0	1	10
BC/DE 00	00			10 X
		1	1	
00	0	1	1	Х

A=0 A=1

Group:

Positions = 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31

Simplified Expression = E