

Esercizi sulle porte logiche

Si fornisca la rappresentazione grafica del circuito e la relativa tabella di verità delle seguenti equazioni logiche:

1. $z = ((a \text{ AND } b) \text{ XOR } c)$
2. $z = a + (b \oplus (a * b))$
3. $z = a \text{ AND } b \text{ OR } (\text{NOT}(a) \text{ OR } \text{NOT}(c))$
4. $z = (a \text{ AND } (\text{NOT}(b))) \text{ OR } c$
5. $z = \text{NOT}(a) \text{ AND } (b \text{ OR } c)$
6. $z = a * (b + c)$
7. $z = \text{NOT}(a) \text{ OR } (\text{NOT}(b) \text{ AND } \text{NOT}(c))$


Per le seguenti equazioni logiche, dopo aver cercato il comportamento delle porte logiche che non si conoscono, si fornisca la rappresentazione grafica del circuito e la relativa tabella di verità.

1. $z = \text{NOT}(a) \text{ NOR } (b \text{ NOR } c)$
2. $z = a \text{ OR } (b \text{ XNOR } (a \text{ AND } b))$
3. $z = ((a \text{ NAND } b) \text{ OR } c) \text{ AND } (b \text{ XOR } c)$

Soluzioni


1. $z = ((a \text{ AND } b) \text{ XOR } c)$

a	b	a AND b	c	((a AND b) XOR c)
0	0	0	0	0
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	0	1
1	1	1	1	0

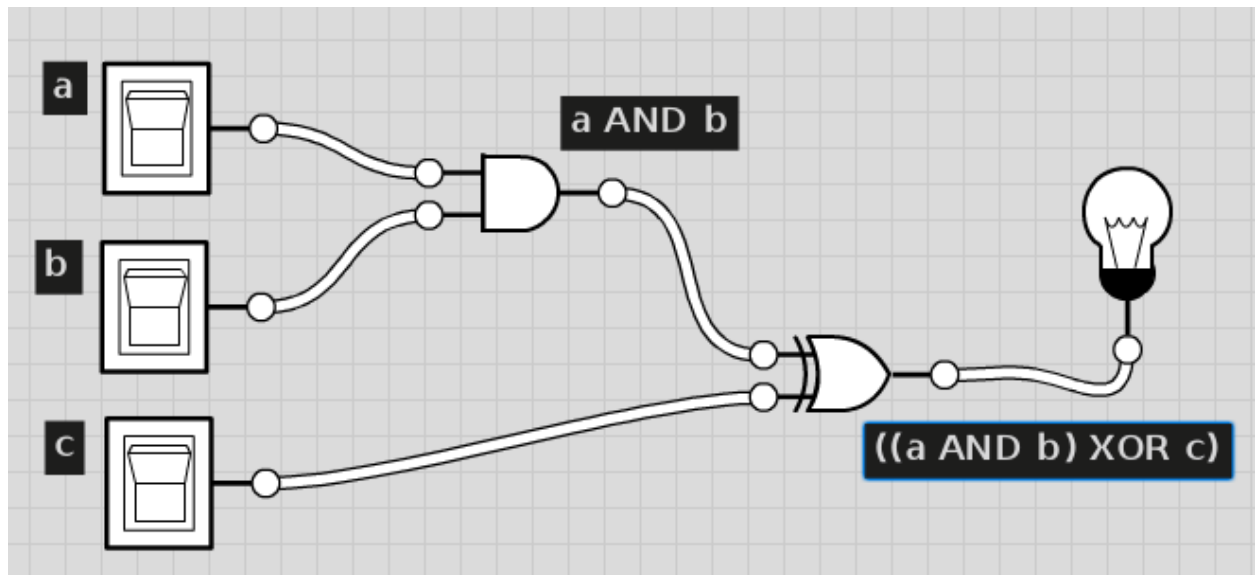

2. $z = a + (b \oplus (a * b))$

a	b	a * b	$b \oplus (a * b)$	$a + (b \oplus (a * b))$
0	0	0	0	0
0	1	0	1	1
1	0	0	0	1
1	1	1	0	1

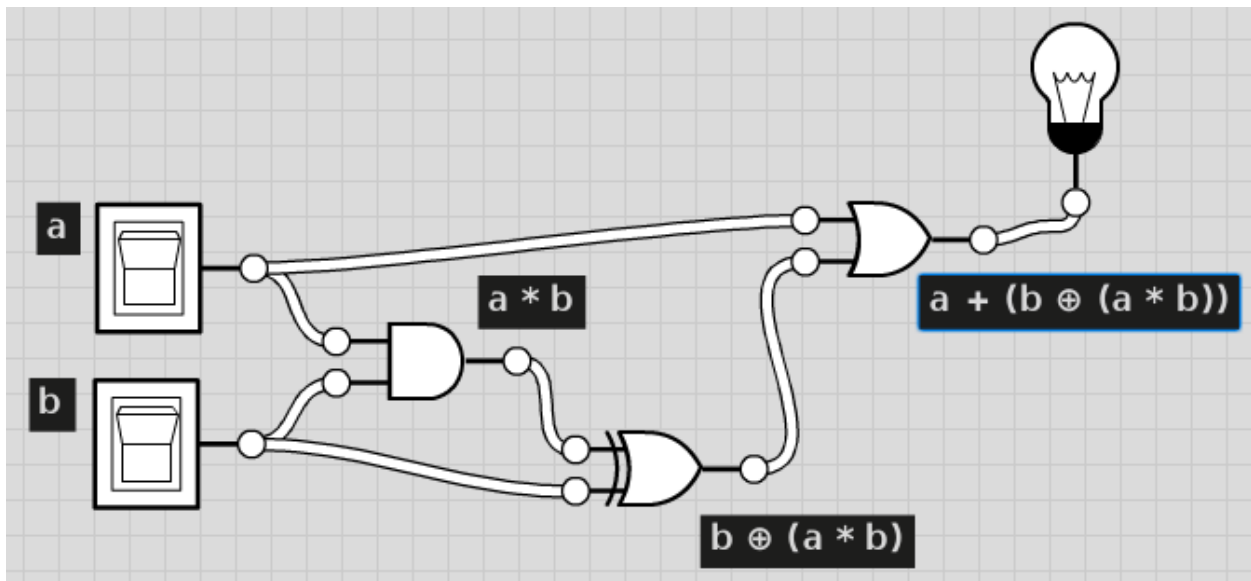

3. $z = a \text{ AND } (b \text{ OR } (\text{NOT}(a) \text{ OR } \text{NOT}(c)))$

a	b	c	NOT(a)	NOT(c)	NOT(a) OR NOT(c)	b OR (NOT(a) OR NOT(c))	a AND (b OR (NOT(a) OR NOT(c)))
0	0	0	1	1	1	1	0
0	0	1	1	0	1	1	0
0	1	0	1	1	1	1	0
1	0	0	0	1	1	1	1
0	1	1	1	0	1	1	0
1	0	1	0	0	0	0	0
1	1	0	0	1	1	1	1
1	1	1	0	0	0	1	1

