

# Department of Electronics & Communication Engineering


(Faculty of Technology, Dharmsinh Desai University, Nadiad)

Academic Year: 2022 - 2023


## TUTORIAL – 1

**Subject** : (ESC101) BASIC ELECTRICAL ENGINEERING  
**Class** : B. Tech. Sem.I (EC/CE/IT)  
**Topics** : Temperature dependance of resistance, Kirchoff current and voltage laws

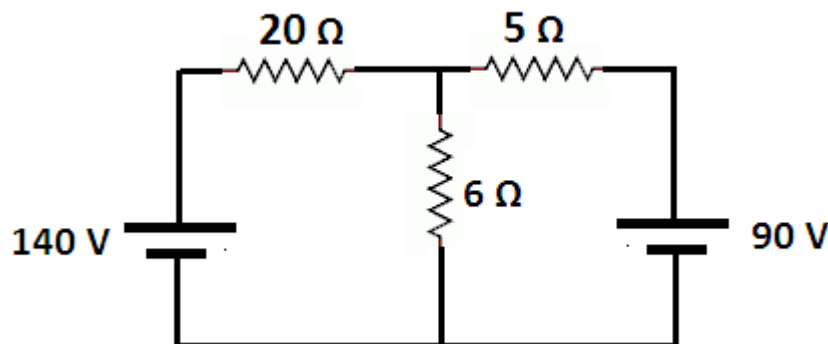
1. A coil has a resistance of  $21.6 \Omega$  when its mean temperature is  $20^\circ\text{C}$  and of  $24 \Omega$  when its mean temperature is  $50^\circ\text{C}$ . Find its mean temperature rise, when its resistance is  $25.2 \Omega$  and the surrounding temperature is  $16^\circ\text{C}$ .
2. The resistance of a field coil measures  $55 \Omega$  at  $25^\circ\text{C}$  and  $65 \Omega$  at  $75^\circ\text{C}$ . Find the temperature co-efficient of conductor at  $0^\circ\text{C}$ .
3. A coil has a resistance of  $18 \Omega$ , when its mean temperature is  $20^\circ\text{C}$ ; and  $20 \Omega$ , when its mean temperature rise is  $50^\circ\text{C}$ . Find its mean temperature rise when its resistance is  $21 \text{ ohms}$  and the surrounding temperature is  $15^\circ\text{C}$ .
4. Find current and voltages across all the resistors.



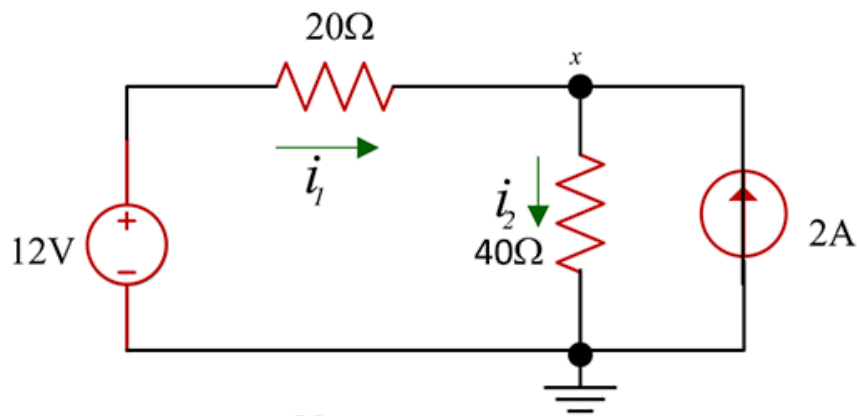
5. Find the current through  $20 \Omega$  and  $40 \Omega$  resistors.



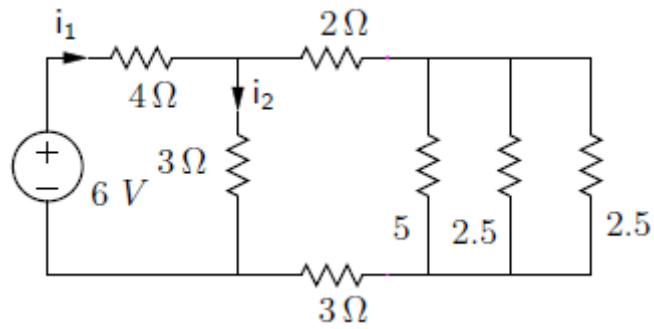6. Find current  $i_1$  for the circuit shown in figure.



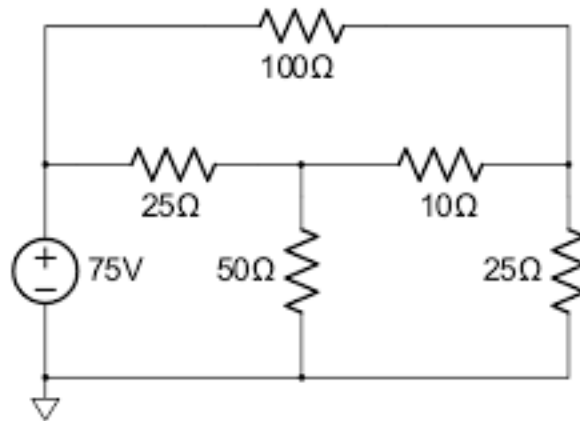7. Find node voltages in the following circuit.



Prof. Hetal Shah ([shahhetal.ec@ddu.ac.in](mailto:shahhetal.ec@ddu.ac.in))  
Prof. J. M. Shah ([jmshah.ec@ddu.ac.in](mailto:jmshah.ec@ddu.ac.in))