



WESTSIDE HIGH SCHOOL

Level Up: *RISE* to Your Potential

24-25 Lesson Plan Template

Teacher: **Asma Akhter**

Subject: **On level physics A**

Week of: DATE 02/17/2025	Monday 02/17	Tuesday 02/18	Wed./Thurs 02/19- 02/20	Friday 02/21
TEKS	N	<p>P.6D Analyze, design, and construct series and parallel circuits using schematics and materials such as switches, wires, resistors, lightbulbs, batteries, voltmeters, and ammeters.</p> <p>PHY.6.E Calculate current through, potential difference across, resistance of, and power used by electric circuit elements connected in both series and</p>	<p>PHY.6.E Calculate current through, potential difference across, resistance of, and power used by electric circuit elements connected in both series and parallel circuits using ohm's law.</p> <p>P.6D Analyze, design, and construct series and parallel circuits using schematics and materials such as switches, wires, resistors, lightbulbs, batteries, voltmeters, and ammeters.</p>	<p>PHY.6.E Calculate current through, potential difference across, resistance of, and power used by electric circuit elements connected in both series and parallel circuits using ohm's law.</p> <p>P.6D Analyze, design, and construct series and parallel circuits using schematics and materials such as</p>

		parallel circuits using Ohm's law. Electricity in Electric Circuits		switches, wires, resistors, lightbulbs, batteries, voltmeters, and ammeters.
Learning Objective	O	SWBAT design and construct a simple electric circuit and calculate the power used by elements in series or parallel configurations using appropriate formulas derived from Ohm's law.	SWBAT design and construct a simple electric circuit and calculate the power used by elements in series or parallel configurations using appropriate formulas derived from Ohm's law.	SWBAT design and construct a simple electric circuit and calculate the power used by elements in series or parallel configurations using appropriate formulas derived from Ohm's law.
Higher Order Thinking Questions	SC	2. In a series circuit with a 120 V power supply, if the current is 2 A, what is the total power? .	In a series circuit, if three resistors with resistances of 4 Ω , 6 Ω , and 10 Ω are connected to a 24 V power supply, what is the total power dissipated?	The charges $q_1=10$ cm between the ce between the cente magnitude of the n

Agenda	<ul style="list-style-type: none"> • H 	<ul style="list-style-type: none"> • Do Now about power • Student Activity from Hisd • DOL 	<ul style="list-style-type: none"> • Do now • Review with a galley walk • Quizizz.com 	Test 2 (6 weeks test from Hisd)
Demonstration of Learning	OO	Given 5 questions, students will design and construct a simple electric circuit and calculate the power used by elements in series or parallel configurations using appropriate formulas derived from Ohm's law by answering at least 4 of 5 questions correctly.	Given one open ended questions, higher order thinking question, and students will be able to answer on the response card.	Test will be given in On track
Intervention & Extension	L	Extra time At least finish 50% and one extra day	Extra time At least finish 50% and one extra day	o

Resources		<ul style="list-style-type: none">● District resources and teacher's google slides● Teacher's teaching with notes included formula chart	<ul style="list-style-type: none">● District resources and teacher's google slides● Review● Quizizz	I
------------------	--	---	---	---