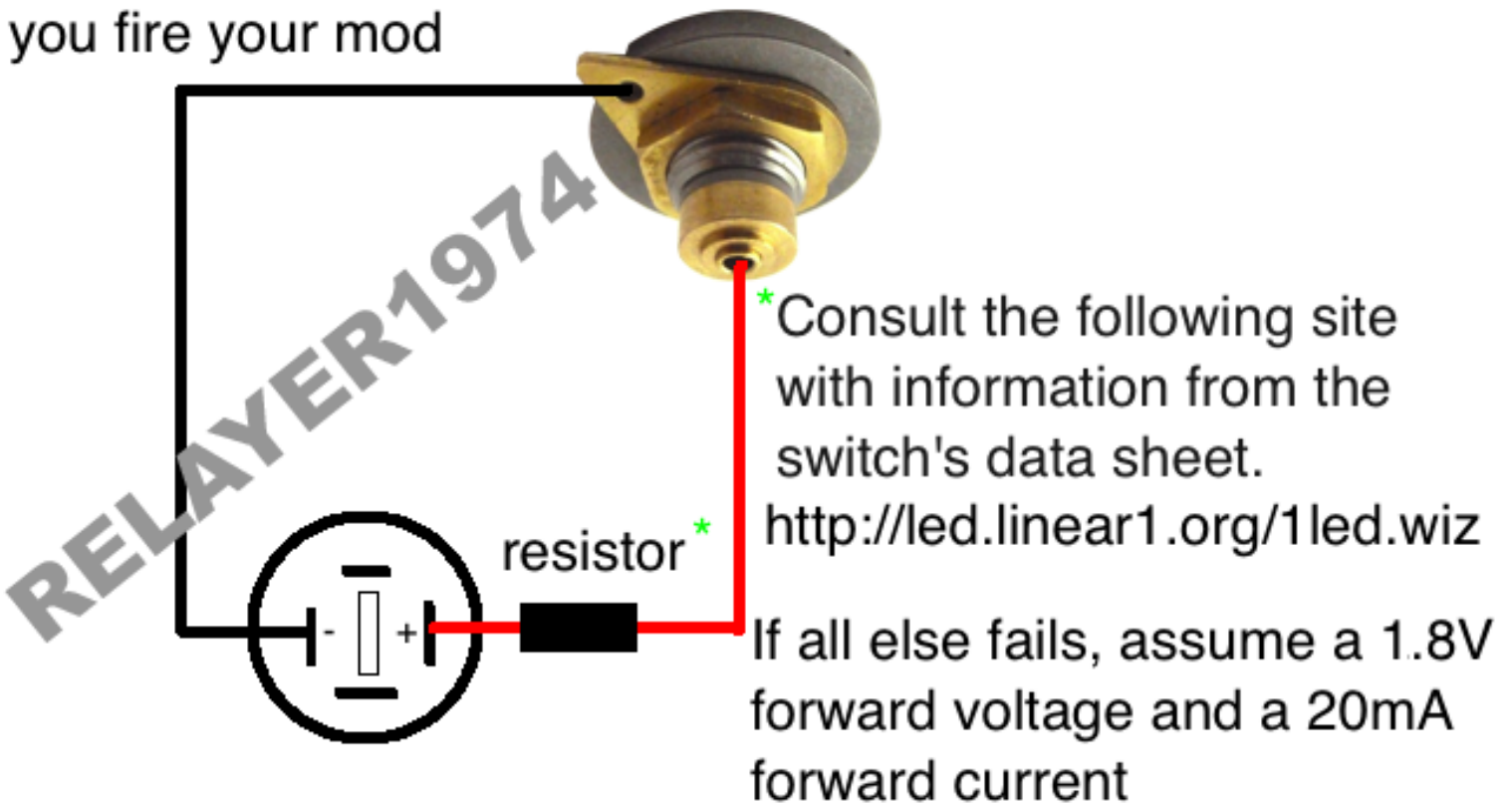


This diagram shows how an illuminated switch can be connected to any mod. Here's a video that will help as well: <https://www.youtube.com/watch?v=vFWMuumr-Uk>

## ILLUMINATED SWITCH WIRING

This is how you wire an illuminated switch to come on when you fire your mod



Use the other two contacts like you would any other switch.

**SEE BELOW FOR THE FIVE-PIN DIAGRAM:**

**CONNECT THE POSITIVE WIRE TO THE PLUS AND THE NEGATIVE WIRE TO THE MINUS. STOP MAKING SIMPLE SHIT HARD.**

**CONNECT THE POSITIVE WIRE TO THE PLUS AND THE NEGATIVE WIRE TO THE MINUS. STOP MAKING SIMPLE SHIT HARD.**



**THESE SWITCHES USUALLY HAVE AN INTERNAL LED DRIVER ENABLING A WIDE VOLTAGE INPUT RANGE. READ THE INFORMATION PROVIDED WITH THE SWITCH BEFORE YOU DO SOMETHING STUPID WITH IT.**