

Roll No.....

Total No. of Printed Pages: [01]

Total No. of Questions: [09]

**B. Tech (Mech. Engg.) (Semester – 2<sup>nd</sup>)**  
**BASICS OF ELECTRICAL ENGINEERING**  
**Subject Code: BELE0101**  
**Paper ID: [110004]**

**Time: 03 Hours**

**Maximum Marks: 60**

**Instruction for candidates:**

1. Section A is compulsory. It consists of 10 parts of two marks each.
2. Section B consist of 5 questions of 5 marks each. The student has to attempt any 4 questions out of it.
3. Section C consist of 3 questions of 10 marks each. The student has to attempt any 2 questions.

**Section – A**

**(2 marks each)**


Q1. Attempt the following:

- a) Define Kirchhoff's Laws.
- b) What are the limitations of ohm's law?
- c) What is meant by power factor?
- d) What do you understand by cut-off frequency?
- e) What is the power associated with pure resistance in an a.c. circuit?
- f) What are the relationships between phase and line quantities in case of 3- $\Phi$  star connection?
- g) Which material is used for making core of transformers and why?
- h) Define the term voltage regulation.
- i) What is the function of commutator in DC machines?
- j) What is meant by the term slip?

**Section – B**

**(5 marks each)**

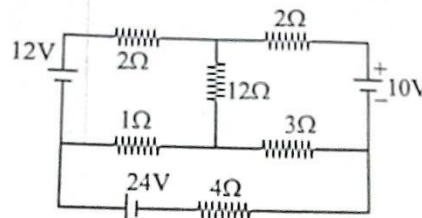Q2. Determine the current in  $4\Omega$  branch using loop current method of the circuit shown below:-



- Q3. What is the use of star-delta and delta-star transformation in the circuits? Explain the method for transforming star network into a delta network.
- Q4. Explain resonance phenomenon in a parallel circuit.
- Q5. Derive the relationship between phase and line quantities in case of delta connections.
- Q6. Explain the construction and working principle of induction motor.

**Section – C**

**(10 marks each)**

- Q7. A resistance of 10 ohms, an inductance of 0.24H and a capacitance of  $100\mu\text{F}$  are connected in series across 200V, 50Hz supply. Find out:-
  - (i) Impedance
  - (ii) Current
  - (iii) Voltage across R, L and C
  - (iv) Active and Passive powers
  - (v) Power factor of the circuit.
- Q8. Explain the working of 1-phase practical transformer with equivalent circuit diagram. Also draw the phasor diagram of transformer on resistive, inductive and capacitive loads.
- Q9. Explain the major parts of DC machines. Draw the sketch and discuss them in detail.