
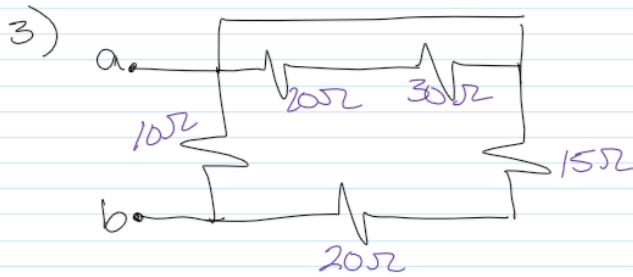
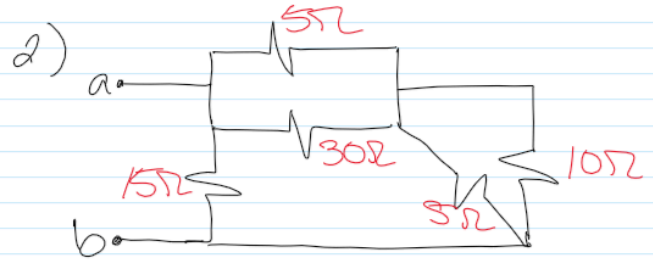


Finding Equivalent Resistance













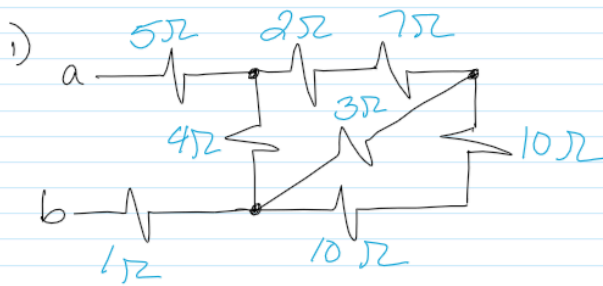
Problem Set 1: Equivalent Resistances

Find $R_{eq} = R_{ab}$ in the following circuits:





Solutions

Solutions:

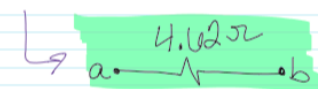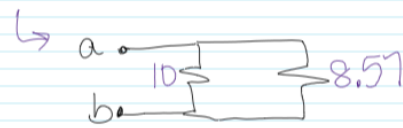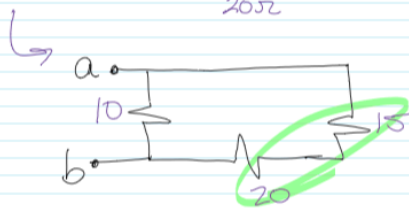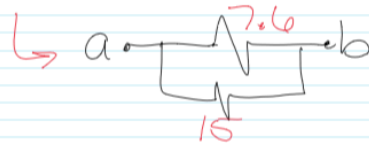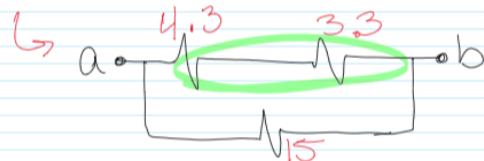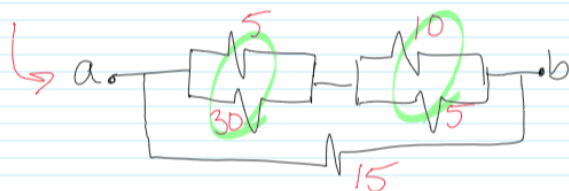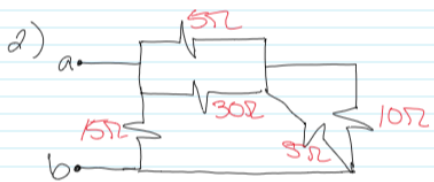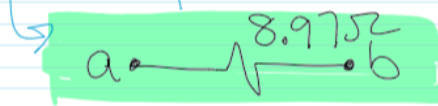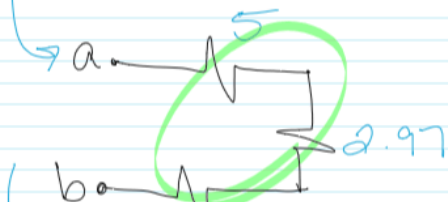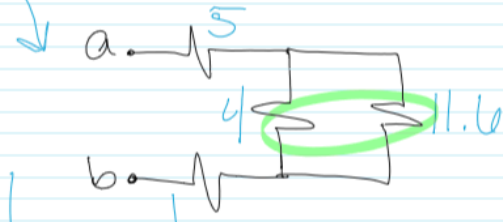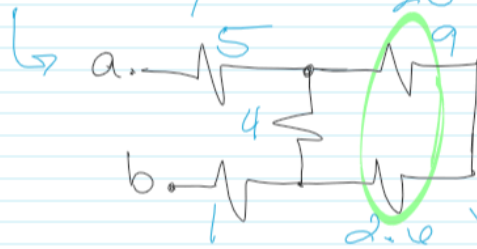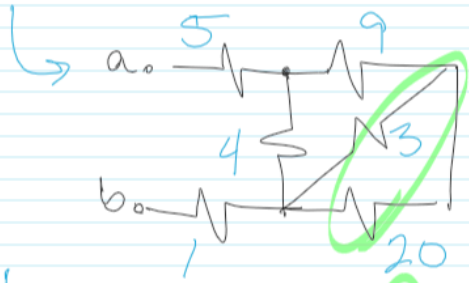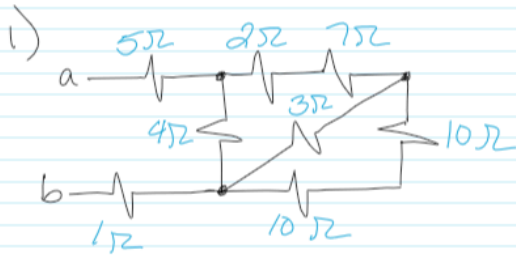

Finding Voltages

Problem Set 2: finding Voltages

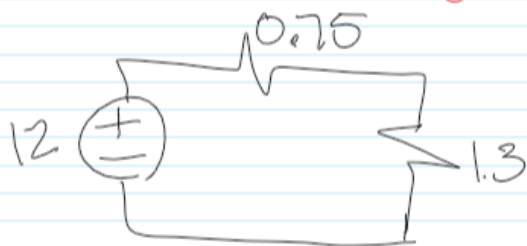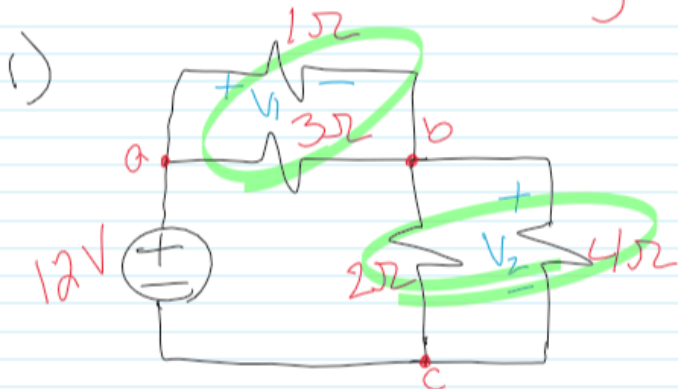


Use KVL:

$$-12 + 0.75i + 1.3i = 0$$

$$i \approx 5.9 \text{ A}$$

$$V_{ab} = i \cdot 0.75 = 4.4 \text{ V} = V_1$$
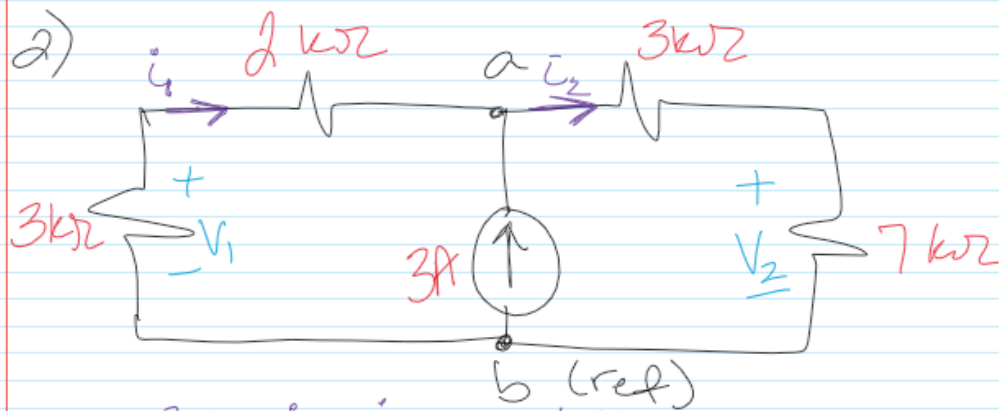
$$V_{bc} = i \cdot 1.3 = 7.7 \text{ V} = V_2$$



$$3A + i_1 = i_2 \quad \text{KCL}$$

$$i_1 = \frac{V_b - V_a}{5k\Omega} = \frac{-V_a}{5k\Omega}; \quad i_2 = \frac{V_a - V_b}{10k\Omega} = \frac{V_a}{10k\Omega}$$

$$3 - \frac{V_a}{5k} = \frac{V_a}{10k} \quad \Rightarrow \quad i_1 = \frac{-10kV}{5k\Omega} = -2A$$

$$30k - 2V_a = V_a \quad \Rightarrow \quad i_2 = \frac{10kV}{10k\Omega} = 1A$$

$$30k = 3V_a$$

$$V_a = 10kV$$

⇓

$$V_1 = -i_1 \cdot 3k\Omega = -(-2)(3k)$$

$$V_1 = 6kV$$


$$V_2 = i_2 \cdot 7k\Omega = 1 \cdot 7k$$

$$V_2 = 7kV$$

Finding Thevenin and Norton Equivalent Voltages/Currents

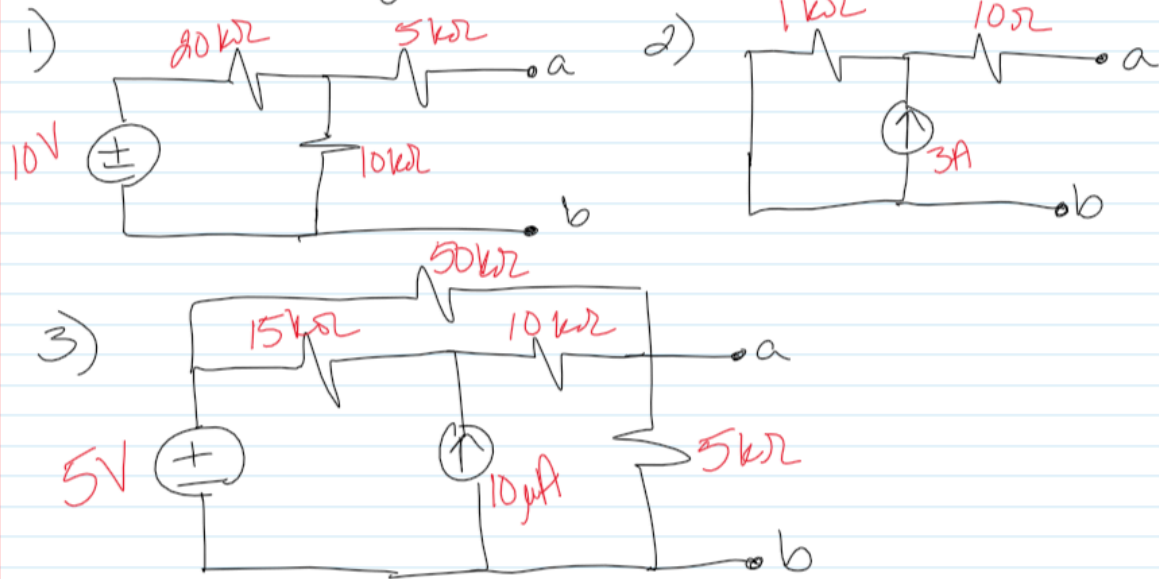Problem Set 3: Thevenin & Norton Eq. Circuits


Find both Thevenin & Norton eq. circuits for the following problems:




Solution for Problem #1

Solutions:

1)

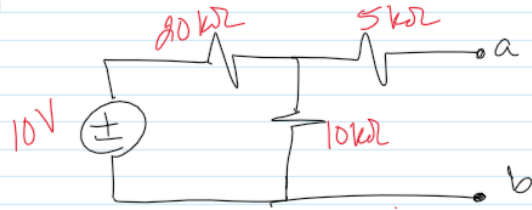


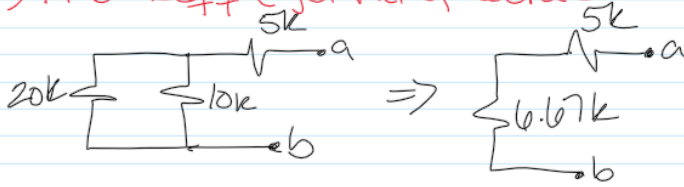1) Find R_{eq} (get rid of sources: $V \rightarrow sc / I \rightarrow oc$)




$$R_{th} = 11.67 \text{ k}\Omega$$

2) Find V_{th}

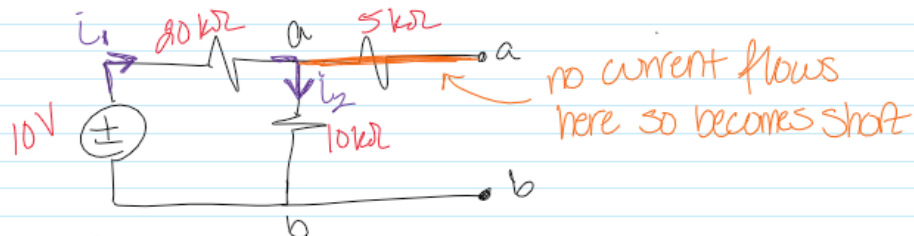

$$i_1 = i_2$$

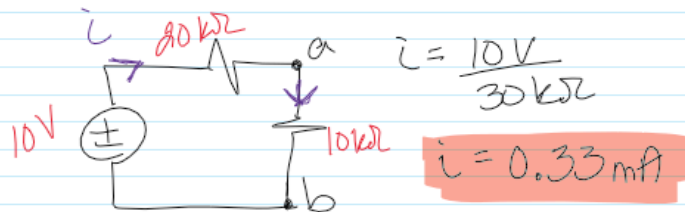

$$V_{th} = V_{ab} = i \cdot 10 \text{ k}\Omega$$


$$V_{th} = 3.3 \text{ V}$$

3) Find I_N

$$I_N = \frac{V_{th}}{R_{eq}} = \frac{3.3 \text{ V}}{11.67 \text{ k}\Omega} = 0.283 \text{ mA} = I_N$$

Solution for Problem #2


2)

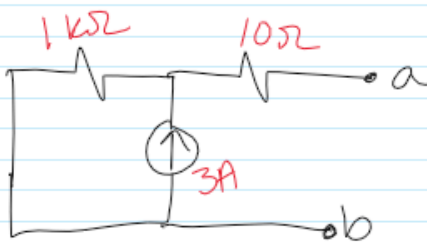

1) Find R_{th} ($I \rightarrow oc$)

$$R_{th} = 11 \text{ k}\Omega$$

2) Find V_{th}

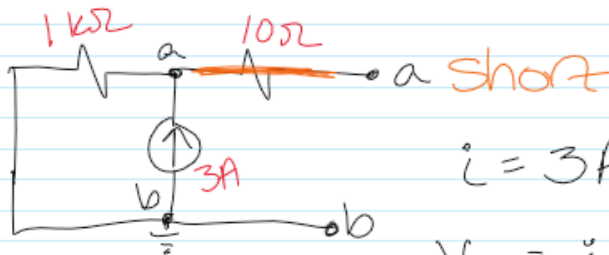

$$i = 3 \text{ A}$$


$$V_{ab} = i \cdot 1 \text{ k}\Omega = 3 \text{ kV}$$

$$\& V_{ab} = V_{th} = 3 \text{ kV}$$


3) Find I_N

$$I_N = \frac{V_{th}}{R_{eq}} = \frac{3 \text{ kV}}{11 \text{ k}\Omega} = 0.27 \text{ A} = I_N$$

Solution for Problem #3

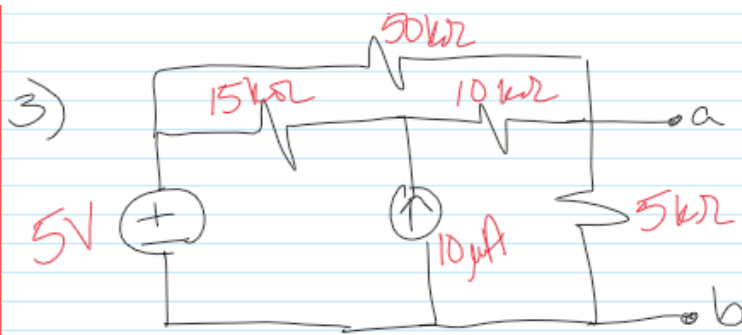


1) find R_{eq}

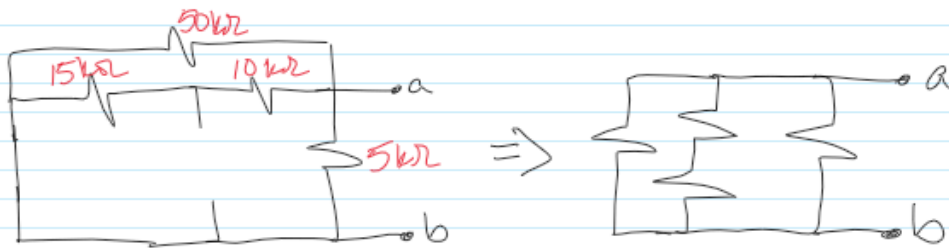

$$R_{eq} = [50k \parallel (15k + 10k)] \parallel 5k$$

$$R_{eq} = 3.85 k\Omega$$

2) find V_{th}

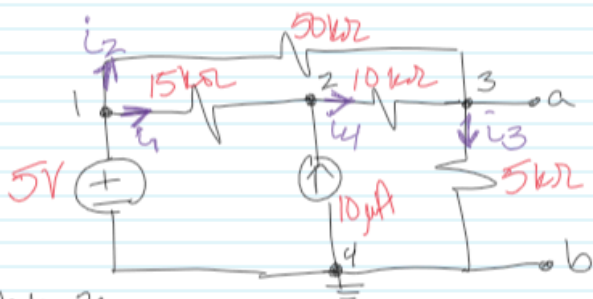

Node 2:

$$V_1 = 5V, i_1 + 10\mu A = i_4$$

$$i_1 = \frac{5 - V_2}{15k}, i_4 = \frac{V_2 - V_3}{10k}$$

$$\therefore \left(\frac{5 - V_2}{15k} + 10\mu \right) \cdot 15k = \frac{V_2 - V_3}{10k} \cdot 15k$$

$$5 - V_2 + 0.15 = 1.5V_2 - 1.5V_3$$

$$5.15 = 2.5V_2 - 1.5V_3$$

System of equations:

$$5.15 = 2.5V_2 - 1.5V_3$$

$$5 = -5V_2 + 16V_3$$

$$V_2 = 2.77V, V_3 = 1.18V$$

$$V_3 = V_{ab} = V_{th} = 1.18V$$

Node 3:

$$i_2 + i_4 = i_3$$

$$i_2 = \frac{5 - V_3}{50k}, i_3 = \frac{V_3}{5k}$$

$$\therefore \left(\frac{5 - V_3}{50k} + \frac{V_2 - V_3}{10k} \right) \cdot 50k = \frac{V_3}{5k} \cdot 50k$$

$$5 - V_3 + 5V_2 - 5V_3 = 10V_3$$

$$5 + 5V_2 - 6V_3 = 10V_3$$




$$5 = 16V_3 - 5V_2$$

3) find I_N



$$I_N = \frac{V_{th}}{R_{eq}} = \frac{1.18V}{3.85k\Omega} = 0.306mA = I_N$$

Finding Currents in a Circuit

Problem Set 4: finding currents

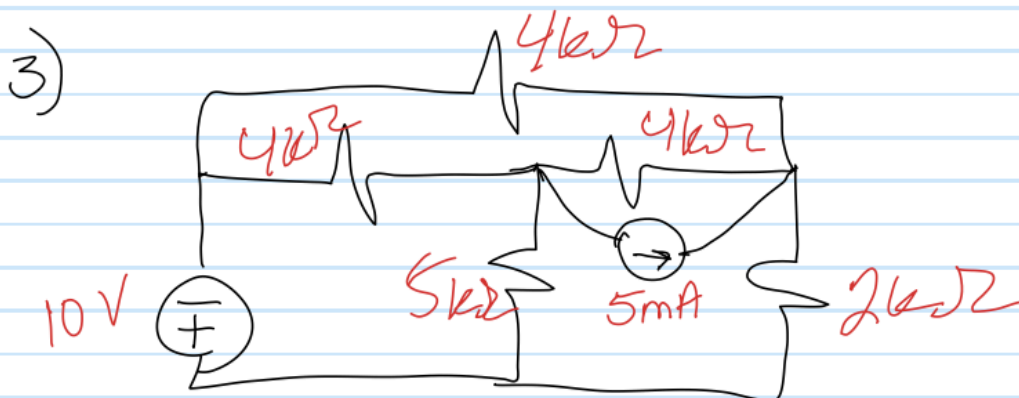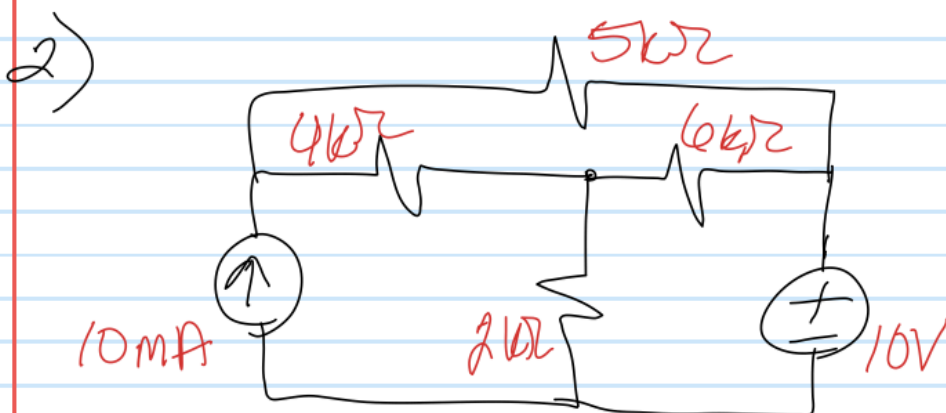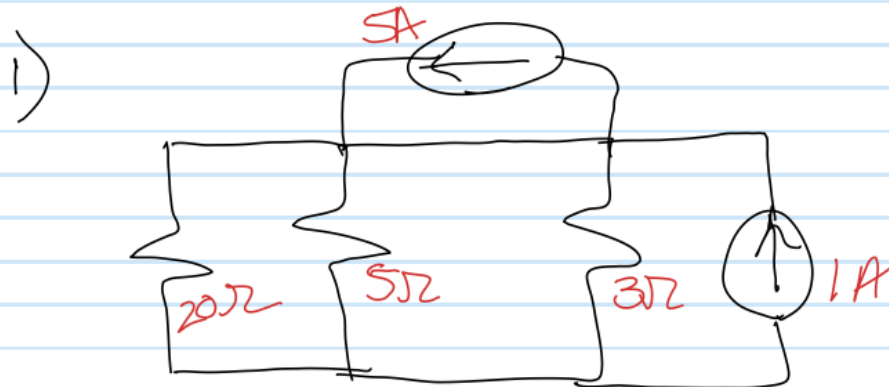

Solution for Problem #1

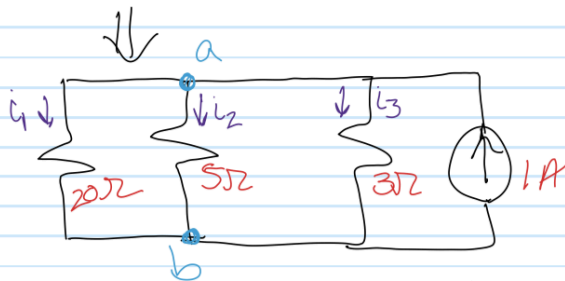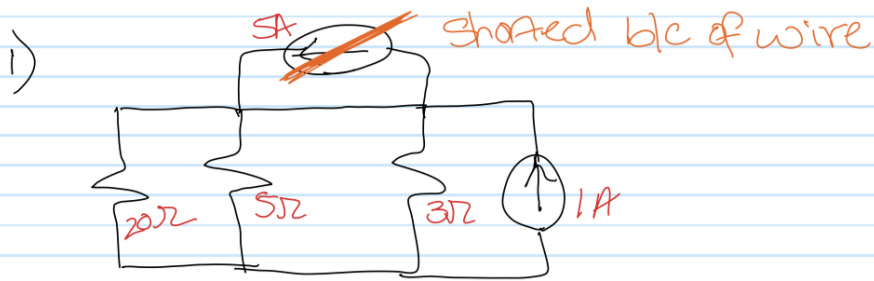

$$V_{ab} = 1A \cdot R_t$$

$$R_t = 20 \parallel 5 \parallel 3$$

$$R_t = 1.71 \Omega$$

$$\hookrightarrow V_{ab} = 1.71 V$$

$$i_1 = \frac{V_{ab}}{20\Omega}$$

$$i_2 = \frac{V_{ab}}{5\Omega}$$

$$i_3 = \frac{V_{ab}}{3\Omega}$$


$$i_1 = 0.0857 A$$

$$i_2 = 0.34 A$$

$$i_3 = 0.57 A$$

$$\approx 85.7 mA$$

Solution for Problem #2

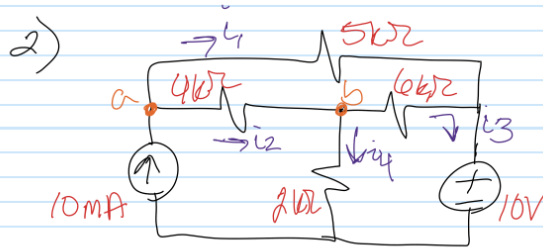

node 1: $10 \cdot 10^{-3} - i_1 - i_2 = 0$

$$\left[10 \cdot 10^{-3} - \left(\frac{V_a - 10}{5k} \right) - \left(\frac{V_a - V_b}{4k} \right) = 0 \right] 20k$$

$$200 - 4V_a + 40 - 5V_a + 5V_b = 0$$

$$9V_a - 5V_b = 240$$

node 2: $i_2 - i_3 - i_4 = 0$

$$\left[\left(\frac{V_a - V_b}{4k} \right) - \left(\frac{V_b - 10}{6k} \right) - \left(\frac{V_b}{2k} \right) = 0 \right] 12k$$

$$3V_a - 3V_b - 2V_b + 20 - 6V_b = 0$$

$$3V_a - 11V_b = -20$$

System:
$$\begin{cases} 9V_a - 5V_b = 240 \\ 3V_a - 11V_b = -20 \end{cases}$$

$$V_a = 32.62 \text{ V}$$

$$V_b = 10.7 \text{ V}$$


$$i_1 = \frac{V_a - 10}{5k} = 4.52 \text{ mA}$$

$$i_2 = \frac{V_a - V_b}{4k} = 5.48 \text{ mA}$$

$$i_3 = \frac{V_b - 10}{6k} = 0.12 \text{ mA}$$

$$i_4 = \frac{V_b}{2k} = 5.35 \text{ mA}$$

Solution for Problem #3

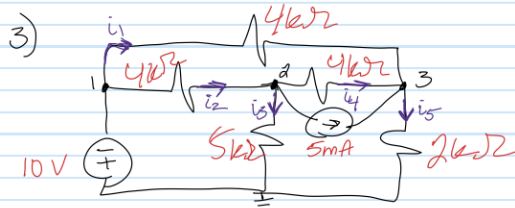

Node 1: $V_1 = -10V$ $i_1 = \frac{-10V - V_3}{4k\Omega}$
 Node 2: $i_2 - i_3 - i_4 - 5mA = 0$ $i_2 = \frac{-10V - V_2}{4k\Omega}$ $i_4 = \frac{V_2 - V_3}{4k\Omega}$
 Node 3: $i_1 + i_4 - i_5 + 5mA = 0$ $i_3 = \frac{V_2 - 0}{5k\Omega}$ $i_5 = \frac{V_3 - 0}{2k\Omega}$

Node 2:

$$\left[\frac{-10V - V_2}{4k} - \frac{V_2}{5k} - \frac{V_2 - V_3}{4k} - 5mA = 0 \right] 20k$$

$$-50 - 5V_2 - 4V_2 - 5V_2 + 5V_3 - 100 = 0$$

$$\underline{-14V_2 + 5V_3 = 150}$$

Node 3:

$$\left[\frac{-10V - V_3}{4k} + \frac{V_2 - V_3}{4k} - \frac{V_3}{2k} + 5mA = 0 \right] 4k$$

$$-10 - V_3 + V_2 - V_3 - 2V_3 + 20 = 0$$

$$\underline{-4V_3 + V_2 = -10}$$

System:

$$\begin{cases} -14V_2 + 5V_3 = 150 \\ +V_2 - 4V_3 = -10 \end{cases}$$

$$V_2 = -10.8V$$

$$V_3 = -0.2V$$

$$i_1 = \frac{-10V - V_3}{4k\Omega} = \frac{-10 - (-0.2)}{4k} = \underline{-2.45mA}$$

$$i_2 = \frac{-10V - V_2}{4k\Omega} = \frac{-10 - (-10.8)}{4k} = \underline{0.2mA}$$

$$i_3 = \frac{V_2 - 0}{5k\Omega} = \frac{-10.8}{5k} = \underline{-2.16mA}$$

$$i_4 = \frac{V_2 - V_3}{4k\Omega} = \frac{-10.8 - (-0.2)}{4k} = \underline{-2.65mA}$$

$$i_5 = \frac{V_3 - 0}{2k\Omega} = \frac{-0.2}{2k} = \underline{-0.1mA}$$