

Roll No.....

Total No. of Printed Pages: 1

Total No. of Questions: [09]

B.Sc. Hons. (Aircraft Maintenance Engineering) (Semester 1st)

ELECTRICAL FUNDAMENTALS - I

Sub code: BAME3-105

Paper ID: [20131103]

Time: 03 Hours

Maximum Marks: 60

Instruction for candidates:

1. Section A is compulsory. It consists of 10 parts of two marks each.
2. Section B consist of 5 questions of 5 marks each. The student has to attempt any 4 questions out of it.
3. Section C consist of 3 questions of 10 marks each. The student has to attempt any 2 questions.

Section – A

(2 marks each)

Q1. Attempt the following:

- a) Define RC time constant with the help of charging curve of capacitor.
- b) Define Kirchoff's law.
- c) An emf source of 6 V is connected to a purely resistive lamp and a current of 2 amperes flows. What is the resistance of the lamp?
- d) Write short note on series DC circuit and parallel DC circuit.
- e) Find the equivalent resistance when the 1Ω and $10^3\Omega$ and $10^6\Omega$ resistances are connected in parallel.
- f) Write down the factors on which capacitance of the capacitor depends?
- g) Define the advantages of transformer.
- h) In a series RLC circuit, if the current at resonance is 10A, then the current corresponding to half power delivered is
- i) Define Faraday's laws of electromagnetic induction.
- j) Write short note on Variable Resistor.

Section – B

(5 marks each)

- Q2. Describe the Precautions to be taken while handling ESD components.
- Q3. Explain the working and applications of Thermistors and Photo conductive cells.
- Q4. Explain the procedure to find the value of unknown resistance by Resistor color coding method.
- Q5. Explain the operation of T type and π type filters.
- Q6. Differentiate between Series Resonant circuit and Parallel Resonant circuit.

Section – C

(10 marks each)

- Q7. Explain the coefficient of self-induction and mutual induction. Also derive the expression for coefficient of coupling.
- Q8. Explain the types of Magnets and Magnetic hysteresis loop in detail.
- Q9. Explain the Active power, Reactive power, apparent power, Power factor and Q factor of a coil.