

Electric Circuits

1. Describe what is an electric current.
2. What is a simple circuit?
3. Describe what is current.
4. Explain what is voltage.