

1-Build an Adder circuit which add two 4-bit numbers by using a 4-bit parallel adder .
(using the 7483)





