

1. Complete the truth table for a half adder

Input A	Input B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Explanation:

A Half Adder performs binary addition of two bits.

- $\text{Sum} = A \oplus B$
 - $\text{Carry} = A \cdot B$
-

2. What is the main difference between a half adder and a full adder?

- **Half Adder:** Adds two input bits (A and B). It cannot handle carry input from a previous addition.
- **Full Adder:** Adds three bits — A, B, and a carry input (Cin) — and produces a Sum and Carry output.
 - o Formula:
 - $\text{Sum} = A \oplus B \oplus \text{Cin}$
 - $\text{Carry} = (A \cdot B) + (\text{Cin} \cdot (A \oplus B))$

A full adder includes the carry input; a half adder does not.

3. Using the full 4-bit adder in the slide, draw the full 2-bit adder. Then, add the following binary numbers:

Let's perform both additions step by step.

(a) 01 + 11

```
  0 1
+ 1 1
-----
 1 00
```

Result: 100 (3 + 1 = 4 in decimal)

(b) 10 + 11

$$\begin{array}{r}
 10 \\
 + 11 \\
 \hline
 101
 \end{array}$$

Result: 101 (2 + 3 = 5 in decimal)

4. Using the full 4-bit subtractor, draw the logic circuit of a 2-bit subtractor. Label the inputs and outputs. Then compute:

Subtraction uses the formula:

$$\mathbf{A - B = A + (2's\ complement\ of\ B)}$$

That means:

1. Invert each bit of B
 2. Add 1 to the least significant bit (LSB)
-

(a) 10 – 01

$$\begin{array}{r}
 10 \\
 - 01 \\
 \hline
 01
 \end{array}$$

Result: 01 (2 – 1 = 1 in decimal)

(b) 11 – 10

$$\begin{array}{r}
 11 \\
 - 10 \\
 \hline
 01
 \end{array}$$


Result: 01 (3 – 2 = 1 in decimal)

Operation	Result (Binary)	Result (Decimal)
01 + 11	100	4
10 + 11	101	5
10 – 01	01	1


Operation Result (Binary) Result (Decimal)

11 – 10 01 1

2-bit Adder

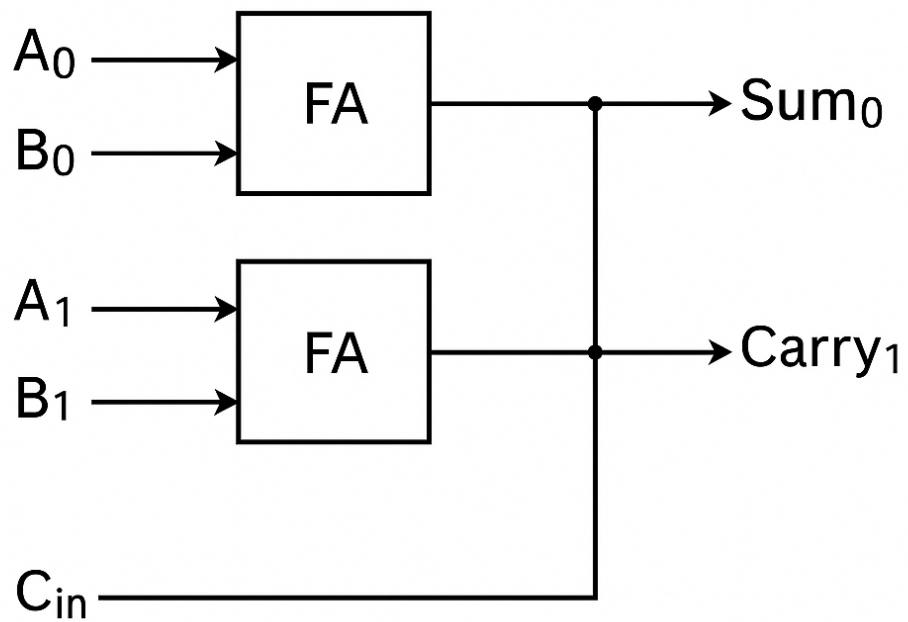

2-bit Subtractor

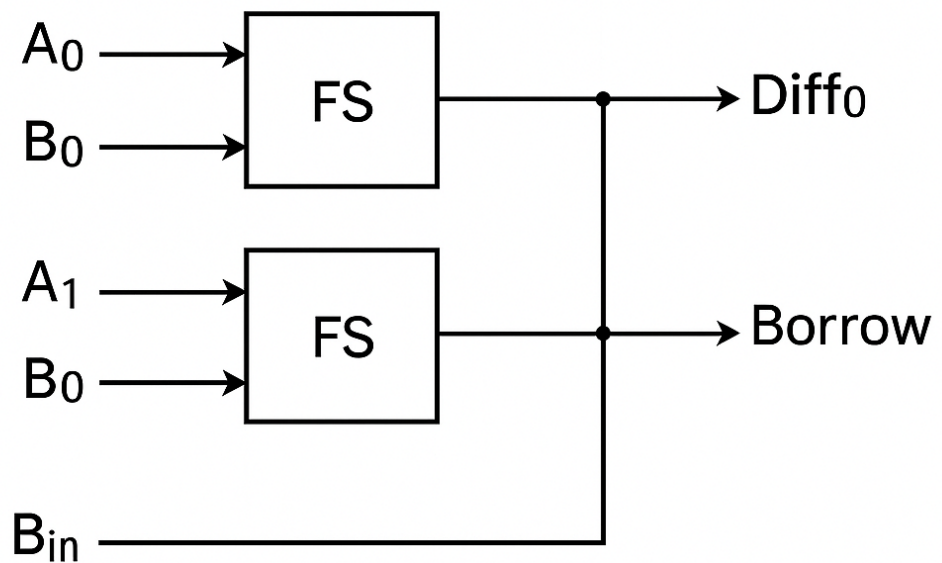

////////////////////////////////////
////////////////////////////////////
////////////////////////////////////

1] Half Adder (Truth Table) أكمل جدول الصواب

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

الشرح:

(A و B) يجمع بتين Half Adder الـ

- **Sum = A XOR B** ناتج
- **Carry = A AND B** ناتج

فمثلاً:

- $A=1$ و $B=0 \Rightarrow \text{Sum}=1, \text{Carry}=0$ إذا كانت
- $A=1$ و $B=1 \Rightarrow \text{Sum}=0, \text{Carry}=1$ إذا كانت

2] Full Adder و Half Adder ما الفرق الرئيسي بين

♦ **Half Adder:**

من عملية سابقة (Carry-in) ولا يأخذ بالحسبان أي حمل، (A و B) يجمع بتين فقط

المدخلات: A, B

المخرجات: Sum, Carry

♦ **Full Adder:**

(من عملية سابقة Carry-in و A، B،) يجمع 3 بتات

المدخلات: A, B, Cin

المخرجات: Sum, Carry-out

✓ الفرق الرئيسي:

Half بينما الـ (bit adder) يمكن استخدامه في عمليات الجمع المتسلسلة (مثل Full Adder الـ 4) لا يمكنه التعامل مع الحمل من العمليات السابقة Adder

واحسب bit adder-ارسم 2، bit adder-باستخدام 4

أ) $(11 + 01)$

ب) $(11 + 10)$

(Full Adders): من خلال توصيل مجمعين كاملين bit adder-يمكنك تمثيل 2

- لجمع البت الأقل FA أول (LSB)
- مع حمل من الأول (MSB) لجمع البت الأعلى FA ثاني

أ) $(11 + 01)$

$$\begin{array}{r} 01 \\ + 11 \\ \hline 100 \end{array}$$

✓ (أي الناتج الفعلي هو 100 (4 بالعشري $\rightarrow \text{Carry} = 1$ الناتج = 00 مع).

ب) $(11 + 10)$

$$\begin{array}{r} 10 \\ + 11 \\ \hline 101 \end{array}$$

✓ (الناتج الفعلي 101 (5 بالعشري $\rightarrow \text{Carry} = 1$ الناتج = 01 مع).

واحسب bit subtractor-ارسم 2، bit subtractor-باستخدام 4

أ) $(01 - 10)$

ب) $(10 - 11)$

Full Subtractor في الطرح الثنائي نستخدم دائرة المعادلات الأساسية:

- $\text{Difference} = A \text{ XOR } B \text{ XOR Bin}$
- $\text{Borrow} = (\neg A \text{ AND } B) \text{ OR } (\text{Bin AND } \neg(A \text{ XOR } B))$

أ) $(01 - 10)$

$$\begin{array}{r} 10 \\ - 01 \\ \hline 01 \end{array}$$


✓ Borrow. الناتج = 01 (1 بالعشري) بدون

ب) 11 - 10

$$\begin{array}{r} 11 \\ - 10 \\ \hline 01 \end{array}$$

✓ Borrow. الناتج = 01 (1 بالعشري) بدون

2-bit Adder

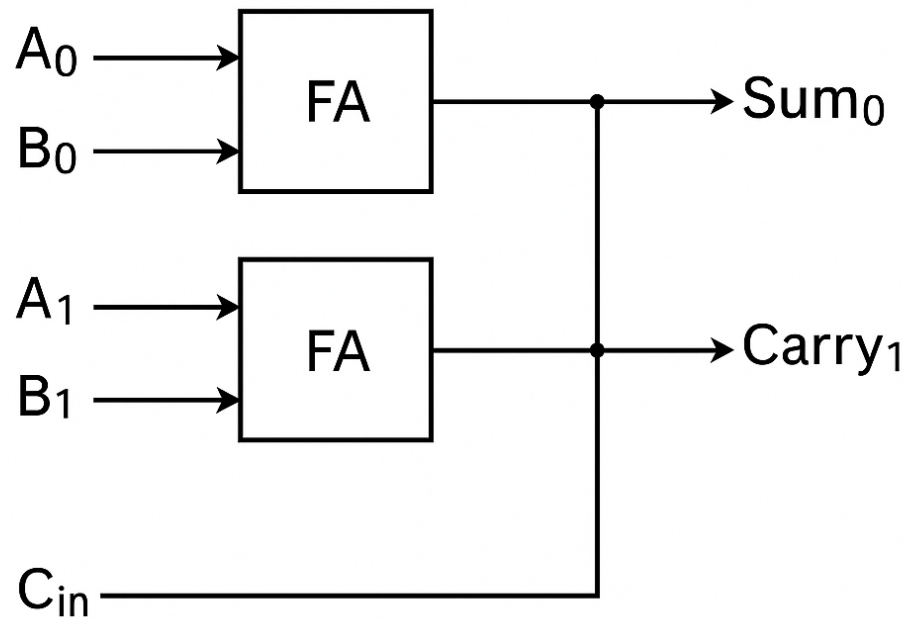

2-bit Subtractor

