

PREVIOUS YEAR QUESTIONS

(Chapterwise)

CHAPTER NAME: CURRENT ELECTRICITY

SUMMARY POINTS

Concept	Key Points & Formulae	SI Units
Electric Current (I)	- Rate of flow of charge: $I = \frac{Q}{t}$, where Q is charge and t is time.	- Ampere (A)
Ohm's Law	- $V = IR$, where V is voltage, I is current, and R is resistance.	- Volt (V), Ohm (Ω)
Resistance (R)	- $R = \frac{\rho L}{A}$, where ρ = resistivity, L = length, A = cross-sectional area.	- Ohm (Ω)
Resistivity (ρ)	- $\rho = R \frac{A}{L}$.	- Ohm-meter ($\Omega\cdot m$)
Conductance (G)	- Reciprocal of resistance: $G = \frac{1}{R}$.	- Siemens (S)
Series Combination of Resistors	- Total resistance: $R_{\text{total}} = R_1 + R_2 + \dots + R_n$.	- Ohm (Ω)
Parallel Combination of Resistors	- Total resistance: $\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$.	- Ohm (Ω)
Power (P)	- Rate of energy consumption: $P = VI = I^2R = \frac{V^2}{R}$.	- Watt (W)
Energy (E)	- $E = Pt = VIt$, where t = time.	- Joule (J)

Key Formulas and Notes:

Formulas

1. Current:

$$I = \frac{Q}{t}$$

2. Ohm's Law:

$$V = IR$$

3. Resistance:

$$R = \frac{\rho L}{A}$$

4. Series Combination:

$$R_{\text{total}} = R_1 + R_2 + \dots + R_n$$

5. Parallel Combination:

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

6. Power:

$$P = VI = I^2 R = \frac{V^2}{R}$$

7. Energy:


$$E = Pt = VIt$$

Key Notes:

- **Ohm's Law:** Voltage is directly proportional to current for a constant resistance.
- **Factors affecting resistance:**
 - Length of conductor: $R \propto L$.
 - Area of cross-section: $R \propto \frac{1}{A}$.
 - Material: $R \propto \rho$, where ρ is resistivity.
- **Resistivity** depends only on material and temperature.
- **Power in Circuits:** Higher resistance reduces current and hence decreases power consumption.

Q.NO.: 1	The specific resistance of a conductor depends on its: (a) length (b) material (c) area of cross section (d) radius	YEAR [2024]
ANS.:	(b) material	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 2	The potential difference between terminals of a cell in a closed electric circuit is: (a) terminal voltage (b) electro motive force (c) voltage drop (d) none of these	YEAR [2024]
ANS.:	(a) terminal voltage.	
TOPIC:	Page No.:	Ref. Link

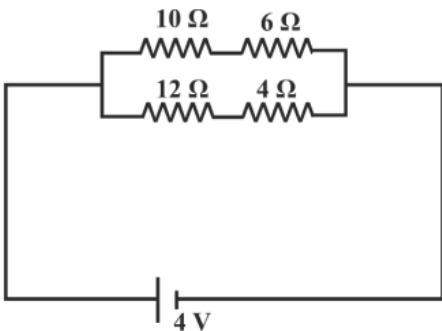Q.NO.: 3	Study the diagram:  (a) Calculate the total resistance of the circuit. (b) Calculate the current drawn from the cell. (c) State whether the current through 10 Ω resistor is greater than, less than or equal to the current through the 12 Ω resistor.	YEAR [2024]
ANS.:		
TOPIC:	Page No.:	Ref. Link

Q.NO.: 4	When a current I flows through a wire of resistance R for time t then the electrical energy produced is given by: a. $F \cdot Rt$ b. I^2Rt c. IRt d. IRt^2	YEAR [2023]
ANS.:	The electrical energy produced is given by I^2Rt. Explanation: This formula is also used for heat energy and is a standard relationship in current electricity.	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 5	Choose the correct relation for e.m.f.(ϵ) and terminal voltage V: a. $\epsilon = V$ [always] c. $V < \epsilon$ [when the cell is in use] b. $V > \epsilon$ [always] d. None of these	YEAR [2023]
----------	---	------------------------

ANS.:	Terminal voltage is less than EMF when the cell is in use $\{V > \varepsilon \text{ [always]}\}$. Explanation: When a cell is in use, there is a voltage drop due to internal resistance, thus the terminal voltage is less than the EMF of the cell.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 6	'A geyser is rated 240 W - 220 V'. Explain the meaning of this statement.	YEAR [2023]
ANS.:	It means that when the geyser is operated on a 220V supply, it consumes 240 W of electric power, or it consumes 240 Joules of electrical energy in one second. Explanation: This describes the power rating of the geyser under standard operating conditions.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 7	(a) Define specific resistance. (b) What happens to the specific resistance of a conductor if its length is doubled? (c) Name a substance whose specific resistance remains almost unchanged with the increase in its temperature.	YEAR [2023]
ANS.:	(a) Specific resistance (also known as resistivity) is the resistance of a material with a unit length and a unit cross-sectional area . It is a measure of how strongly a material opposes the flow of electric current. The specific resistance of a material is the resistance of a wire of that material with unit length and unit area of cross section. (b) • If the length of a conductor is doubled, its specific resistance remains unchanged . • Specific resistance does not depend on the dimensions of the wire (like length or cross-sectional area). It is an intrinsic property of the material. (c) Manganin is a substance whose specific resistance remains almost unchanged with an increase in its temperature.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 8	Find the value of current I drawn from the cell. (a) Calculate the current I. (b) Calculate the terminal voltage.	YEAR [2023]
-----------------	--	------------------------------

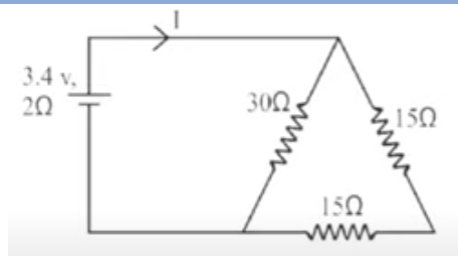

ANS.:

(a) To calculate the current, you need the total electromotive force (EMF) and the total resistance of the circuit.

- The **EMF** of the cell is given as **3.4 volts**.
- The circuit contains a **2-ohm** resistor that is part of the cell and a combination of resistors arranged in a triangle.
- The triangle consists of two **15-ohm** resistors in series and a **30-ohm** resistor.
- The two 15-ohm resistors in series are equivalent to a 30-ohm resistance ($15 + 15 = 30$).
- The 30-ohm resistor and the equivalent 30-ohm from the series pair are in parallel, which gives an effective resistance of 15 ohms. This is calculated using the formula $1/R_p = 1/30 + 1/30$, resulting in $R_p = 15$.
- The total resistance of the circuit is the parallel resistance plus the internal resistance of the battery:
15 ohms + 2 ohms = 17 ohms.

- Using Ohm's Law ($I = \text{EMF} / \text{Total Resistance}$), the current is calculated as:
 $I = 3.4 \text{ V} / 17 \text{ ohms} = 0.2 \text{ A}$

(b) Calculating the Terminal Voltage

- Terminal voltage is the potential difference across the terminals of the cell.
- To calculate the terminal voltage, only the external resistance is considered and not the internal resistance of the battery.
- The external resistance in this case is the equivalent resistance of the resistor combination, which is 15 ohms.
- Using Ohm's Law again, the terminal voltage (V) is calculated as: **$V = I * R$** .
- The current I is 0.2 amperes and external resistance R is 15 ohms.
- Therefore, the terminal voltage **$V = 0.2 \text{ A} * 15 \text{ ohms} = 3 \text{ volts}$**

TOPIC:

Page No.:

[Ref. Link](#)


Q.NO.: 9

The graph plotted for potential difference (V) against current (I) for ohmic resistors is:

- a. A curve passing through the origin.**
- b. A straight line not passing through origin.**
- c. A straight line passing through the origin.**

YEAR
[2022]

	d. A circle centred at the origin.	
ANS.:	(c) A straight line passing through the origin. <i>Explanation:</i> This is a characteristic of ohmic resistors, where the voltage and current are directly proportional.	
TOPIC:	Page No.:	Ref. Link

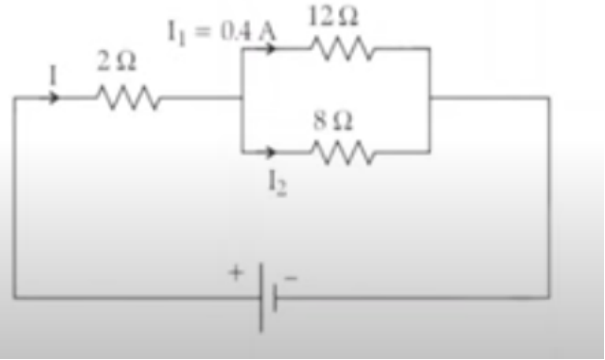Q.NO.: 10	In the below circuit diagram, calculate: (a) the external resistance of the circuit. (b) the current i^2 (c) the current i. 	YEAR [2022]
ANS.:	(a) External resistance: 6.8Ω. The resistors are connected in parallel, and the result of that is then added to the remaining resistance in series. (b) Current i^2: 0.6 A. Ohm's law and the principle that voltage is the same across parallel branches was used to calculate the current i^2. (c) Total current i: 1 A. Total current was found by adding the currents in the parallel paths. <i>Explanation:</i> This problem uses series and parallel resistance rules and Ohm's law to solve.	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 11	An appliance rated 440 W, 220V is connected across 220V supply. (a) Calculate the maximum current that the appliance can draw. (b) Calculate the resistance of the appliance.	YEAR [2022]
------------------	--	--------------------------------------

ANS.:	(a) Maximum Current: 2 A. Calculated by dividing power by voltage ($I = P/V$). (b) Resistance: 110 Ω. Calculated using ($R = V^2/P$) or Ohm's law. Explanation: Power and voltage ratings are used to calculate current and resistance.	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 12	If a wire of resistance 25 gets stretched to thrice its original length: (a) Calculate the new resistance of the wire. (b) What happens to the specific resistance of the wire?	YEAR [2022]
ANS.:	(a) New resistance: 18 Ω. The calculation accounts for the increase in length and corresponding decrease in area. (b) Specific resistance: Remains unchanged. Specific resistance depends only on the material, not dimensions. Explanation: This problem shows the effect of changing dimensions on resistance while remembering that specific resistance is an intrinsic property.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 13	Define a kilowatt hour. How is it related to joule?	YEAR [2020]
ANS.:	A kilowatt-hour is the energy spent or work done by a source of 1kW power in 1 hour. $1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$. Explanation: This defines a unit of energy used in electrical contexts and gives the conversion to Joules.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 14	Calculate the total resistance across AB.	YEAR [2020]
------------------	--	------------------------------

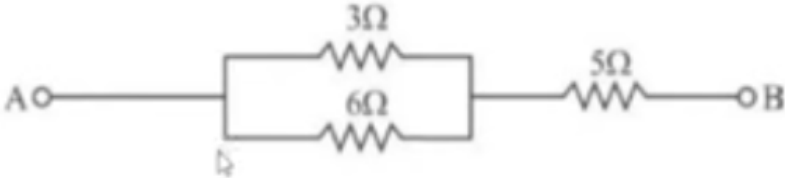
		
ANS.:	7 Ω. Series and parallel combinations of resistors are used to find the total resistance. Explanation: This involves combining parallel resistances and then adding them to series resistances.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 15	(i) What are superconductors? (ii) Calculate the current drawn by an appliance rated 110 W, 220 V when connected across 220 V supply. (iii) Name a substance whose resistance decreases with the increase in temperature.	YEAR [2020]
ANS.:	(i) Superconductors are materials with zero resistance at very low temperatures. (ii) 0.5 A. Calculated using $I = P / V$ (iii) Carbon or Silicon Explanation: This question covers superconductors, current calculation, and materials with a negative temperature coefficient of resistance.	
TOPIC:	Page No.:	Ref. Link

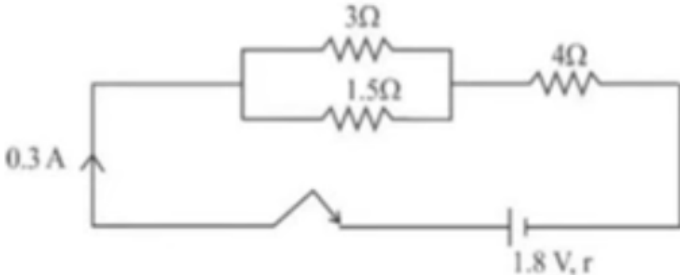
Q.NO.: 16	 The diagram above shows three resistors connected across a cell of e.m.f. 1.8 V and internal resistance r.	YEAR [2020]
------------------	--	--------------------------------------

	Calculate: (i) Current through 3Ω resistor. (ii) The internal resistance r.	
ANS.:	(i) Current through 3Ω resistor: 0.1 A. The potential across the parallel combination is used and Ohm's law then gives the current. (ii) Internal resistance: 1Ω. The formula $E = I(R + r)$ was used to calculate the internal resistance. Explanation: This involves using Ohm's law and internal resistance to solve.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 17	How does an increase in the temperature affect the specific resistance of (i) Metal and (ii) Semiconductor?	YEAR [2019]
ANS.:	(i) Metal: Specific resistance increases; (ii) Semiconductor: Specific resistance decreases. Explanation: This describes the temperature dependence of resistivity for different materials.	
TOPIC:	Page No.:	Ref. Link

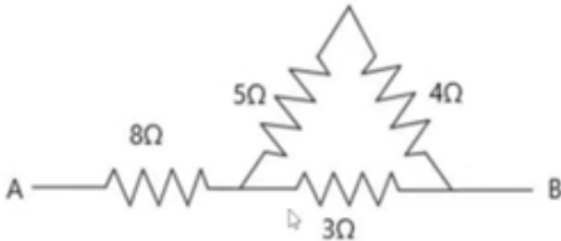Q.NO.: 18	Calculate the effective resistance across AB:- 	YEAR [2019]
ANS.:	10.25 Ω. Series and parallel combinations are used to get the total resistance. Explanation: Series and parallel resistor combinations are key to solving this problem.	

TOPIC:	Page No.:	Ref. Link
--------	-----------	---------------------------

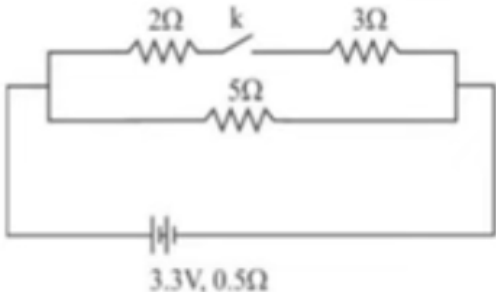Q.NO.: 19	 The diagram above shows a circuit with the key k open. Calculate: (i) the resistance of the circuit when the key k is open. (ii) the current drawn from the cell when the key k is open. (iii) the resistance of the circuit when the key k is closed. (iv) the current drawn from the cell when the key k is closed.	YEAR [2019]
ANS.:	(i) Resistance when k is open: 5.5 Ω (ii) Current when k is open: 0.6 A (iii) Resistance when k is closed: 3 Ω (iv) Current when k is closed: 1.1 A Explanation: This problem focuses on circuit behavior under different conditions (open and closed key), involving series and parallel circuit analysis.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 20	You have three resistors of values 2Ω, 3Ω and 5Ω. How will you join them so that the total resistance is more than 7Ω? (i) Draw a diagram for the arrangement. (ii) Calculate the equivalent resistance.	YEAR [2018]
ANS.:	(i) The resistors are joined in series. (ii) The equivalent resistance is 10 Ω.	

	Explanation: To obtain the maximum equivalent resistance, the resistors are connected in series.	
TOPIC:	Page No.:	Ref. Link

Q.NO.:21	Find the equivalent resistance between A and B. 	YEAR [2018]
ANS.:	5 Ω Explanation: This involves calculating the resistance of two parallel sets of resistors and then adding them in series.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 22	An electric iron is rated 220V, 2kW. If the iron is used for 2h daily find the cost of running it for one week if it costs 4.25 per kWh.	YEAR [2018]
ANS.:	The total energy consumed is 28 kWh, and the cost is ₹119. Explanation: The problem combines power consumption, time, and cost calculations.	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 23	An electric bulb of resistance 500S, draws a current of 0.4A. Calculate the power of the bulb and the potential difference at its end.	YEAR [2017]
ANS.:	Power is 80 W and potential difference is 200 V. Explanation: Ohm's law and power relationships are used to solve.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 24	A music system draws a current of 400 mA when connected to a 12 V battery. (i) What is the resistance of the music system? (ii) The music system is left playing for several hours and finally the battery	YEAR [2016]
ANS.:	(i) Resistance: 30 Ω (ii) Voltage: 9.6 V Explanation: The same resistance value is used to find the voltage with the new current.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 25	Calculate the quantity of heat produced in a 2Ω resistor carrying 2.5A current in 5 minutes.	YEAR [2016]
ANS.:	37500 J. Explanation: This uses the formula for heat ($H = I^2Rt$).	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 26	What happens to the resistivity of semi-conductors with the increase of temperature?	YEAR [2015]
ANS.:	The resistivity decreases. Explanation: This discusses the behavior of semiconductors with respect to temperature.	
TOPIC:	Page No.:	Ref. Link


Q.NO.: 27	Find the equivalent resistance between points A and B.	YEAR [2015]
-----------	--	---------------------------------------

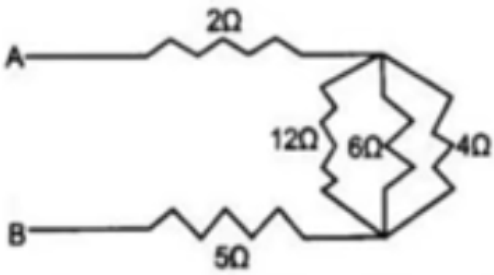		
ANS.:	9 Ω.	
	<i>Explanation:</i> This involves series and parallel combinations of resistors.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 28	The relationship between the potential difference and the current in a conductor is stated in the form of a law. (i) Name the law. (ii) What does the slope of V-I graph for a conductor represent? (iii) Name the material used for making the connecting wire.	YEAR [2015]
ANS.:	(i) Ohm's law (ii) Resistance (iii) Copper	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 29	A cell of e.m.f. 2 V and internal resistance 1.2 Ω is connected with an ammeter of resistance 0.8 Ω and two resistors of 4.5 Ω and 9 Ω as shown in the diagram below	YEAR [2015]
-----------	---	------------------------------

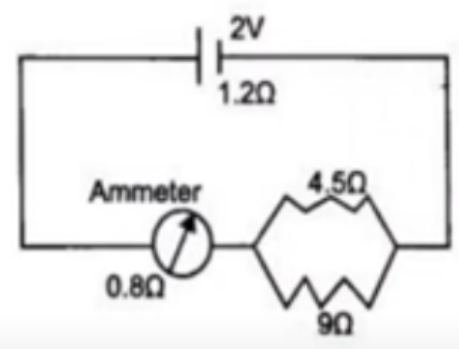	 (i) What would be the reading on the Ammeter? (ii) What is the potential difference across the terminals of the cell?	
ANS.:	(i) Ammeter Reading: 0.4 A (ii) Terminal Voltage: 1.52 V Explanation: This problem focuses on the use of Ohm's law and understanding of internal resistance and terminal voltage.	
TOPIC:	Page No.:	Ref. Link

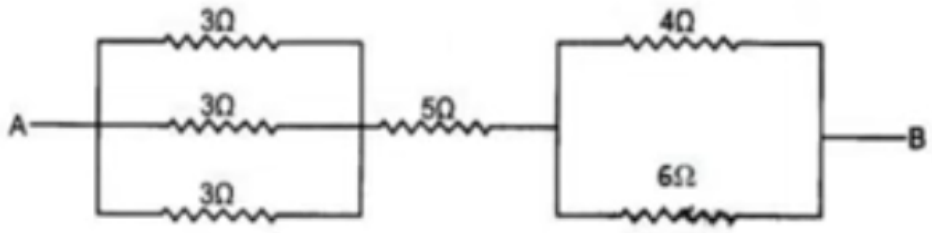Q.NO.: 30	Find the equivalent resistance between points A and B. 	YEAR [2014]
ANS.:	8.4 Ω. Explanation: Series and parallel resistor combinations are used to solve the problem.	
TOPIC:	Page No.:	Ref. Link

Q.NO.: 31	(a) Two resistors of 4Ω and 6Ω are connected in parallel to a cell to draw 0.5 A current from the cell.	YEAR [2014]
-----------	--	--------------------------------------

	(i) Draw a labelled circuit diagram showing the above arrangement. (ii) Calculate the current in each resistor. (b) (i) What is an Ohmic resistor? (ii) Two copper wires are of the same length, but one is thicker than the other. (1) Which wire will have more resistance? (2) Which wire will have more specific resistance?	
ANS.:	(a) (ii) Current in 4Ω resistor: 0.3 A Current in 6Ω resistor: 0.2 A Explanation: This problem combines circuit drawing with current distribution in a parallel circuit. (b) (i) A resistor that obeys Ohm's law. (ii) (1) Thin wire has more resistance (2) Specific resistance is the same for both. Explanation: This describes the properties of ohmic resistors and resistance relative to dimensions and material.	
TOPIC:	Page No.:	Ref. Link