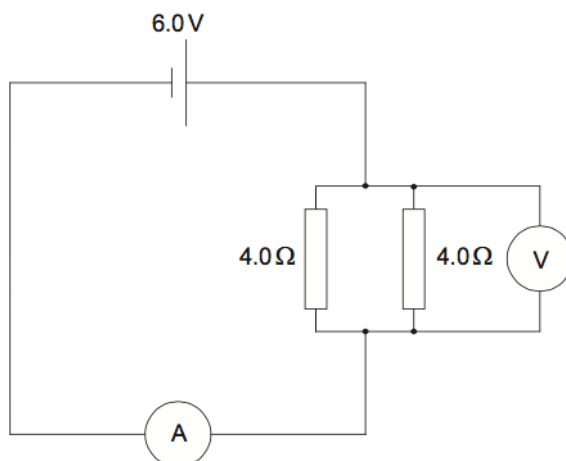


emf and Ir topic questions


1. A circuit consists of a cell of electromotive force (emf) 6.0V and negligible internal resistance connected to two resistors of 4.0Ω .



The ammeter has resistance equal to 1.0Ω and the voltmeter is ideal. What are the readings of the ammeter and the voltmeter?

| | Ammeter | Voltmeter |
|----|----------------|------------------|
| A. | 2.0A | 3.0V |
| B. | 3.0A | 3.0V |
| C. | 2.0A | 4.0V |
| D. | 3.0A | 4.0V |

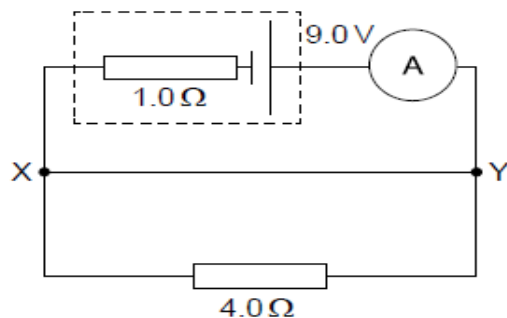
2. A circuit contains a cell of electromotive force (emf) 9.0 V and internal resistance $1.0\ \Omega$ together with a resistor of resistance $4.0\ \Omega$ as shown. The ammeter is ideal. XY is a connecting wire.



What is the reading of the ammeter?

- A. 0 A
- B. 1.8 A
- C. 9.0 A
- D. 11 A

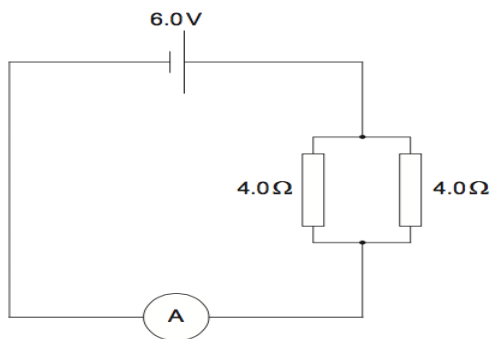
3. A circuit consists of a cell of electromotive force (emf) 6.0V and negligible internal resistance connected to two resistors of $4.0\ \Omega$.



The resistance of the ammeter is $1.0\ \Omega$. What is the reading of the ammeter?

- A. 2.0A
- B. 3.0A
- C. 4.5A
- D. 6.0A

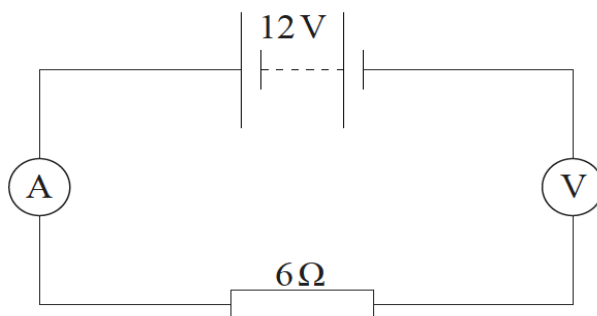
4. A battery of emf 12 V and negligible internal resistance is connected to a resistor of constant resistance $6\ \Omega$, an ideal ammeter and an ideal voltmeter.



What is the reading on the ammeter and on the voltmeter?

| | Ammeter reading / A | Voltmeter reading / V |
|----|---------------------|-----------------------|
| A. | 2.0 | 0 |
| B. | 2.0 | 12 |
| C. | 0 | 0 |
| D. | 0 | 12 |

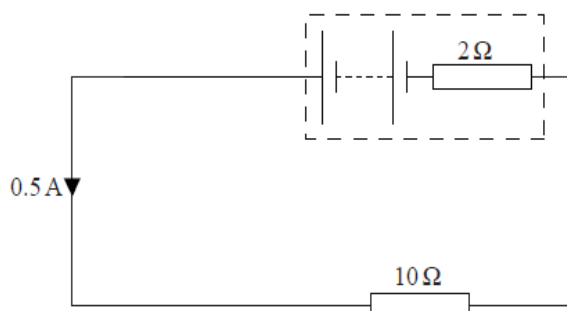
5. A battery of internal resistance $2\ \Omega$ is connected to an external resistance of $10\ \Omega$. The current is 0.5 A.



What is the emf of the battery?

- A. 1.0 V
- B. 5.0 V
- C. 6.0 V
- D. 24.0 V

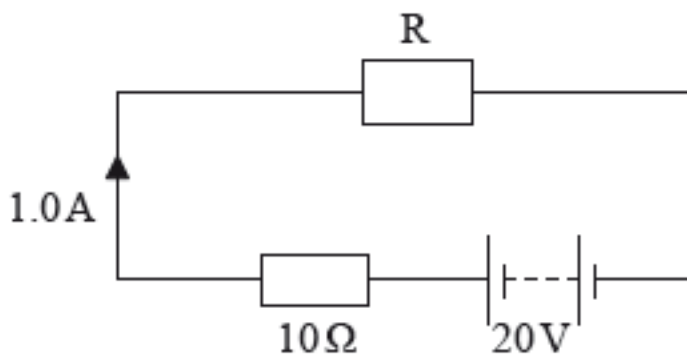6. The circuit shows a resistor R connected in series with a battery and a resistor of resistance $10\ \Omega$. The emf of the battery is 20 V and it has negligible internal resistance. The current in the circuit is 1.0 A.




Which of the following is the resistance of R?

- A. $1.0\ \Omega$
- B. $2.0\ \Omega$
- C. $10\ \Omega$
- D. $20\ \Omega$

7. A battery of emf 6.0V is connected to a $2.0\ \Omega$ resistor. The current in the circuit is 2.0A. The internal resistance of the battery is

- A. zero.
- B. $1.0\ \Omega$.
- C. $3.0\ \Omega$.
- D. $4.0\ \Omega$.

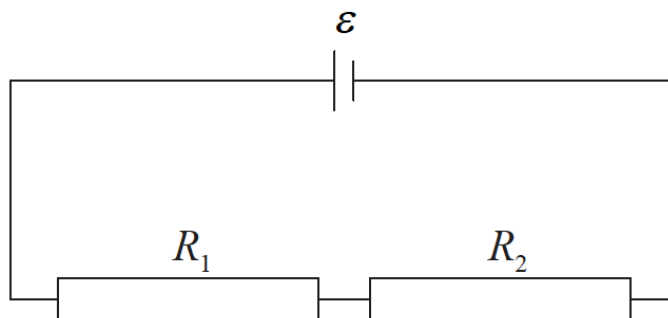8. Two resistors, of resistance R_1 and R_2 , are connected in series with a cell of emf \mathcal{E} and negligible internal resistance.



Which expression gives the potential difference across the resistor of resistance R_1 ?

A. $\left(\frac{R_1}{R_1 + R_2} \right) \mathcal{E}$

B. $\left(\frac{R_1 + R_2}{R_1} \right) \mathcal{E}$


C. $\left(\frac{R_2}{R_1 + R_2} \right) \mathcal{E}$

D. $\left(\frac{R_1 + R_2}{R_2} \right) \mathcal{E}$

9. The electromotive force (emf) of a cell is defined as

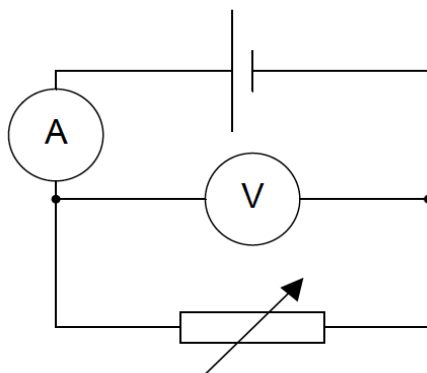- A. the power supplied by the cell per unit current from the cell.
- B. the force that the cell provides to drive electrons round a circuit.
- C. the energy supplied by the cell per unit current from the cell.
- D. the potential difference across the terminals of the cell.


10a. In an experiment a student constructs the circuit shown in the diagram. The ammeter and the voltmeter are assumed to be ideal.



State what is meant by an ideal voltmeter.

| |
|--|
| <p>.....</p> <p>.....</p> <p>.....</p> |
|--|

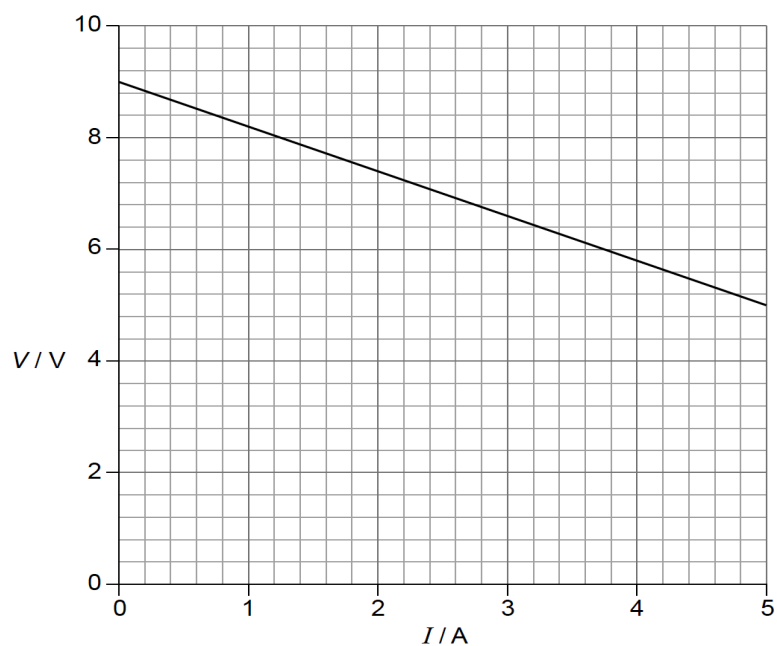10b. The student adjusts the variable resistor and takes readings from the ammeter and voltmeter. The graph shows the variation of the voltmeter reading V with the ammeter reading I .



Use the graph to determine

(i) the electromotive force (emf) of the cell.

(ii) the internal resistance of the cell.

.....

.....

.....

.....

.....

.....