

# [Network Analysis & Synthesis]

---

[Question Bank]

*BY*

***Parashuram***

**[23-05-2024]**

**Q1.** Sketch the following signals.

(I)  $t^2 [u(t-1) - u(t-3)]$

(II)  $5u(t+2) + 10u(t-4) - 20u(t-6)$

(III)  $u(t) + \sum_{k=-1}^{\infty} (-1)^k 3u(t-k)$

**Q2.** What do you mean by network analysis and synthesis?

**Q3.** What is unit step function? What is its relationship with unit impulse function?

**Q4.** Make symbols of ideal dependent current source, ideal dependent voltage source, ideal independent current source and ideal independent voltage source.

**Q5.** Write the equation of currents and voltages across inductor and capacitor with respect to time 't'.

**Q6.** Define unit step function, unit ramp function, unit impulse function and unit doublet Function?

**Q7.** A step voltage of 10V is applied at  $t=0$  in a series RC circuit where  $R=10$  ohms and  $C=2$ F. The initial charge on the capacitor is nil. Find  $i(t)$ .

**Q8.** What do poles and zeros signify?

**Q9.** Determine the voltage across a  $2\text{-}\mu\text{F}$  capacitor if the current through it is  $i(t) = 6e^{-3000t}$  mA. Assume that the initial capacitor voltage is zero. Also draw the current wave form.


**Q10.** The current through a  $0.1\text{-H}$  inductor is  $i(t) = 10te^{-5t}$  A. Find the voltage across the inductor and the energy stored in it. [Hint: Energy stored in Inductor  $= \int P(t)dt = \int v(t).i(t)dt$  ]

**Q11.** (I) if  $f(t) = e^{j\omega t}$  then find  $\int_{-\infty}^{+\infty} e^{j\omega t} \delta(t-T)dt$ , and (II) if  $f(t) = \sin t$  then find  $\int_{-\infty}^{+\infty} \sin t \delta(t - \frac{\pi}{4})dt$

**Q12.** Define electrical circuit. Write the examples of active and passive elements.


**Q13.** Describe initial and final value condition of Inductor and capacitor.

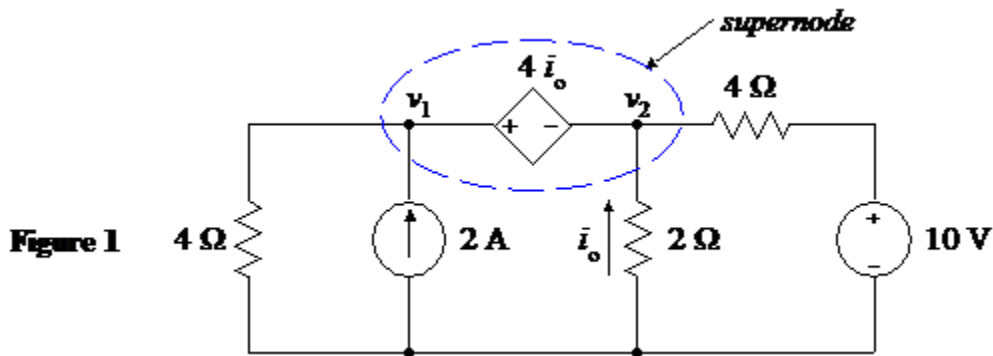**Q14.** In the circuit of Figure 1, find the current  $i_o$  using nodal analysis.




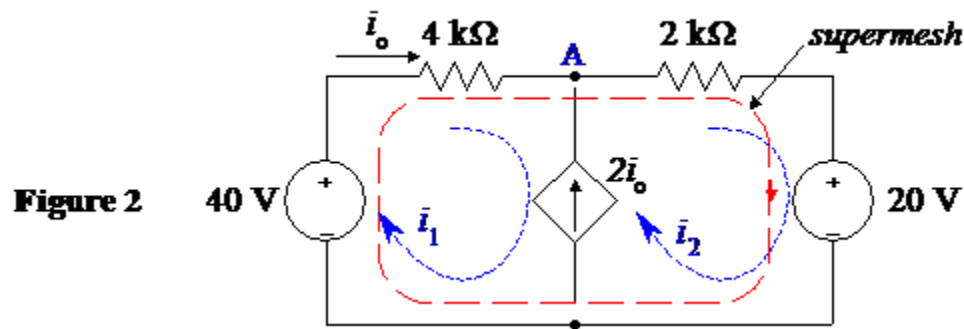**Q15.** In the circuit of Figure 2,

- Find the current  $i_o$  using mesh analysis.
- Find the power supplied by the dependent current source.



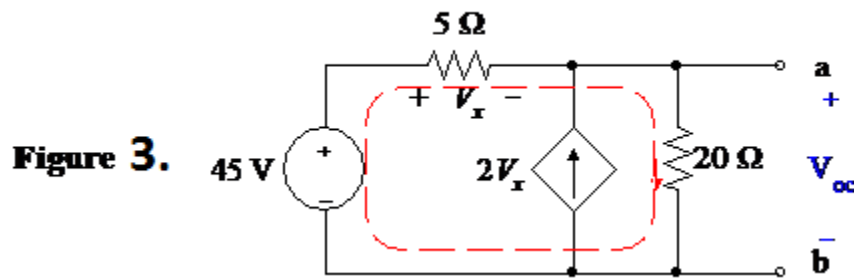
**Q16.** Obtain the Thevenin equivalent of the circuit in Figure 3 with respect to the terminals a-b.



**Q17.** State Norton's theorem and give steps to develop Norton's equivalent circuit from Thevenin's theorem.


**Q18.** State and explain Thevenin's theorem.

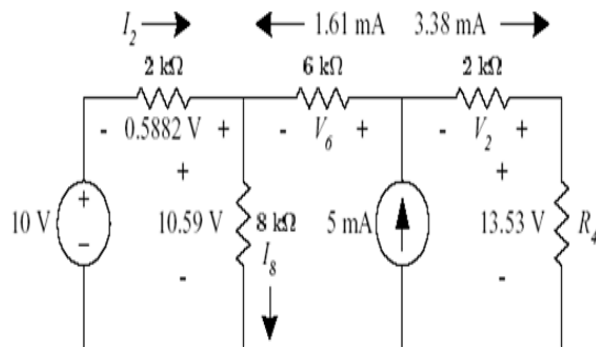**Q19.** For the given network find out the values of  $I_2$ ,  $V_6$ ,  $R_4$ ,  $V_2$  and  $I_8$ .




**Q20.** Describe the network elements and the transformed circuit.

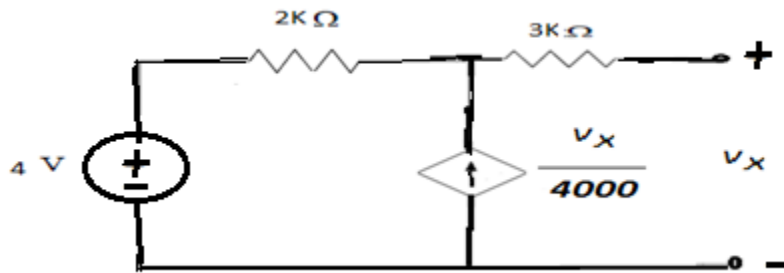**Q21.** Determine the Thevenin's equivalent of the circuit shown in Fig.



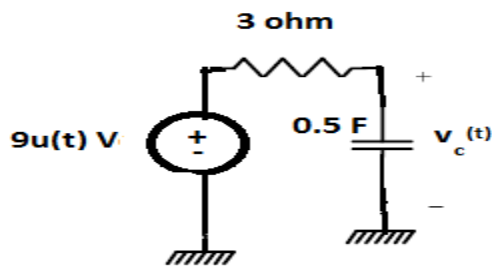**Q22.** Determine  $v_c(t)$  in the circuit of the figure. Given an initial voltage  $v_c(0^-) = -2V$ .




**Q23. (I).** What is significance of poles and zeros (OR) Classify the response based on location of poles and zeros? **(II).** Using graphical method, find the time domain response if the voltage wave

form is given by 
$$V(s) = \frac{4s}{(s+2)(s^2+2s+2)}$$

$$F(s) = \frac{s^3 + 4s^2 + 7s + 5}{s^2(s^2 + 2s + 5)}$$

**Q24.** Find the partial fraction expansion for  $F(s)$  and find Laplace inverse.

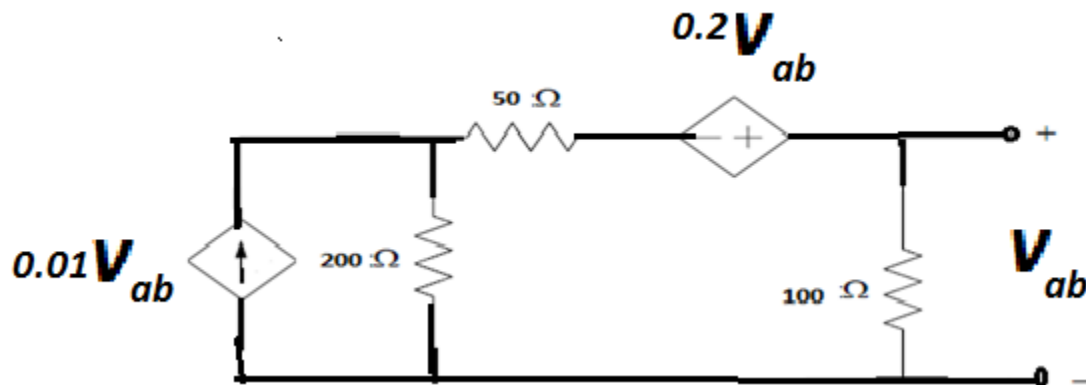**Q25.** Find the Thevenin's and Norton's equivalents of the circuits shown in Fig.




**Q26.** Define poles and zeros.

**Q27.** Derive the frequency shifting (complex translation) and time shifting (Real Translation) properties of Laplace transform.


**Q.28.** State the real differentiation properties of Laplace Transform

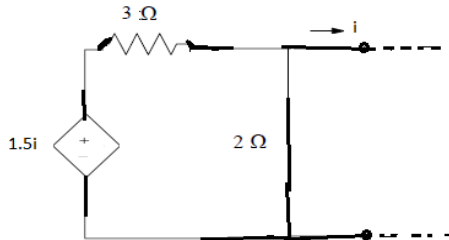**Q.29.** Determine the Thevenin equivalent of the circuit shown in Fig.




**Q30.** Write the statements of Thevenin's and Norton's theorem and also write the limitations.

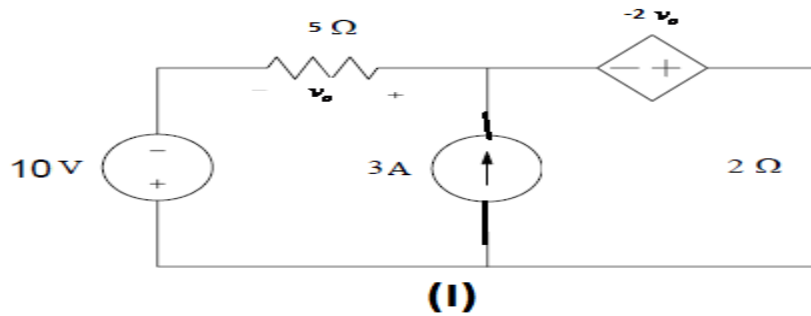**Q31.** Find the current in 2 Ohm resistance in the network shown in Fig. (I). (using Norton's theorem)



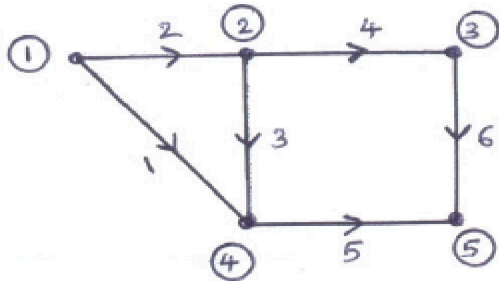**Q32.** Write the complete and reduced incidence matrix for given graph a network.



**Q33.** Define the basic elements of network topology

**Q34.** Draw the oriented graph of incidence matrix shown below

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$$


**Q35.** Draw the oriented graph of incidence matrix shown below

$$\mathbf{A}_a = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 & -1 & 0 \end{bmatrix}$$


**Q36.** Show that determinant of the incidence matrix of a closed loop is zero.

**Q37.** (a) For the given network shown. Draw the graph, select a tree with branches 9, 4, 7, 5, & 8 and write the tie-set matrix. The number inside the brackets indicates branch numbers.

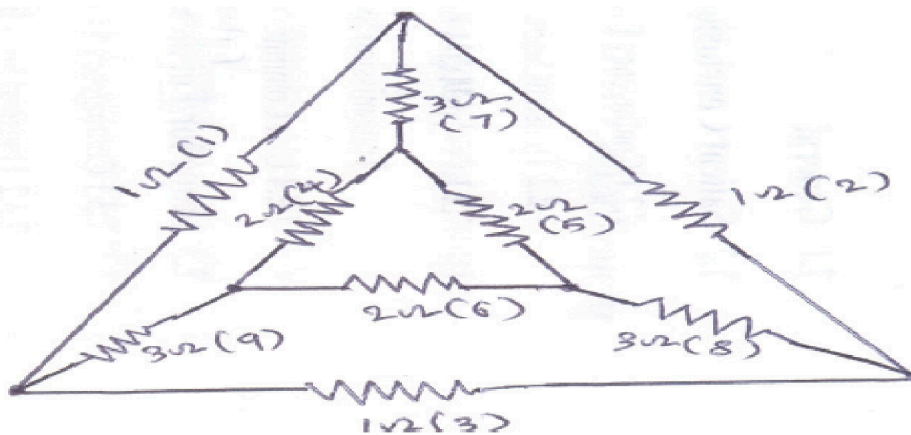(b) Using the above tie-set matrix formulate equilibrium equations.



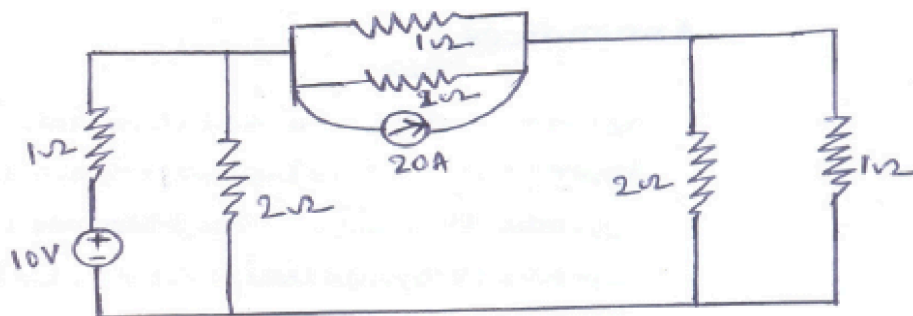**Q38.** Draw the graph for the network shown in figure below. Write the cut-set schedule & obtain equilibrium equations and hence calculate values of branch voltages and branch currents




**Q.39.** Write basic equations representing transmission parameters.

**Q.40.** Which parameters are preferred for cascade connected networks and why?


**Q.41.** In terms of ABCD parameters when is a two-port network symmetrical?

**Q.42.** Give the difference between the Transmission and Inverse Transmission Parameters for reciprocity and symmetry.

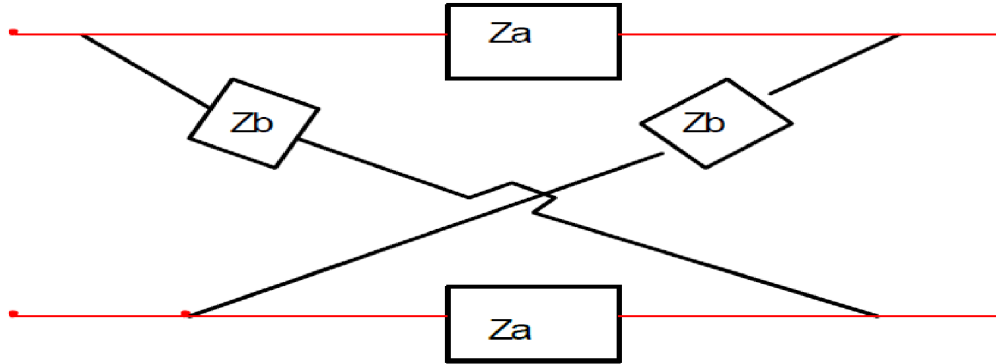**Q.43.** The open-circuit transfer impedance  $Z_{21}$  of the two-port network is



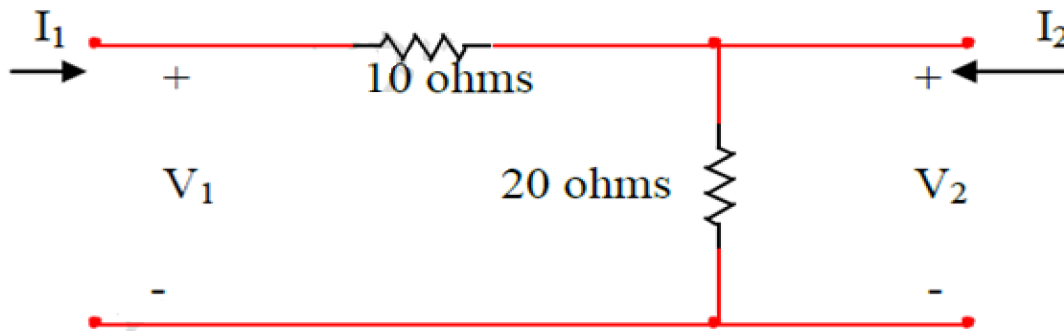**Q.44.** Find the h parameters of the circuit shown in figure.



**Q.45.** Give the internal block diagram of op-amp and mention the role of each stage. Give the pin-diagram of IC 741 and illustrate the concept of virtual ground.

**Q.46.** Summarize the frequency expressions for LPF, HPF and BPF.

**Q.47.** Enumerate the advantages & disadvantages of passive filters?

**Q.48.** What do you understand by filters? Give its classification.

**Q.49.** Discuss with necessary theory, the working of a second order high pass filter.

**Q.50.** State the advantages of active filters.

**Q.51.** Draw the first order low pass Butterworth filter and obtain its frequency response.

**Q.52.** Draw the first order high pass Butterworth filter and obtain its frequency response.

**Q.53.** An impedance function is given by  $Z(s) = \frac{K(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$ . If  $Z(-2) = \frac{-130}{16}$ , synthesize the impedance in **FOSTER-II and CAUER-I form**.

**Q.54.** An impedance function is given by  $Z(s) = \frac{K(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$ . If  $Z(-2) = \frac{-130}{16}$ , synthesize the impedance in **FOSTER-I and CAUER-II form**.

**Q.55.** Check whether the given functions are positive real function or not??

(I).  $F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$

(II).  $F(s) = \frac{s^3 + s^2 + 3s + 5}{s^2 + 6s + 8}$

(II).  $F(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$

**Q.56.** Define Hurwitz polynomial and Write its properties.

**Q.57.** Define positive realness (p.r.f.) and Write the properties of Positive real function (p.r.f.)

**Q.58.** Write the properties of L-C immittance functions.

**Q.59.** Write the properties of R-C impedance or R-L admittance functions.

**Q.60.** Write the properties of R-L impedance or R-C admittance functions.

**Q.61.** Check whether the given functions are positive real function or not??

(I).  $F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$

(II).  $F(s) = \frac{s^3 + s^2 + 3s + 5}{s^2 + 6s + 8}$

(II).  $F(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$

**Q.62.** Check whether the given functions are positive real function or not??

(I).  $Z(s) = \frac{as^2 + b}{s}$

(II).  $Z(s) = s + 3$

(III).  $Z(s) = s + j$

(IV).  $Z(s) = s^2 + 1$

(V).  $Z(s) = \frac{s^2 + 1}{s^3}$

(VI).  $Z(s) = s^{0.8}$

(VII).  $Z(s) = s - 4$

**Q.63.** What do we mean by Network synthesis? How is it different from network analysis?

**Q.64.** Write necessary and sufficient conditions for a function to be positive real (**OR**) Write *the necessary and sufficient* condition of positive real function (p.r.f.)

**Q.65.** Find the R-L network corresponding to the driving point impedance using Cauer form I

$$Z(S) = \frac{(s+4)(s+8)}{(s+2)(s+6)}$$

and Cauer form II.

**Q.66.** Find the R-C network corresponding to the driving point impedance using Cauer form I and Cauer form II.

$$Z(S) = \frac{(s+2)(s+6)}{(s+4)(s+8)}$$



**Q.67.** Find the R-L network corresponding to the driving point impedance using **FOSTER-I** and

$$Z(S) = \frac{(s+4)(s+8)}{(s+2)(s+6)}$$

**FOSTER-II** .

**Q.68.** Find the R-C network corresponding to the driving point impedance using **FOSTER-I** and

$$Z(S) = \frac{(s+4)(s+8)}{(s+2)(s+6)}$$

**FOSTER-II** .

**Q.69.** An impedance function is given by  $Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$  . Synthesize the impedance in **FOSTER-II and CAUER-I form**.

**Q.70.** An impedance function is given by  $Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$  . Synthesize the impedance in **FOSTER-I and CAUER-II form**.

**Q.71.** An admittance function is given by  $Y(s) = \frac{4s^2+6s}{s+1}$  . Realize the network using Cauer's first and second forms.

**Q.72.** Check whether the given polynomials are Hurwitz or not?

(I).  $F(s) = s^4 + s^3 + 5s^2 + 3s + 4$

(II).  $F(s) = s^5 + 7s^4 + 6s^3 + 9s^2 + 8s$

(III).  $F(s) = s^4 + s^3 + 2s^2 + 4s + 1$

**Q.73.** What is a transfer function? Write necessary conditions for transfer functions.

**Q.74.** What is driving point impedance? List four important properties of a driving point impedance function of an RC network.

**Q.75.** Write the properties of transfer function.

**Q.76.** Write the properties of open circuit parameters.

**Q.77.** Write the properties of short circuit parameters.

**Q.78.** What is a zero of transmission?

**Q.79. Find zeros of transmission for following cases:**

(I). L-C parallel combination in series arm

(II). L-C Series combination in shunt arm

(III). R-C parallel combination in series arm

**Q.80. Find zeros of transmission for following cases:**

(I). R-C Series combination in shunt arm

(II). R-L Series combination in parallel arm

(III). R-L parallel combination in series arm