 


①

UNIT-III

I/O and Memory Interface

* LCD Interfacing with 8051:



① LCD Pin description:

1. GND ——— Ground
2. VCC ——— +5V power supply
3. VEE ——— Contrast control power supply.
4. RS ——— 0 = select command register,
1 = select data register.
5. R/W ——— 0 = write; 1 = Read.
6. EN ——— Enable.
- 7-14 D0-D7 ——— 8-bit data bus.

② Commands or instruction codes of LCDs

01H — clear display screen.

→ LCD ^{instructions} allow selecting the display functions, cursor positioning, blinking, selecting character font, number of lines etc.

* → In LCD module, there are 3 control lines & 8-data lines.

→ The three control lines are enable, Register select & Read/write.

→ EN line is to instruct the LCD that μ c is sending the data.

→ 1 to 0 transitions on EN line will complete the display operation.

→ Register select line, when made low, means that the data is treated as a command or instruction to the LCD module.

→ when RS line is high, the data is a text data to be displayed on the LCD.

→ the read/write line RW, when made low, the information on data bus is written to LCD & when RW line is high, it means that the data is being read from the LCD.

→ There is only one read command, namely Get LCD status.


→ The EN line must go from high to low for LCD to execute the instruction.

→ Get LCD status command will make bit 7 of data bus high if it is busy in executing the command & will make it low if the LCD is not busy.

→ RS line must be low, while sending any of the commands.

→ For writing the text, set line EN & RS. EN line must go from high to low for the execution of LCD operation.

* Keyboard Interfacing with 8051:

 

Hex Key Pad.

0	4	8	C
1	5	9	D
2	6	A	E
3	7	B	F

→ Port '1' pins 4, 5, 6, 7 are pulled high through 10K resistors and are configured as inputs.

→ 1K resistors are connected in each of the rows to pins 3, 2, 1, 0 to avoid any short circuit between these pins in case two keys are pressed simultaneously.

→ Pins 3, 2, 1, 0 are configured as outputs & are used as the scan lines.

→ Pins 7, 6, 5, 4 are the return lines.

→ For example, if a scan line '3' is made low through a software instruction & if key '0' is pressed, it will drive the return line '4' low.

→ Thus, the keycode for the key '0' will be "0111 0111".

→ More important is that the scan lines are driven low under software control & the return lines are tested for '0'.

→ Thus, it requires only testing upper four bits for every scan condition given by software driven lower four bits.


→ For testing any key closure in spite of which key is pressed all the scan lines may be driven low & test for any return line becoming low.

→ Initially, the program register must be loaded with B"1111 0000".

* Key Encoding:

Scan lines 3:2:1:0	Return lines 4:6:5:4	Key
0 1 1 1 (3 low)	0 1 1 1 1 0 1 1 1 1 0 1 1 1 1 0	0 4 8 C
Next row		
1 0 1 1 (RB2 low)	0 1 1 1 1 0 1 1 1 1 0 1 1 1 1 0	1 5 9 D
Next row		
1 1 0 1 (1 low)	0 1 1 1 1 0 1 1 1 1 0 1 1 1 1 0	2 6 A E
Next row		
1 1 1 0 (0 low)	0 1 1 1 1 0 1 1 1 1 0 1 1 1 1 0	3 7 B F

* Interfacing External ROM with 8051:

 

- In 8051 ports 0 & 2 provides 16-bit address to access the external memory.
- P0 is multiplexed address/data bus.
- By using ALE pin
 - ALE = 0 → Data path (Access data from P0)
 - ALE = 1 → address path. (Access address from P0)
- o/p signal of 8051 must be connected to (PSEN) the OE pin of ROM containing the program code.
- EA pin (active low):
 - 1 → pgm is on on-chip ROM
 - 0 → pgm to be access from external pgm memory.
- PSEN:
 - 0 → can access external memory.
 - 1 → Cannot access external memory.


→ Latch is a 8-bit latch used for address & data multiplexing. (4)

* → External program memory access is possible in 8051 if the $\overline{EA}$ pin is low.

→ It is necessary to latch the lower address byte when the external program byte is read on the data bus.

→ The lower order address byte is latched, as the ALE pulse goes low.

* Interfacing of External RAM to 8051:

 


→ External data memory up to 64K can be accessed using a 16-bit data pointer (DPTR).

→ If the access is to data memory, then the signals $\overline{RD}$ & $\overline{WR}$ are generated by 8051.

→ During read cycle, $\overline{RD}$ signal goes low & a data byte from the external memory location is loaded onto the data bus.

→ $\overline{WR}$ signal is generated to write this byte into the external data memory.

* Interfacing ADC to 8051:

 

→ The designer has to write a subroutine for the control of ADC operation.

→ The analog to digital converter is treated (5) as an input device by the microcontroller, that sends an initialising signal to ADC to start the analog to digital data conversion process.

→ The soc signal is a pulse of a specific duration.

→ The process of ADC is a slow process, & the uc has to wait for digital data till the conversion is over.

→ After the conversion is over, the ADC sends EOC signal to inform the uc about it & the result is ready at the o/p buffer of ADC.


→ The time taken by the ADC from the active edge of soc pulse till the active edge of EOC signal is called the conversion delay of ADC.

→ These converters initially have a 3:8 analog multiplexer so that at a time 8 different analog inputs can be connected to the chips.

→ Out of these 8 inputs only one can be selected for conversion by using address lines A, B & C.

Analog i/p Selected	Address lines		
	C	B	A
I/P 0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

* Interfacing of DAC to 8051 *

 

→ The DAC convert binary numbers into their equivalent analog voltages.

→ An operational amplifier is used as a current to voltage converter at the o/p of DAC to convert current o/p to a proportional o/p voltage.

→ An external feedback resistor acts to control the gain.
