

Attaching Meters

Ammeter - _____

Symbol -

Voltmeter - _____

(_____ Difference)

(= Energy Change/Coulomb)

Voltmeters


are _____ 'in _____'

Symbol -


Ammeters

are _____ 'in _____'


Find Ammeter, Voltmeter

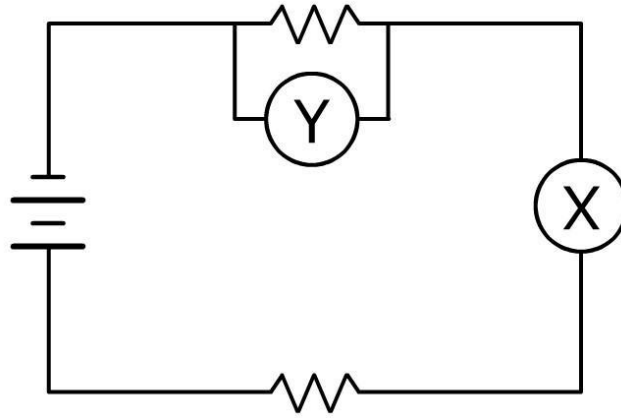



Ex) Which circuit is correct?

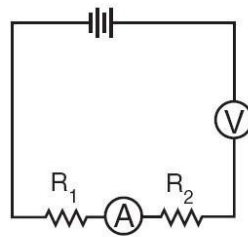

(1)

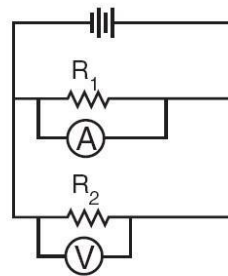

(3)

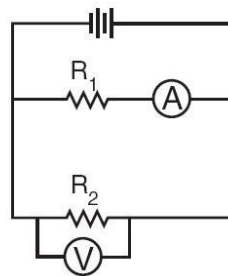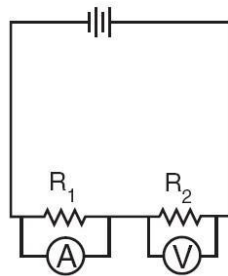

Identify the switch in the circuit and circuit diagram shown below.

