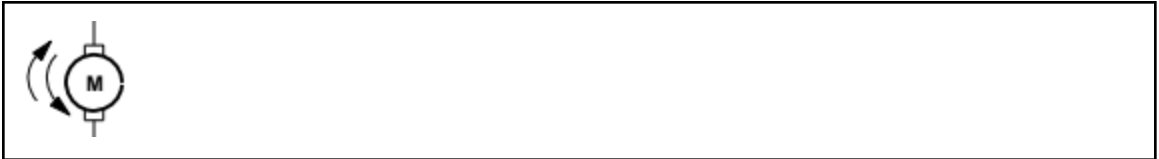


Lesson 21 DC Motors

1. What would happen if we connected a motor directly to your arduino?

2. How many motors can a L293D chip control?

3. What does this symbol represent in the schematic?



4. What output number would you use to rotate the motor at max speed?

5. **Challenge:** Can you change the code to switch the direction the motor spins? What did you change in the code and what happened?