

- 10.37** Analyze the network in Fig. P10.37 and determine whether a value of X_c can be found such that the output voltage is equal to twice the input voltage.

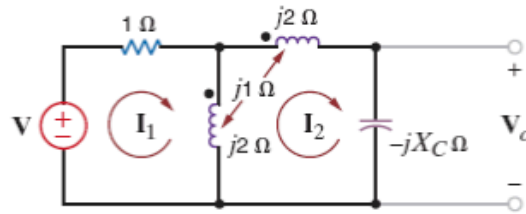


Figure P10.37

SOLUTION:

$$\text{KVL: } (1+j2)\bar{I}_1 - j2\bar{I}_2 + j1\bar{I}_2 = \bar{V}$$

$$(1+j2)\bar{I}_1 - j1\bar{I}_2 = \bar{V}$$

$$\text{KVL: } -j2\bar{I}_1 + j(4-X_c)\bar{I}_2 - j1\bar{I}_2 + j1(\bar{I}_1 - \bar{I}_2) = 0$$

$$-j1\bar{I}_1 + j1\bar{I}_2(2-X_c) = 0$$

$$\bar{I}_1 = (2-X_c)\bar{I}_2$$

$$\bar{V} = [(1+j2)(2-X_c) - j1]\bar{I}_2$$

$$\bar{V} = [2-X_c + j(3-2X_c)]\bar{I}_2$$

$$\bar{V}_o = -jX_c\bar{I}_2$$

$$\frac{\bar{V}_o}{\bar{V}} = \frac{-jX_c}{2-X_c + j(3-2X_c)} = 2+j0$$

$$2 - X_C = 0$$

$$X_C = 2 \Omega$$

$$\frac{V_o}{V} = \frac{-j2}{0 + j(3 - 4)}$$

$$\frac{V_o}{V} = 2 + j0$$

$$X_C = 2 \Omega$$

11.71 Find C in the network in Fig. P11.71 such that the total load has a power factor of 0.9 lagging.

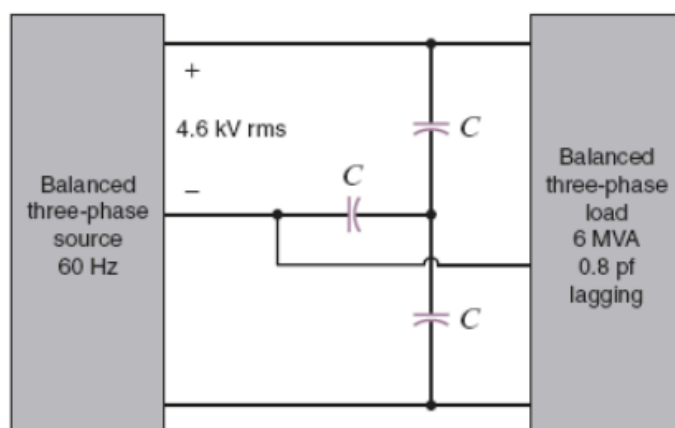


Figure P11.71

SOLUTION:

$$|\bar{V}_{ab}| = 4.6 \text{ kV rms}$$

$$\bar{S}_L = 6 \text{ MVA} \angle \cos^{-1}(0.8)$$

$$\bar{S}_L = 6 \angle 36.87^\circ \text{ MVA}$$

$$P_{1-\phi} = \frac{6 \text{ M}}{3} (0.8) = 1.6 \text{ MW}$$

$$\theta_s = \cos^{-1}(0.8) = 36.87^\circ$$

$$Q_{1-\phi} = 1.2 \text{ MVar}$$

$$P_{1-\phi} = 1.6 \text{ MW}$$

$$Q_{\text{new}} = \frac{P_{1-\phi}}{\text{Pf}_{\text{new}}} \sin [\cos^{-1}(\text{Pf}_{\text{new}})]$$

$$Q_{\text{new}} = \frac{1.6 \text{ M}}{0.9} \sin [\cos^{-1}(0.9)]$$

$$Q_{\text{new}} = 774.9 \text{ kVar}$$

$$Q_c = Q_{\text{new}} - Q_{\text{old}}$$

$$Q_c = 774.9 \text{ k} - 1.2 \text{ M}$$

$$Q_c = -425.1 \text{ kVar}$$

$$Q_c = -|\bar{V}_{ab}|^2 \omega C$$

$$C = \frac{-425.1 \text{ k}}{-(4.6 \text{ k})^2 (377)}$$

$$C = 53.29 \mu\text{F}$$

- 12.49** Given the network in Fig. P12.49, sketch the magnitude characteristic of the transfer function

$$G_v(j\omega) = \frac{V_0}{V_1}(j\omega)$$

Identify the type of filter.


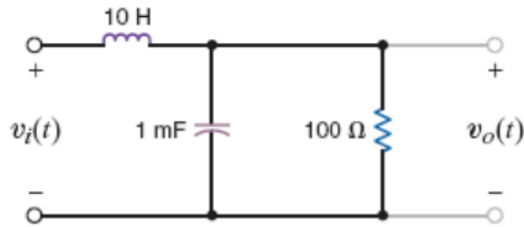


Figure P12.49

SOLUTION:

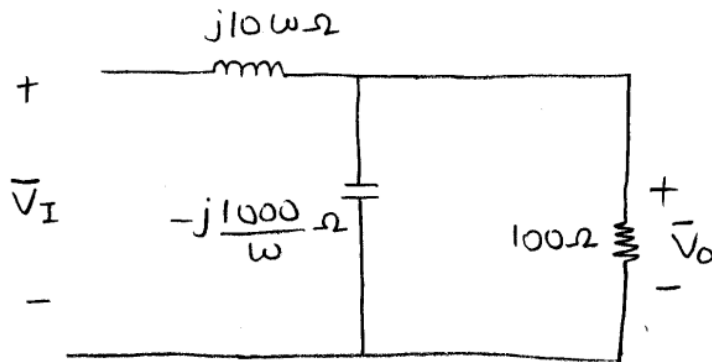

$$\bar{Z}_1 = -j \frac{1000}{\omega} \parallel 100$$

$$\bar{Z}_1 = \frac{-j \frac{1000}{\omega} (100)}{100 - j \frac{1000}{\omega}}$$

$$\bar{Z}_1 = \frac{1000}{1 + j\omega}$$

$$\bar{V}_0 = \left(\frac{\bar{Z}_1}{\bar{Z}_1 + j10\omega} \right) \bar{V}_I$$

$$\frac{\bar{V}_O}{\bar{V}_S} = \left(\frac{\frac{1000}{1+j\omega}}{\frac{1000}{1+j\omega} + j10\omega} \right)$$

$$\frac{\bar{V}_O}{\bar{V}_I} = \frac{1000}{1000 + (j10\omega)(1+j\omega)}$$

$$\frac{\bar{V}_O}{\bar{V}_I} = \frac{1000}{1000 - 10\omega^2 + j10\omega}$$

$$\frac{\bar{V}_O}{\bar{V}_I} = \frac{100}{100 - \omega^2 + j\omega}$$

$$\frac{\bar{V}_O}{\bar{V}_I} = \frac{100}{(j\omega)^2 + j\omega + 100}$$

- 12.45** Determine the value of C in the network shown in Fig. P12.45 for the circuit to be in resonance.


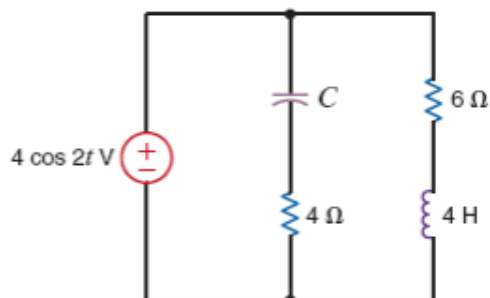


Figure P12.45

SOLUTION:

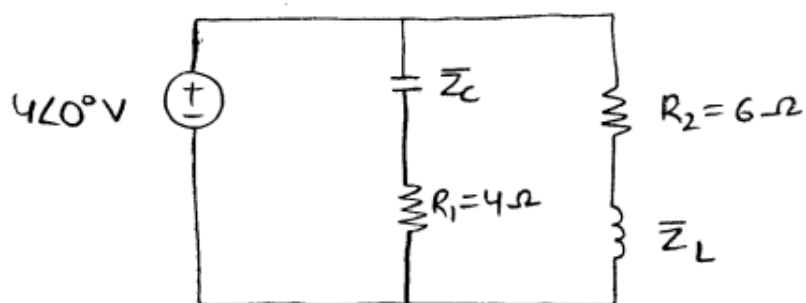


$$\omega = 2 \text{ rad/s}$$

$$\bar{Z}_L = j\omega L = j(2)(4)$$

$$\bar{Z}_L = j8 \Omega$$

$$\bar{Z}_C = \frac{1}{j\omega C} = \frac{1}{j(2)(C)}$$

$$\bar{Z}_C = \frac{-j}{2C} \Omega$$

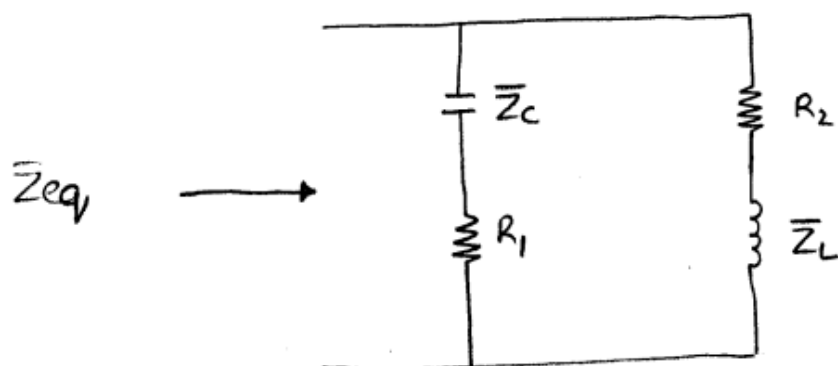

$$\bar{Z}_{eq} = (R_2 + \bar{Z}_L) \parallel (R_1 + \bar{Z}_C)$$

$$\bar{Z}_{eq} = \frac{(R_2 + \bar{Z}_L)(R_1 + \bar{Z}_C)}{R_2 + \bar{Z}_L + R_1 + \bar{Z}_C}$$

$$\bar{Z}_{eq} = \frac{R_1 R_2 + \frac{L}{C} + j(\omega L R_1 - \frac{R_2}{\omega C})}{R_1 + R_2 + j(\omega L - \frac{1}{\omega C})}$$

$\bar{Z}_{eq}$ is real at resonance.

$\therefore$ the phase angle of the numerator and the denominator are equal.

$$\frac{\omega L R_1 - \frac{R_2}{\omega C}}{R_1 R_2 + \frac{L}{C}} = \frac{\omega L - \frac{1}{\omega C}}{R_1 + R_2}$$

$$\frac{2(4)(4) - \frac{6}{2C}}{4(6) + \frac{4}{C}} = \frac{2(4) - \frac{1}{2C}}{4 + 6}$$

$$\frac{32 - \frac{3}{C}}{24 + \frac{4}{C}} = \frac{8 - \frac{1}{2C}}{10}$$

$$\frac{\frac{32C-3}{C}}{\frac{24C+4}{C}} = \frac{\frac{16C-1}{2C}}{\frac{10}{10}}$$

$$\frac{32C-3}{24C+4} = \frac{16C-1}{20C}$$

$$\frac{32C-3}{6C+1} = \frac{16C-1}{5C}$$

$$(32C-3)(5C) = (6C+1)(16C-1)$$

$$160C^2 - 15C = 96C^2 + 16C - 1 - 6C$$

$$64C^2 - 25C + 1 = 0$$

$$C = \frac{25 \pm \sqrt{(-25)^2 - 4(64)(1)}}{2(64)}$$

$$C = \frac{25 \pm 19.21}{128}$$

$$C = 0.19531 \pm 0.15008$$

$$C = \begin{cases} 345 \text{ mF} \\ 45 \text{ mF} \end{cases}$$