

Roll No.....

Total No. of Printed Pages: 1

Total No. of Questions: [09]

B. Tech (EE) (Semester – 3rd)
ANALOG ELECTRONIC CIRCUITS
Subject Code: BELES1302
Paper ID: [18111511]

Time: 03 Hours

Maximum Marks: 60

Instruction for candidates:

1. Section A is compulsory. It consists of 10 parts of two marks each.
2. Section B consist of 5 questions of 5 marks each. The student has to attempt any 4 questions out of it.
3. Section C consist of 3 questions of 10 marks each. The student has to attempt any 2 questions.

Section – A

(2 marks each)

Q1 Attempt the following:

- a. Give the effect of feedback on Gain & Bandwidth on the negative amplifier?
- b. Define the terms: transconductance, Voltage Gain and Power gain of an amplifier.
- c. What is Harmonic distortion in Power amplifiers?
- d. What is Barkhausen criterion in Oscillators?
- e. What are multistage amplifiers?
- f. What is an Oscillator. Classify Oscillators.
- g. What is a MOS Capacitor?
- h. What are the types of Power Amplifiers?
- i. Define Multivibrator. Which are the commonly used multivibrators?
- j. Give difference between ADC and DAC using an example for each?

Section – B

(5 marks each)

- Q2 Discuss the RC coupled multistage amplifier briefly using suitable circuit diagrams.
- Q3 Explain the working principle of Hartley Oscillator? Give its advantages & disadvantages.
- Q4 Explain the working of a Differential Amplifier using suitable circuit diagram.
- Q5 Describe the working operation of a Bipolar Junction Transistor briefly? Draw its V-I Characteristics.
- Q6 Discuss a Triangular wave generator using a suitable diagram.

Section – C

(10 marks each)

- Q7 Discuss various Amplifier Models using suitable equivalent circuits and analyze them?
- Q8 Explain the working principle and operation of a Field Effect Transistor? Give its advantages, disadvantages and applications?
- Q9 Write short note on: Op-Amps for Active filters.