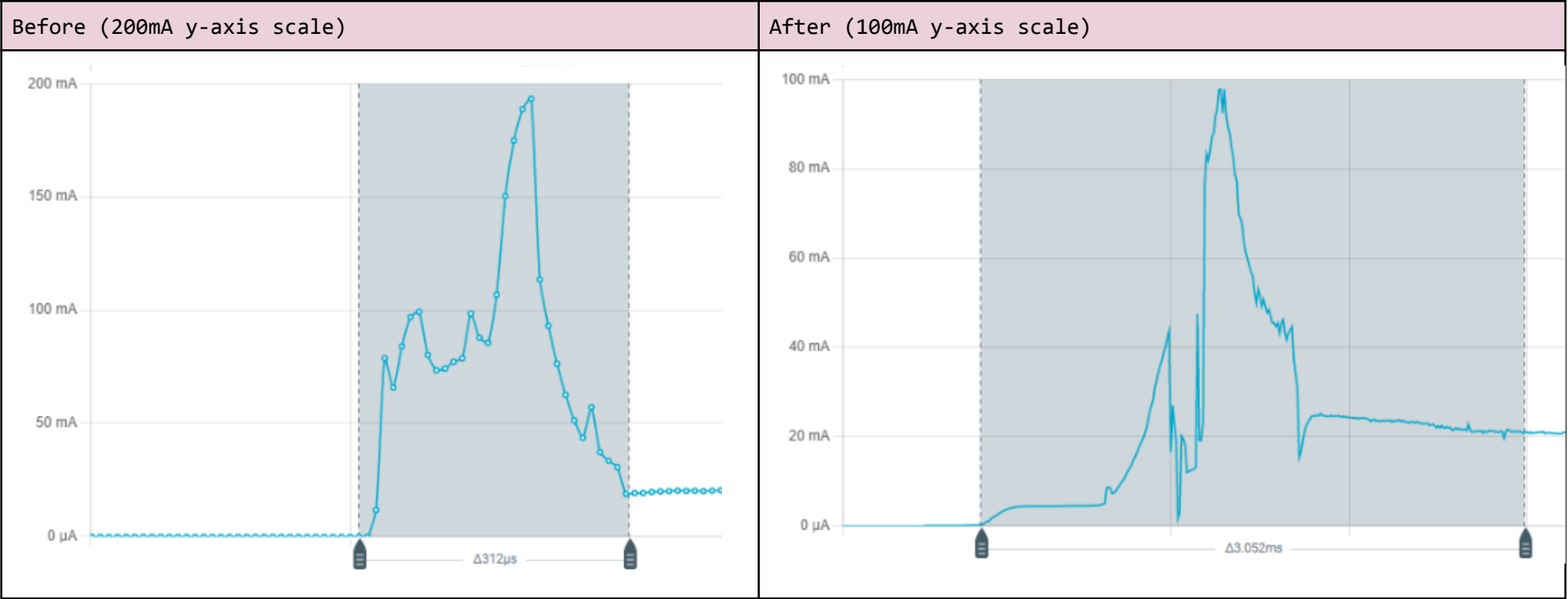


# Results

You can substantially limit the inrush current of a sub-circuit you turn on with a microcontroller.

Using the approach below, a small circuit change was able to reduce the inrush current of the ATGM336H GPS module by 50%.

The inrush duration went from 300us to 3ms.



It is possible to simulate these circuits as well, see Simulation section.

# Summary

## High-Side vs Low-Side Switching Concept

You want to electronically turn a circuit on or off (eg with a microcontroller).

You can interrupt the power to the circuit by cutting off its power supply (high side) or cutting off access to ground (low side).

## High-Side Switching Use Cases

Use when:

- Switching ICs or smart circuits you will communicate with
- Load voltage same as your control voltage

([link](#)) Engineering hobby site elaboration

Generally, you want to keep the ground connected in a circuit and switch the power. One reason is that even when the transistor is fully turned on, there is still a small voltage drop across it. That voltage drop means the ground is not 0 volts for that device.

It does not matter which you switch for something simple like an LED.


However, an active device like a Microcontroller needs its ground to be ground!

So when you have a load that requires ground, you NEED to use a high-side switch.
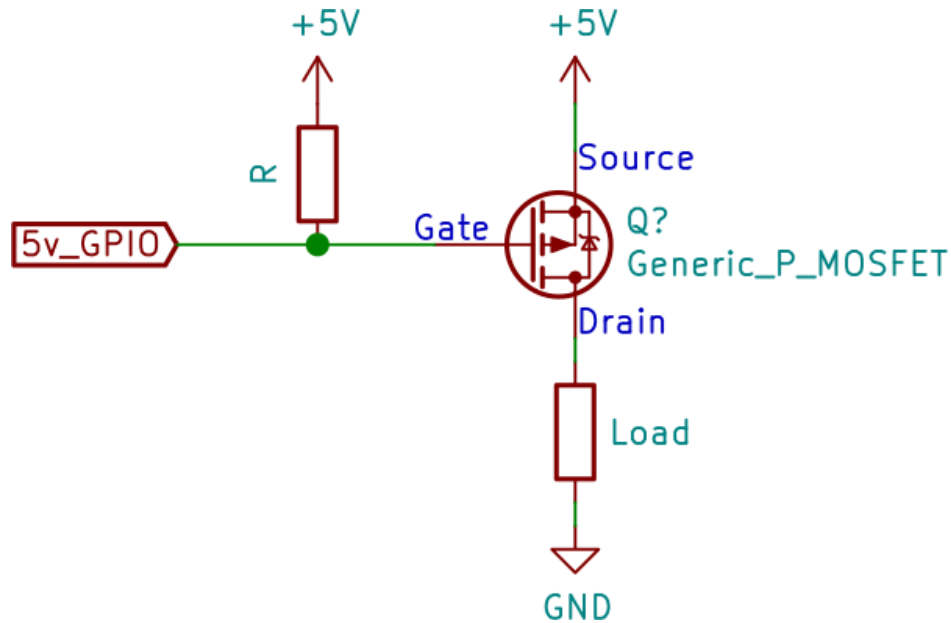
# High-Side Switching Circuit

P-Channel Enhancement MOSFET  
(not N-Channel, nor Depletion)

It is a good idea to have a pull-up resistor to ensure the gate is in a constant state regardless of whether your microcontroller is active or not.



## Inrush Current Problem

When you suddenly activate the load circuit, the capacitance of that circuit will momentarily consume large quantities of current as the capacitors charge up.

This can be bad, as it may exceed the capacity of the power supply to sustain, and cause the power rail voltage to sag, potentially impacting other components negatively.

# Inrush Current Mitigation Circuit

You can not change the capacitance of the load circuit.  
You can change the rate at which you feed it current.

The Gate of the MOSFET does not have to be all the way ON or OFF. You can slowly change the voltage of the gate from OFF to ON over time.


During the time the MOSFET is between OFF and ON, it is changing the rate it allows current to pass through, like a variable resistor.

The circuit below, using a technique described by ON Semiconductor ([link](#)), models this.

In short, the Gate voltage will be influenced by 3 components:

- Pull-up resistor
- Microcontroller series resistor
- Capacitor between Gate and Drain

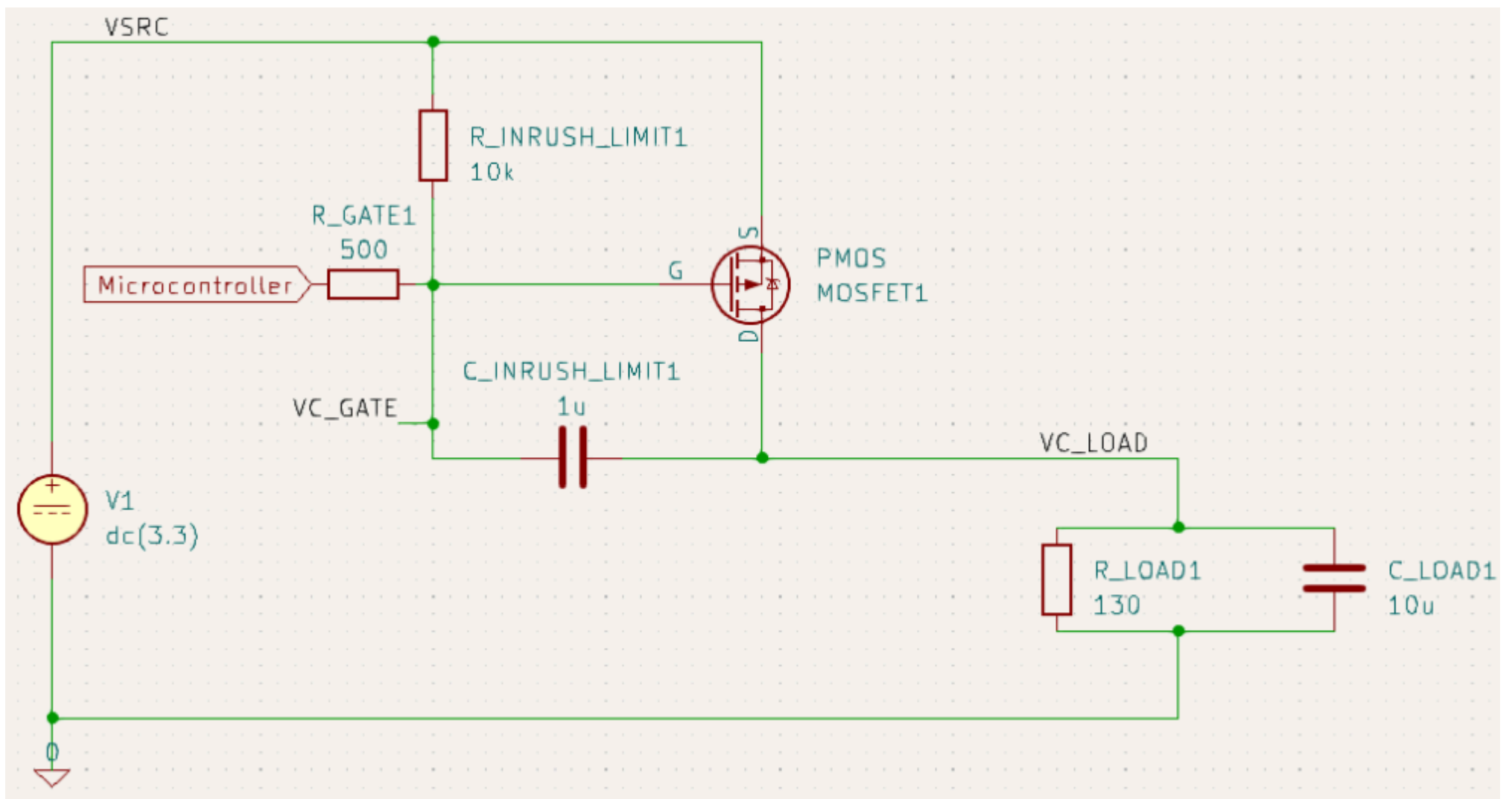The load is modeled as both resistive and capacitive.



# Explanation

(don't forget this is a P-Type MOSFET, so HIGH is OFF, LOW is ON)

In the state where the microcontroller is HIGH (MOSFET is OFF):

- Voltage divider formed between pullup resistor and microcontroller inline resistor
  - This equals the input voltage, both the pullup and microcontroller are applying same voltage
- The capacitor charges to this input voltage

When the microcontroller changes to LOW (MOSFET goes to HIGH):

- The microcontroller voltage goes to 0
  - Now there is a voltage divider in effect between pullup and gate resistor
  - The capacitor still retains some charge (voltage) from prior state
    - So it slowly bleeds off its charge through the microcontroller resistor

In short, when the microcontroller goes from HIGH to LOW, the capacitor doesn't, it takes a little while. That little while slowly decreases the resistance of the MOSFET, slowly turning the MOSFET all the way on.

# Implementation with ATGM336H GPS

All measurements were done on a breadboard, 3.3v supply.

AGTM nRESET, VCC, VBAT, ON/OFF tied together, all GND tied together.

## ATGM Inrush Caps - Turn On





PPK2

CD18951A6ACD



DATA LOGGER

REAL-TIME

ABOUT



MODE

Source meter

Ampere meter

Set supply voltage to 3300 mV


Enable power output



SAMPLING PARAMETERS

100,000 samples per second

Sample for 600 seconds

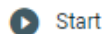Estimated RAM required 240.0 MB  
10 us period

Start

DISPLAY OPTIONS

Timestamps



Digital channels



0

1

2

3

4

5

6

7

SHOW SIDE PANEL




CLEAR LOG

OPEN LOG FILE

AUTOSCROLL LOG



SHOW LOG

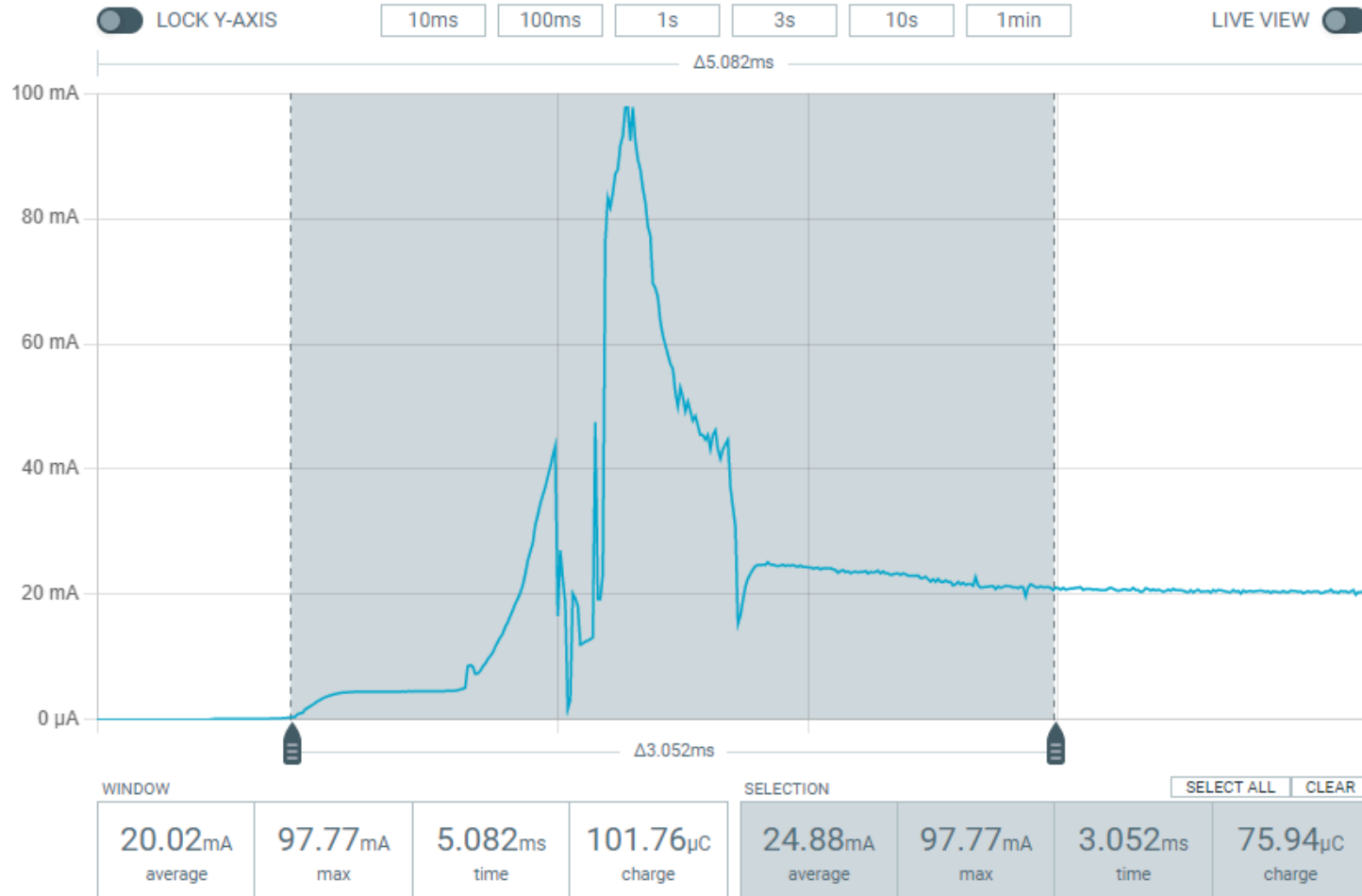




# ATGM Inrush Caps - Turn Off



Takes seconds for caps to discharge

File Edit Capture Measure View Help

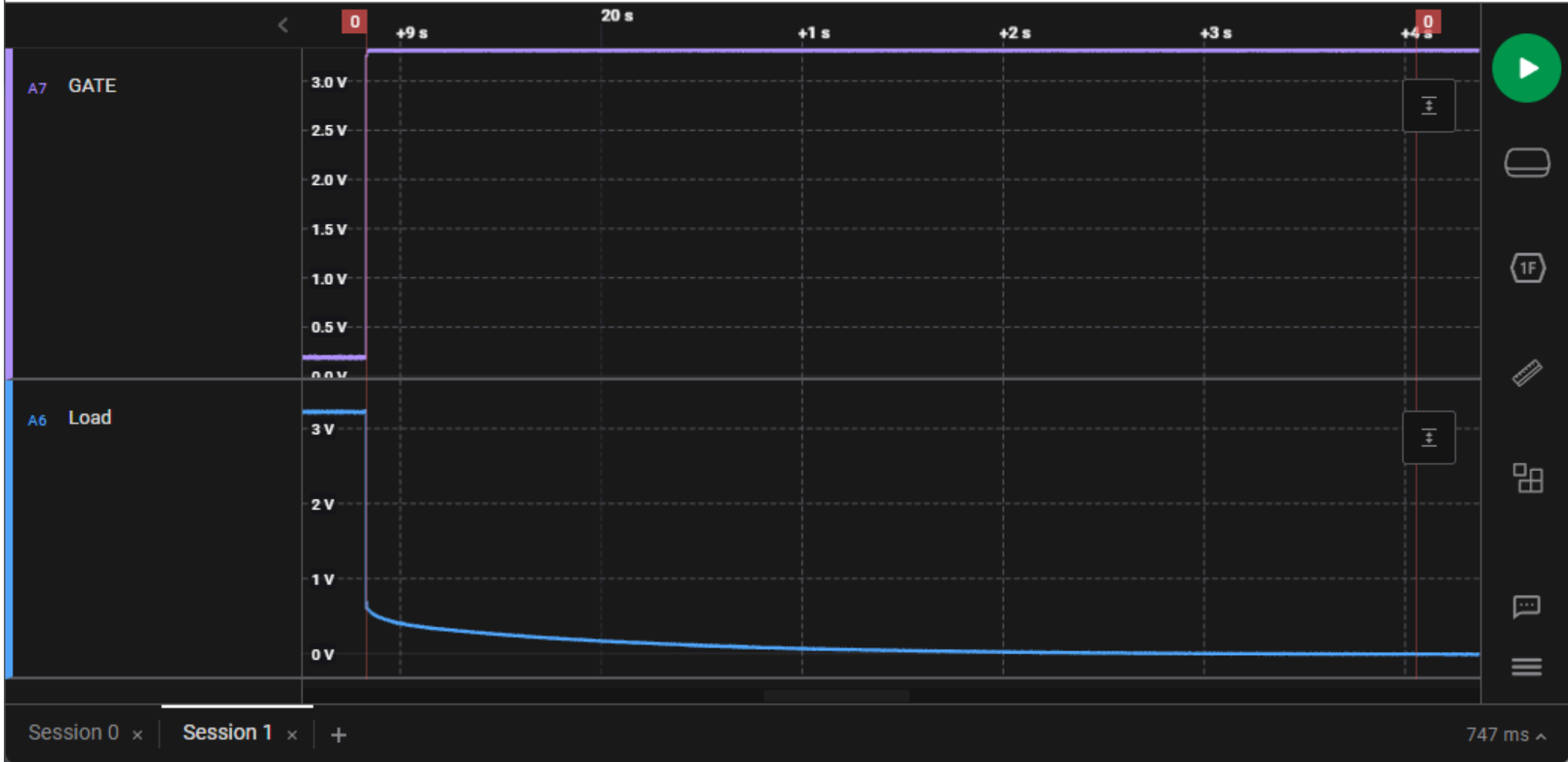

Session 0 × Session 1 × +

747 ms ^



PPK2

CD18951A6ACD



DATA LOGGER

REAL-TIME

ABOUT



MODE

Source meter

Ampere meter

Set supply voltage to 3300 mV


Enable power output



SAMPLING PARAMETERS

100,000 samples per second

Sample for 600 seconds

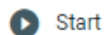Estimated RAM required 240.0 MB  
10 us period

Start

DISPLAY OPTIONS

Timestamps



Digital channels



0

1

2

3

4

5

6

7

SHOW SIDE PANEL




CLEAR LOG

OPEN LOG FILE

AUTOSCROLL LOG



SHOW LOG

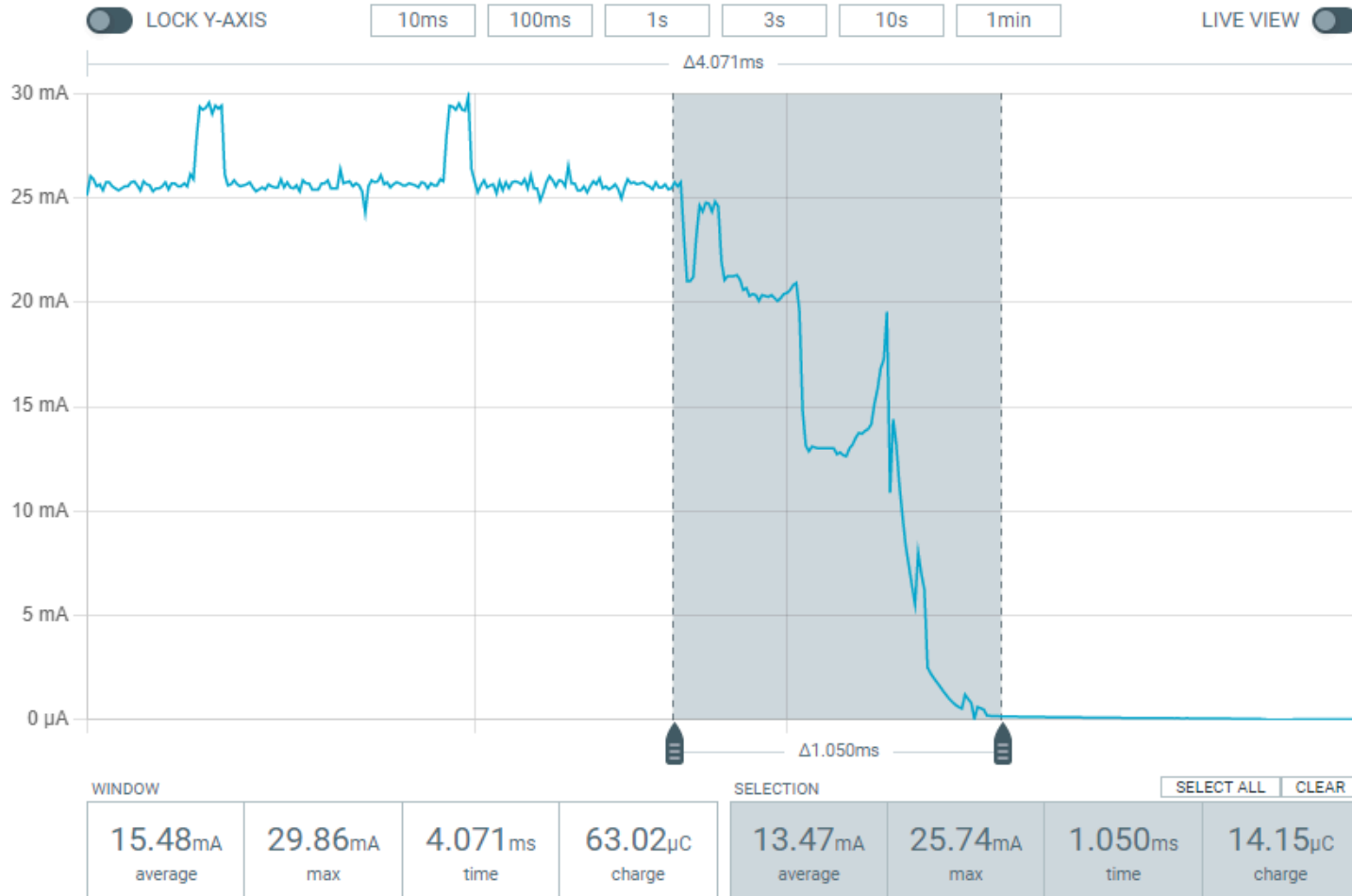

# ATGM No Inrush Caps - Turn On





PPK2

CD18951A6ACD



DATA LOGGER

REAL-TIME

ABOUT



MODE

Source meter

Ampere meter

Set supply voltage to 3300 mV


Enable power output



SAMPLING PARAMETERS

100,000 samples per second

Sample for 600 seconds

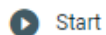Estimated RAM required 240.0 MB  
10 us period

Start

DISPLAY OPTIONS

Timestamps



Digital channels



0

1

2

3

4

5

6

7

SHOW SIDE PANEL




CLEAR LOG

OPEN LOG FILE


AUTOSCROLL LOG




SHOW LOG

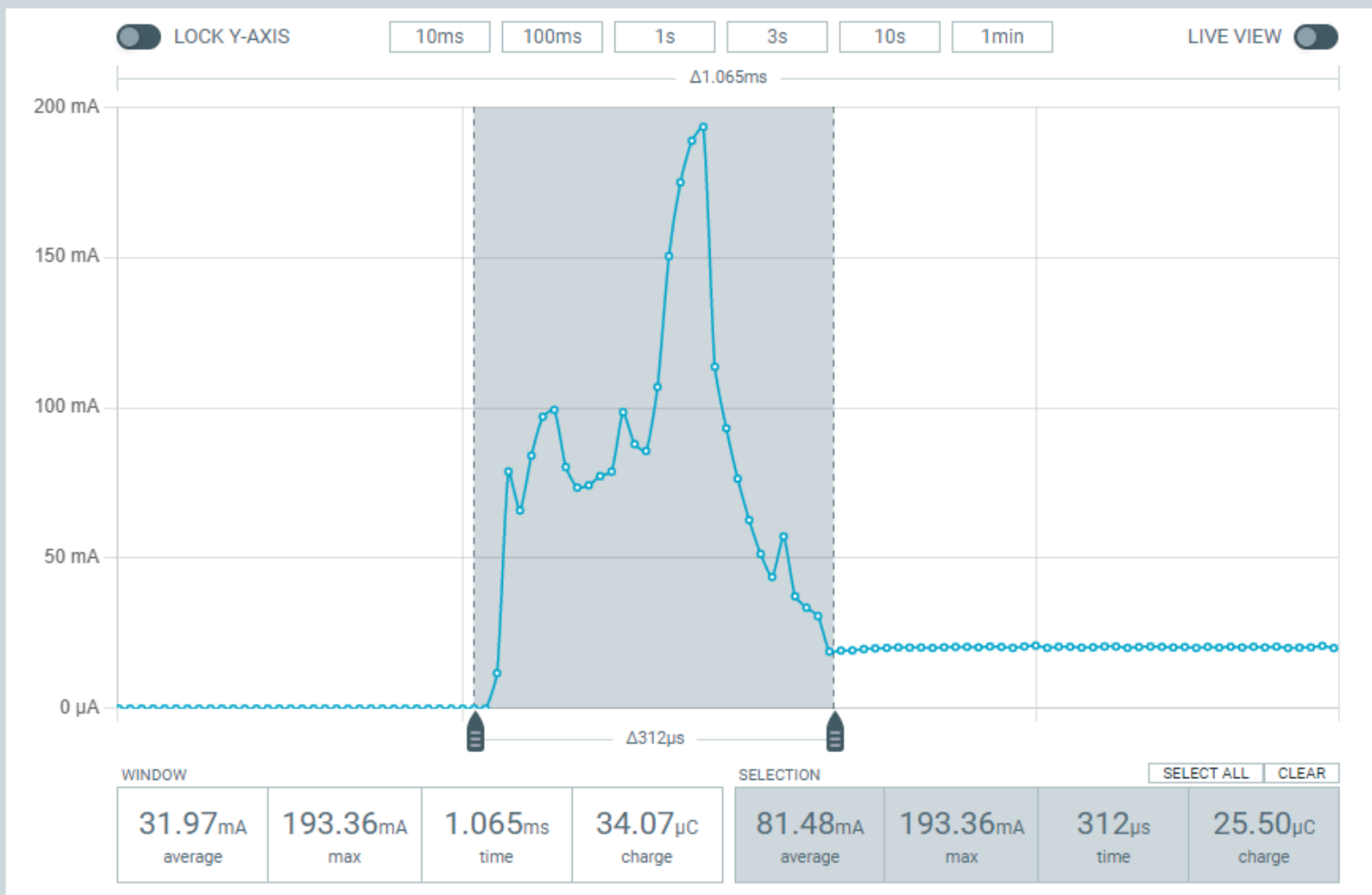

# ATGM No Inrush Caps - Turn Off

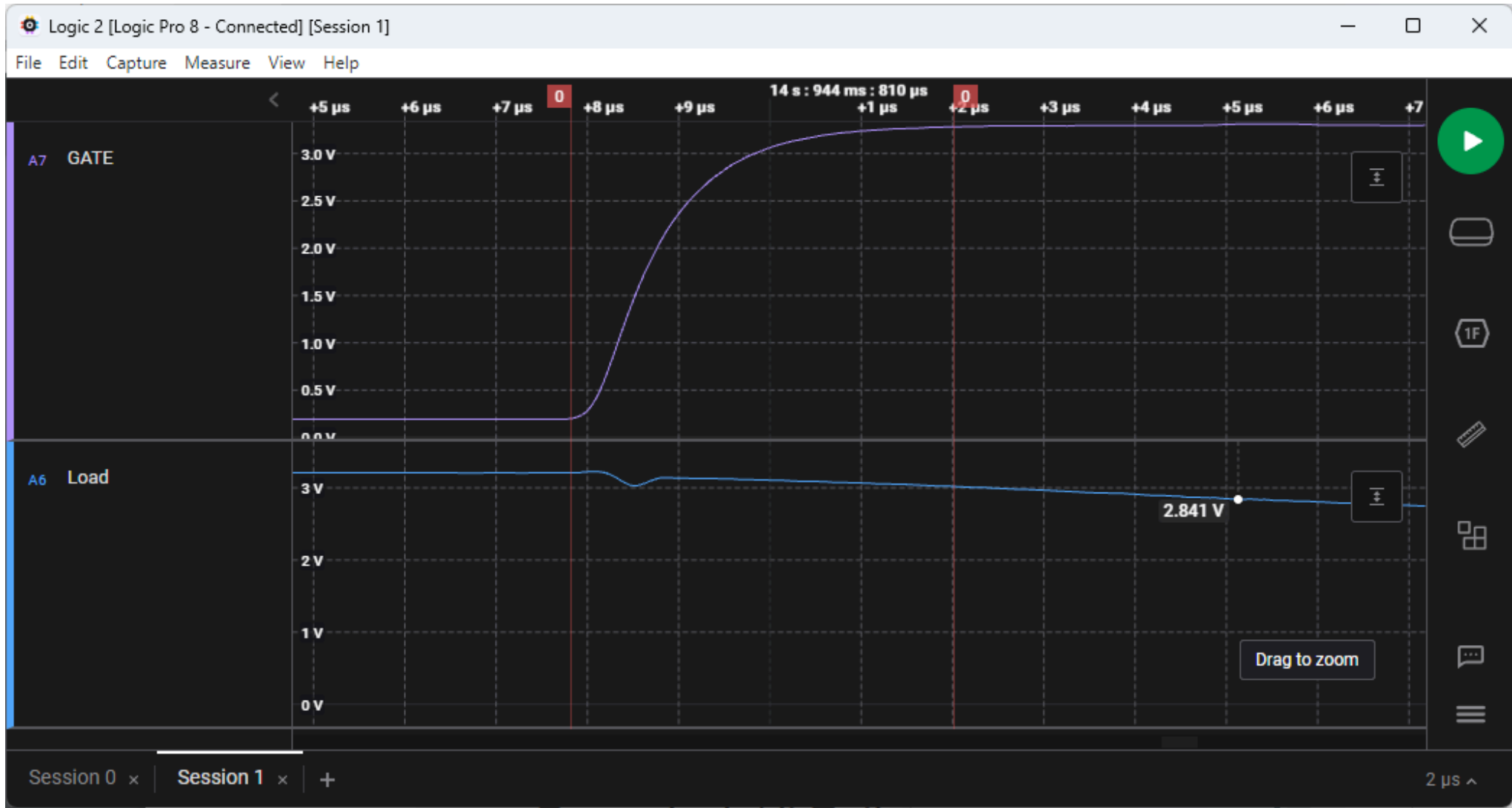

Takes seconds for GPS caps to discharge

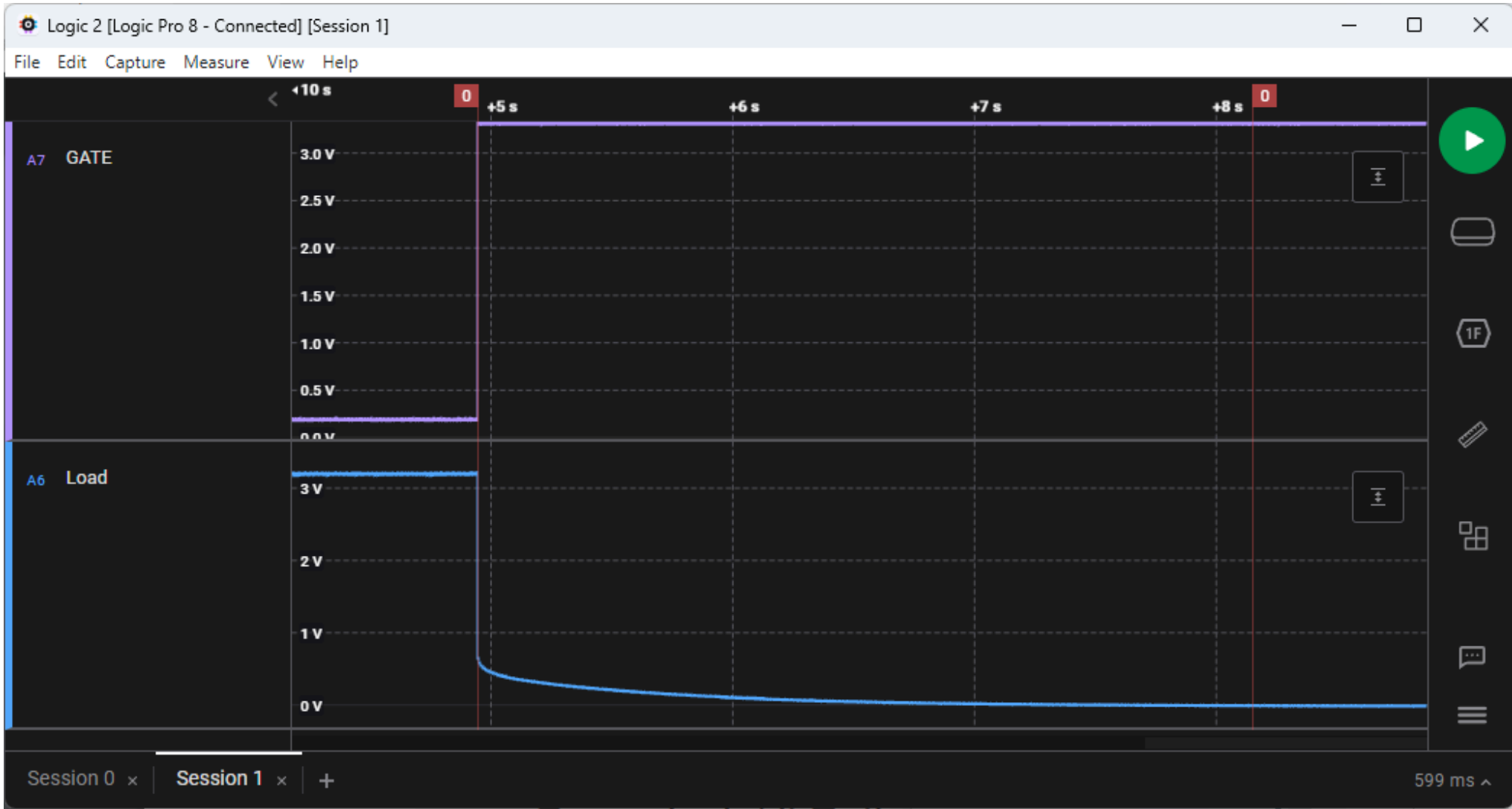



PPK2

CD18951A6ACD



DATA LOGGER

REAL-TIME

ABOUT



MODE

Source meter

Ampere meter

Set supply voltage to 3300 mV


Enable power output



SAMPLING PARAMETERS

100,000 samples per second

Sample for 600 seconds

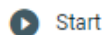Estimated RAM required 240.0 MB  
10 us period

Start

DISPLAY OPTIONS

Timestamps



Digital channels



0

1

2

3

4

5

6

7

SHOW SIDE PANEL




CLEAR LOG

OPEN LOG FILE

AUTOSCROLL LOG



SHOW LOG

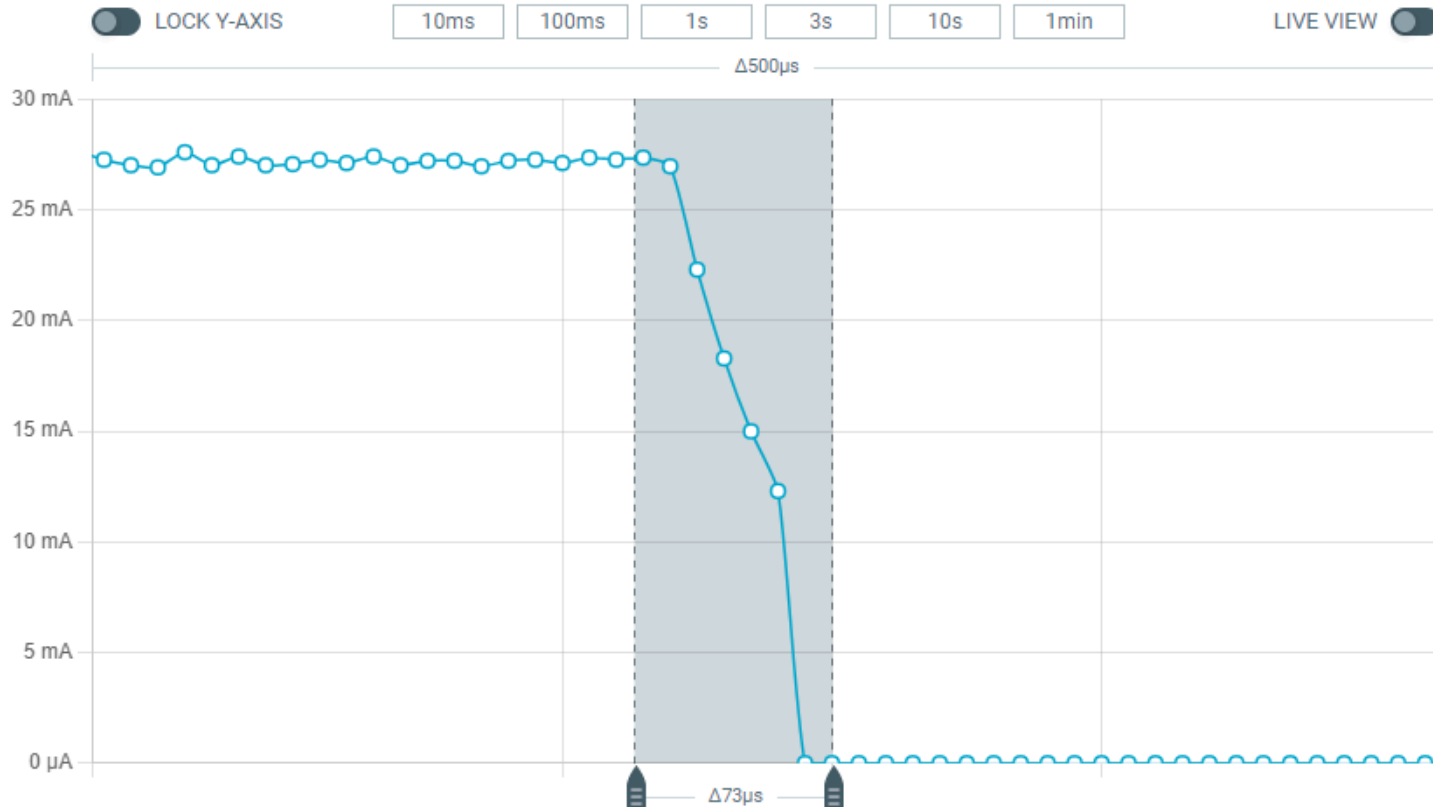

WINDOW

13.32mA  
average27.60mA  
max500 $\mu s$   
time6.66 $\mu C$   
charge

SELECTION

15.27mA  
average27.35mA  
max73 $\mu s$   
time1.12 $\mu C$   
charge

SELECT ALL

CLEAR



# Simulation


([link](#)) YouTube video on how to use KiCad spice simulations

I originally simulated this circuit in KiCad.

I subsequently tested it with a breadboard and misc components.

The results were similar, but not exact, neither were the components though.

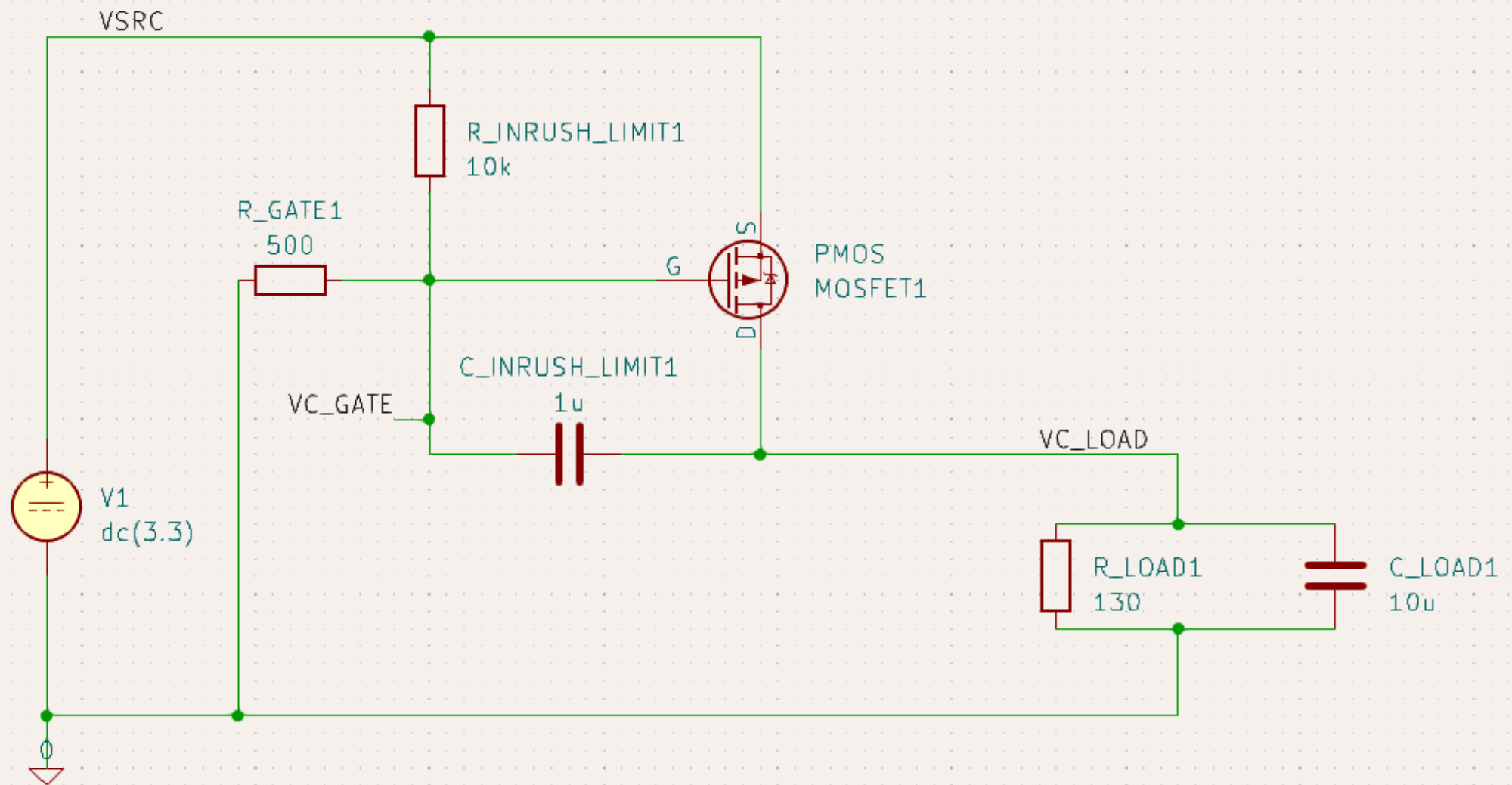Here I have adapted the circuit above to tie the Gate resistor to ground, simulating the microcontroller turning the MOSFET on. The initial conditions are simulated to be as though the MOSFET were off for a long time.



```
.tran 0.000001 .003000
```

```
.ic V(/VC_LOAD)=0
```

```
.ic V(/VC_GATE)=3.3
```

Useful to be able to use the simulator to vary the values of the various components interactively (sliders) to graph new without changing the schematic. Lets you play with values quickly to see the result.

Tune

C\_LOAD1

100u

10u

0

Save

C\_INRUSH\_LIMIT1

10u

1u

0

Save

R\_GATE1

4k

500

0

Save

R\_INRUSH\_LIMIT1

20k

10k

0

Save

R\_LOAD1

160

130.000

40

Save

Signals

I(MOSFET1:s)

V(/VC\_GATE)

V(/VC\_LOAD)

