

Class:	CPE300L			Semester:	Fall 2021
Points		Document author:	Jerrod Batu		
		Author's email:	batuj1@unlv.nevada.edu		
		Document topic:	Postlab 4		
Instructor's comments:					

1. Introduction / Theory of Operation

Throughout this lab, I will continue Verilog review by learning more about latches and flip-flops, synchronous and asynchronous operations, and asynchronous system design. Some of these latches and flip-flops would include a gated D latch with asynchronous Set' and Clear', JK flip-flop with synchronous clear, D flip flop with asynchronous low clear, etc.

1. A **D flip-flop** is a digital electronic circuit that delays output state change until its next rising edge where an input would be called upon. Specifically, the D flip-flop behaves similar to memory as the output will stay constant until it is altered from the D input at the rising clock edge. They are, in fact, utilized as building block shift registers that can store clock cycles. A **JK flip-flop**, in general, is a gated S-R latch with the AND and NOR gates replaced as NAND gates. JK flip-flops are the most used flip-flop designs because they are very universal. The two inputs "J" and "K" are named after the inventor Jack Kilby. The JK flip-flop acts only at a rising clock edge, and the output would toggle from state to state. When J and K are both low, the output is retained and no changes would occur.
2. **Waveforms** are used to check the correctness of a circuit by comparing inputs to the outputs in a "form of a wave"; therefore, the inputs would be clocked at a specific time period that the output would follow based on the combinational logic of the electronic circuit. Waveforms would not be ideal for a large number of inputs as this would become a long and tedious process. **Testbenches** enhances this process by comparing the user's Verilog code to its expected output; hence, comparing a large number of inputs and outputs would allow the user to efficiently check the correctness of a circuit.

2. Prelab

<https://docs.google.com/document/d/18KNm2l3hURA8lTZ1jOOj9OqBpmHYE14P/edit?usp=sharing&ouid=102808507017671072128&rtpof=true&sd=true>

This is the link to my prelab 4 submission.


3. Results of Experiments

Experiment 1

a.

```
1  module asyncDFF (D, Clock, ClearN, Q, QN);
2      input D, Clock, ClearN;
3      output Q, QN;
4      reg Q;
5
6      always @ (posedge Clock, negedge ClearN)
7      begin
8          if (~ClearN)
9              Q = 0;
10         else
11             Q = D;
12     end
13     assign QN = ~Q;
14 endmodule
15
```

 This is the Verilog code for a D flip flop with asynchronous low clear and complementary output.



This is the RTL view for my D flip flop with asynchronous low clear and complementary output.

Experiment 2

a.

```
1  `timescale 1 ns / 100 ps
2
3  module regDFF (D, Clock ,ClearN, Q, QN);
4      input [3:0] D;
5      input Clock, ClearN;
6      output [3:0] Q, QN;
7
8      asyncDFF DFF0 (D[0], Clock, ClearN, Q[0], QN[0]);
9      asyncDFF DFF1 (D[1], Clock, ClearN, Q[1], QN[1]);
10     asyncDFF DFF2 (D[2], Clock, ClearN, Q[2], QN[2]);
11     asyncDFF DFF3 (D[3], Clock, ClearN, Q[3], QN[3]);
12 endmodule
13
14 // asynchronous D Flip Flop
15 module asyncDFF (D, Clock, ClearN, Q, QN);
16     input D, Clock, ClearN;
17     output Q, QN;
18     reg Q;
19
20     always @ (posedge Clock, negedge ClearN)
21     begin
22         if (~ClearN)
23             Q <= 0;
24         else
25             Q <= D;
26         end
27         assign QN = ~Q;
28     endmodule
29
```

This is the Verilog code for instantiating the DFF from experiment 1 into a 4-bit register which uses D flip-flops.

b.


```

1  `timescale 1 ns / 100 ps
2
3  // register D Flip Flop Testbench
4  module regDFF_tb;
5      reg [3:0] Dtb;
6      reg Clocktb = 1'b1;
7      reg ClearNtb = 1'b1;
8      wire [3:0] Qtb, QNtb;
9
10     `define PERIOD 10
11
12     always
13         #(`PERIOD/2) Clocktb = ~Clocktb;
14
15     regDFF U0 (
16         .D (Dtb),
17         .Clock (Clocktb),
18         .ClearN (ClearNtb),
19         .Q (Qtb),
20         .QN (QNtb)
21     );
22
23     initial begin
24         $timeformat (-9, 1, "ns", 9 );
25         $monitor ( "time=%t      Dtb = %b      ClrNtb = %b      Qtb = %b      QNtb = %b", $time, Dtb, ClearNtb, Qtb, QNtb );
26         #(`PERIOD * 100)
27         $display ( "TESTING TIMEOUT" );
28         $finish;
29     end
30
31     task expectedResult (input [3:0] expected);
32         if (Qtb != expected)
33             begin
34                 $display ( "Qtb=%b, but expected value is %b", Qtb, expected);
35                 $display ( "Test Failed" );
36                 $finish;
37             end
38     endtask
39
40     task expectedResultN (input [3:0] expectedN);
41         if (QNtb != expectedN)
42             begin
43                 $display ( "QNtb=%b, but expected value is %b", QNtb, expectedN);
44                 $display ( "Test Failed" );
45                 $finish;
46             end
47     endtask
48
49     initial
50     begin
51         @(negedge Clocktb)
52         { ClearNtb, Dtb } = 5'b1_XXXX; @(negedge Clocktb) expectedResult ( 4'bxxxx ); @(negedge Clocktb) expectedResultN ( 4'bxxxx );
53         { ClearNtb, Dtb } = 5'b0_XXXX; @(negedge Clocktb) expectedResult ( 4'b0000 ); @(negedge Clocktb) expectedResultN ( 4'b1111 );
54         { ClearNtb, Dtb } = 5'b1_XXXX; @(negedge Clocktb) expectedResult ( 4'bxxxx ); @(negedge Clocktb) expectedResultN ( 4'bxxxx );
55         { ClearNtb, Dtb } = 5'b1_1101; @(negedge Clocktb) expectedResult ( 4'b1101 ); @(negedge Clocktb) expectedResultN ( 4'b0010 );
56         { ClearNtb, Dtb } = 5'b1_1010; @(negedge Clocktb) expectedResult ( 4'b1010 ); @(negedge Clocktb) expectedResultN ( 4'b0101 );
57         { ClearNtb, Dtb } = 5'b0_XXXX; @(negedge Clocktb) expectedResult ( 4'b0000 ); @(negedge Clocktb) expectedResultN ( 4'b1111 );
58         { ClearNtb, Dtb } = 5'b1_XXXX; @(negedge Clocktb) expectedResult ( 4'bxxxx ); @(negedge Clocktb) expectedResultN ( 4'bxxxx );
59         { ClearNtb, Dtb } = 5'b1_1010; @(negedge Clocktb) expectedResult ( 4'b1010 ); @(negedge Clocktb) expectedResultN ( 4'b0101 );
60         { ClearNtb, Dtb } = 5'b1_1101; @(negedge Clocktb) expectedResult ( 4'b1101 ); @(negedge Clocktb) expectedResultN ( 4'b0010 );
61         $display ( "*****Test PASSED*****" );
62         $finish;
63     end
64 endmodule
65

```

This is the Verilog code for the 4-bit register which uses D flip-flops testbench.

c.

 

These are my VCS waveforms for the 4-bit DFF register. The blocks of red indicate delay or if the output is a “don’t care (X) value”.

d.

```
Chronologic VCS simulator copyright 1991-2017
Contains Synopsys proprietary information.
Compiler version N-2017.12-SP2-14; Runtime version N-2017.12-SP2-14; Sep 21 23:24 2021
VCD+ Writer N-2017.12-SP2-14 Copyright (c) 1991-2017 by Synopsys Inc.
The file '/home/batuj1/Fall2021/lab4/regDFF_tb/inter.vpd' was opened successfully.
time= 0.0ns Dtb = xxxx ClrNtb = 1 Qtb = xxxx QNtb = xxxx
time= 25.0ns Dtb = xxxx ClrNtb = 0 Qtb = 0000 QNtb = 1111
time= 45.0ns Dtb = xxxx ClrNtb = 1 Qtb = 0000 QNtb = 1111
time= 50.0ns Dtb = xxxx ClrNtb = 1 Qtb = xxxx QNtb = xxxx
time= 65.0ns Dtb = 1101 ClrNtb = 1 Qtb = xxxx QNtb = xxxx
time= 70.0ns Dtb = 1101 ClrNtb = 1 Qtb = 1101 QNtb = 0010
time= 85.0ns Dtb = 1010 ClrNtb = 1 Qtb = 1101 QNtb = 0010
time= 90.0ns Dtb = 1010 ClrNtb = 1 Qtb = 1010 QNtb = 0101
time= 105.0ns Dtb = xxxx ClrNtb = 0 Qtb = 0000 QNtb = 1111
time= 125.0ns Dtb = xxxx ClrNtb = 1 Qtb = 0000 QNtb = 1111
time= 130.0ns Dtb = xxxx ClrNtb = 1 Qtb = xxxx QNtb = xxxx
time= 145.0ns Dtb = 1010 ClrNtb = 1 Qtb = xxxx QNtb = xxxx
time= 150.0ns Dtb = 1010 ClrNtb = 1 Qtb = 1010 QNtb = 0101
time= 165.0ns Dtb = 1101 ClrNtb = 1 Qtb = 1010 QNtb = 0101
time= 170.0ns Dtb = 1101 ClrNtb = 1 Qtb = 1101 QNtb = 0010
*****Test PASSED*****
#finish called from file "regDFF_tb.v", line 62.
#finish at simulation time 185.0ns
Simulation complete, time is 185000 ps.
```

This is my VCS simulation console for the 4-bit DFF register.


Experiment 3

a.


```
1  `timescale 1 ns / 100 ps
2
3  module regBehaveDFF (D, Clock, ClearN, Q, QN);
4      input [3:0] D;
5      input Clock, ClearN;
6      output reg [3:0] Q;
7      output [3:0] QN;
8
9      always @ (posedge Clock, negedge ClearN)
10         begin
11             if (~ClearN)
12                 Q = 4'b0000;
13             else
14                 Q = D;
15         end
16         assign QN = ~Q;
17
18     endmodule
19
```

This is my behavioral Verilog code for instantiating the DFF from experiment 1 into a 4-bit register which uses D flip-flops.

b.

 

 This is the RTL View of the structural 4-bit DFF register.



This is the RTL View of the behavioral 4-bit DFF register.

c.

From the RTL view of both behavioral and structural, both are quite similar in the lower hierarchy. For example, by clicking on each “green” block of the structural RTL view, the instantiation of the DFF is the same as the behavioral RTL view. The reason for the “green” blocks for the structural RTL view is due to the instantiation of the DFF module. Since there is no instantiation for the behavioral model, the D flip-flops can easily be seen in the behavioral view because the 4 bits are designated to each individual D flip-flop within the code. The “green” blocks of the structural code simply just show instantiation of another module; whereas, the behavioral code would show the 4 bits spread to each D flip-flop.

Experiment 4

a.

```
1  `timescale 1 ns / 100 ps
2
3  module modCount (inclk, rst, ud, load, data, count, segments1, segments2);
4      input inclk, rst, ud, load;
5      input [4:0] data;
6      output reg [4:0] count = 0;
7      output reg [6:0] segments1, segments2;
8      wire outclk;
9
10     onehertz U0(                                // calls to the onehertz module
11         .clk_50mhz (inclk),
12         .clk_lhz (outclk)
13     );
14
15     always @ (posedge outclk, posedge rst)
16     begin
17         if (rst == 1)                            // dont count if reset
18             count = 0;
19         else if (load)                            // load input into output
20             count = data;
21         else
22             if (ud == 1)                          // count up
23                 if (count == 25)
24                     begin
25                         count = 0;                // counter is 0 when reached 25
26                     end
27                 else
28                     begin
29                         count = count + 1;        // increment counter
30                     end
31             else                                  // count down
32                 begin
33                     if (count == 0)               // if there is not count...
34                         begin
35                             count = 25;          // counter starts at 25
36                         end
37                     else
38                         begin
39                             count = count - 1;   // decrement counter
40                         end
41                 end
42         end
43
44     // 7-segment display
45     always @ (count) begin
46         case (count)
47             0 : begin
48                 segments1 = 7'b0000001;
49                 segments2 = 7'b0000001;
50             end
51             1 : begin
52                 segments1 = 7'b1001111;
53                 segments2 = 7'b0000001;
54             end
55             2 : begin
56                 segments1 = 7'b0010010;
57                 segments2 = 7'b0000001;
```


58		end
59	☐	3 : begin
60		segments1 = 7'b0000110;
61		segments2 = 7'b0000001;
62		end
63	☐	4 : begin
64		segments1 = 7'b1001100;
65		segments2 = 7'b0000001;
66		end
67	☐	5 : begin
68		segments1 = 7'b0100100;
69		segments2 = 7'b0000001;
70		end
71	☐	6 : begin
72		segments1 = 7'b0100000;
73		segments2 = 7'b0000001;
74		end
75	☐	7 : begin
76		segments1 = 7'b0001111;
77		segments2 = 7'b0000001;
78		end
79	☐	8 : begin
80		segments1 = 7'b0000000;
81		segments2 = 7'b0000001;
82		end
83	☐	9 : begin
84		segments1 = 7'b0000100;
85		segments2 = 7'b0000001;
86		end
87	☐	10 : begin
88		segments1 = 7'b0000001;
89		segments2 = 7'b1001111;
90		end
91	☐	11 : begin
92		segments1 = 7'b1001111;
93		segments2 = 7'b1001111;
94		end
95	☐	12 : begin
96		segments1 = 7'b0010010;
97		segments2 = 7'b1001111;
98		end
99	☐	13 : begin
100		segments1 = 7'b0000110;
101		segments2 = 7'b1001111;
102		end
103	☐	14 : begin
104		segments1 = 7'b1001100;
105		segments2 = 7'b1001111;
106		end
107	☐	15 : begin
108		segments1 = 7'b0100100;
109		segments2 = 7'b1001111;
110		end
111	☐	16 : begin
112		segments1 = 7'b0100000;
113		segments2 = 7'b1001111;
114		end

```

115
116
117
118
119
120
121
122
123
124
125
126
127
128
129
130
131
132
133
134
135
136
137
138
139
140
141
142
143
144
145
146
147
148
149
150
151
152
153
154
155
156
157
158
159
160
161
162
163
164
165
166
167
168
169
170
171

```

```

17 : begin
    segments1 = 7'b0001111;
    segments2 = 7'b1001111;
end
18 : begin
    segments1 = 7'b0000000;
    segments2 = 7'b1001111;
end
19 : begin
    segments1 = 7'b0000100;
    segments2 = 7'b1001111;
end
20 : begin
    segments1 = 7'b0000001;
    segments2 = 7'b0010010;
end
21 : begin
    segments1 = 7'b1001111;
    segments2 = 7'b0010010;
end
22 : begin
    segments1 = 7'b0010010;
    segments2 = 7'b0010010;
end
23 : begin
    segments1 = 7'b0000110;
    segments2 = 7'b0010010;
end
24 : begin
    segments1 = 7'b1001100;
    segments2 = 7'b0010010;
end
25 : begin
    segments1 = 7'b0100100;
    segments2 = 7'b0010010;
end
26 : begin
    segments1 = 7'b0100000;
    segments2 = 7'b0010010;
end
default:
    begin
        segments1 = 7'b1111111;
        segments2 = 7'b1111111;
    end
endcase
end
endmodule

module onehertz(clk_50mhz, clk_1hz);
    input clk_50mhz;
    output clk_1hz;
    reg clk_1hz;
    reg [24:0] count;
    always @ (posedge clk_50mhz)
        begin

```

```

172 if(count == 24999999) begin
173     count <= 0;
174     $dumpfile("f.vcd");
175     clk_lhz <= ~clk_lhz;
176 end
177 else begin
178     count <= count + 1;
179 end
180 end
181 endmodule
182

```

This is my Verilog code for the 5-bit mod-25 up/down counter including a clock divider and a 7 segment display.

b.


```

1 `timescale 1 ns / 100 ps
2
3 // modCount Testbench
4 module modCount_tb;
5     reg clkfb = 1'b1;
6     reg rstfb = 1'b1;
7     reg udfb;
8     reg loadfb;
9     reg [4:0] datatb;
10    wire [4:0] counttb;
11    wire [6:0] seg1, seg2;
12    `define PERIOD 10
13
14    always
15    #('PERIOD/2) clkfb = ~clkfb;
16
17    modCount U0 (
18        .clk (clkfb),
19        .rst (rstfb),
20        .ud (udfb),
21        .load (loadfb),
22        .data (datatb),
23        .count (counttb),
24        .segments1 (seg1),
25        .segments2 (seg2)
26    );
27
28    initial begin
29        $timeformat (-9, 1, "ns", 9);
30        $monitor ( "time=%t   datatb = %b   rstfb = %b   udfb = %b   counttb = %b", $time, datatb, rstfb, udfb, counttb);
31        #('PERIOD * 100)
32        $display ( "TESTING TIMEOUT" );
33        $finish;
34    end
35
36    task expectedResult (input [4:0] expected);
37        if (counttb != expected)
38        begin
39            $display ( "counttb=%b, but expected value is %b", counttb, expected);
40            $display ( "Test Failed" );
41            $finish;
42        end
43    endtask
44
45    initial
46    begin
47        @(posedge clkfb)
48        { rstfb, loadfb, udfb, datatb } = 8'b0_1_1_0011; @(posedge clkfb) expectedResult ( 5'b00111 );
49        { rstfb, loadfb, udfb, datatb } = 8'b0_0_1_10101; @(posedge clkfb) expectedResult ( 5'b01000 );
50        { rstfb, loadfb, udfb, datatb } = 8'b0_0_1_01010; @(posedge clkfb) expectedResult ( 5'b01001 );
51        { rstfb, loadfb, udfb, datatb } = 8'b0_0_1_00000; @(posedge clkfb) expectedResult ( 5'b01010 );
52        { rstfb, loadfb, udfb, datatb } = 8'b0_0_1_01010; @(posedge clkfb) expectedResult ( 5'b01011 );
53        { rstfb, loadfb, udfb, datatb } = 8'b0_0_0_11001; @(posedge clkfb) expectedResult ( 5'b01010 );
54        { rstfb, loadfb, udfb, datatb } = 8'b0_0_0_11111; @(posedge clkfb) expectedResult ( 5'b01001 );
55        { rstfb, loadfb, udfb, datatb } = 8'b0_1_0_01010; @(posedge clkfb) expectedResult ( 5'b01010 );
56        { rstfb, loadfb, udfb, datatb } = 8'b0_0_0_01010; @(posedge clkfb) expectedResult ( 5'b01001 );
57        { rstfb, loadfb, udfb, datatb } = 8'b0_0_0_01011; @(posedge clkfb) expectedResult ( 5'b01000 );
58
59        { rstfb, loadfb, udfb, datatb } = 8'b0_0_1_01000; @(posedge clkfb) expectedResult ( 5'b01001 );
60        { rstfb, loadfb, udfb, datatb } = 8'b1_0_0_01010; @(posedge clkfb) expectedResult ( 5'b00000 );
61        { rstfb, loadfb, udfb, datatb } = 8'b1_0_1_10101; @(posedge clkfb) expectedResult ( 5'b00000 );
62        $display ( "*****Test PASSED*****" );
63        $finish;
64    end
65 endmodule

```

This is my Verilog code for the 5-bit mod-25 up/down counter testbench.

C.

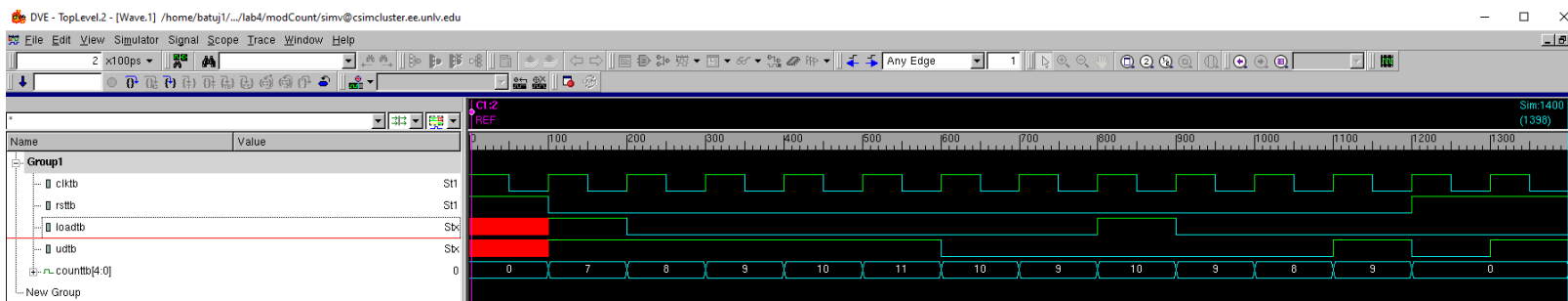


These are my VCS waveforms for the 5-bit mod-25 up/down counter.

```
Type: [Symbol] Severity: [Symbol] Code: All
Chronologic VCS simulator copyright 1991-2017
Contains Synopsys proprietary information.
Compiler version N-2017.12-SP2-14; Runtime version N-2017.12-SP2-14; Sep 26 16:27 2021
VCD+ Writer N-2017.12-SP2-14 Copyright (c) 1991-2017 by Synopsys Inc.
The file '/home/batuj1/Fall2021/lab4/modCount/inter.vpd' was opened successfully.
time= 0.0ns      datatb = xxxxx      rsttb = 1      udtb = x      counttb = 00000
time= 10.0ns     datatb = 00111      rsttb = 0      udtb = 1      counttb = 00111
time= 20.0ns     datatb = 10101      rsttb = 0      udtb = 1      counttb = 01000
time= 30.0ns     datatb = 01010      rsttb = 0      udtb = 1      counttb = 01001
time= 40.0ns     datatb = 00000      rsttb = 0      udtb = 1      counttb = 01010
time= 50.0ns     datatb = 01010      rsttb = 0      udtb = 1      counttb = 01011
time= 60.0ns     datatb = 11001      rsttb = 0      udtb = 0      counttb = 01010
time= 70.0ns     datatb = 11111      rsttb = 0      udtb = 0      counttb = 01001
time= 80.0ns     datatb = 01010      rsttb = 0      udtb = 0      counttb = 01010
time= 90.0ns     datatb = 01010      rsttb = 0      udtb = 0      counttb = 01001
time= 100.0ns    datatb = 01011      rsttb = 0      udtb = 0      counttb = 01000
time= 110.0ns    datatb = 01000      rsttb = 0      udtb = 1      counttb = 01001
time= 120.0ns    datatb = 01010      rsttb = 1      udtb = 0      counttb = 00000
time= 130.0ns    datatb = 10101      rsttb = 1      udtb = 1      counttb = 00000
*****Test PASSED*****
```

This is my VCS console for the 5-bit mod-25 up/down counter.

d.

 

This is my RTL view for the 5-bit mod-25 up/down counter including a clock divider and a 7 segment display.

e.

Fitter Status	Successful - Sun Sep 26 16:58:40 2021
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	modCount
Top-level Entity Name	modCount
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	95 / 33,216 (< 1 %)
Total combinational functions	95 / 33,216 (< 1 %)
Dedicated logic registers	31 / 33,216 (< 1 %)
Total registers	31
Total pins	28 / 475 (6 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

This is my compilation report of the total utilization, combinational ALUTs, and dedicated logic registers for the 5-bit mod-25 up/down counter including a clock divider and a 7 segment display.

f. <https://drive.google.com/file/d/1hoacqdm103irNyL9vXW9phvNSH5imaPM/view?usp=sharing>

This is the link to my video delivery of 4(b). The video will also be included within the batuj1_postlab_4.zip file.

4. Answers to questions

Question 1:

Regarding *Logic Utilization* from the *Quartus Compilation Report*, the *ALUT* is utilized to show half-ALMS (half-adaptive logic modules). Half-ALMS are half-adaptive logic modules, meaning that the ALUT has 2 combinational logic look up tables (LUTs) and 2 registers becoming one total adaptive look up table (ALUT). ALUTs show the actual number of partial or final half-ALMs in the design after it is placed. In general, the ALUT reveals the combinational logic needed for each register or flip-flop to form. The *Dedicated Logic Registers* are the two registers within the ALM. The ALM is the essential building block of supported device families and is made to maximize the performance of registers as well as resource usage. Each adaptive logic module can hold up to 8 inputs and 8 outputs. The reason for the ALM is to show the logic registers used to complete the total logic elements within the Verilog code design.

Question 2:

Clock-gating is when the clock is directed to each flip-flop within the design to reveal that each flip-flop is clocked continuously rather than individually. The purpose of clock-gating is to reduce unnecessary clocking to each register; thus, registers do not need to be clocked if the input data does not change. Clock-gating is inserted in two ways: local clock-gating and global clock-gating. Local clock-gating has the logic synthesizer find and utilize local gating opportunities and the RTL code would have the clock-gating cell instantiated within it. Global clock-gating specifically specifies the clock gating within the RTL code and follows the local clock-gating where the clock-gating cell is instantiated within it. Overall, clock-gating saves unnecessary clocking to each register by continuous clocking rather than individual clocks assigned to each individual register.

Question 3

The key difference between tasks and functions is that a function is to return a single value in regards to processing the input; whereas, a task can return multiple values and return these values using the output arguments. Tasks can also contain timing simulations where functions cannot utilize any timing. Tasks and functions are used when an operation is continuously repeated throughout the Verilog code. Instead of rewriting that same code, the task or function operation can be used. This reduces copy and paste errors and permits faster development time as well as making a code cleaner and easier to read.

5. Conclusions & Summary

This lab was one of the easier labs, and I was able to go more in depth with my knowledge of flip-flops and registers. In the CPE 200 lab, I had a hard time implementing the clock within my code; therefore, the provided clock divider definitely helped for the 4th experiment. The main issues within this lab occurred with experiment 4. When I originally coded my design, I did not take into account the clock behaving differently than my own interpretation of it; therefore, I used the clock divider. Although I had already completed the testbench, VCS console, and the VCS waveforms of my code, the clock divider gave several issues within my assignment. Without the clock divider, I would not be able to properly output my code into the DE2 board and make it properly output. I hope this issue does not continue into more labs, and I will be able to fix it for the future.