



**TONTADARYA COLLEGE OF ENGINEERING**  
**Department of Electrical & Electronics Engineering**  
 Internal Assessment – I (18EE33)

Subject: **Transformers and Generators**  
 Semester: III

Date: 10/12/2021  
 Time: 9.30am to 11.00am

Note: Answer one question from each part.  
 Assume missing data suitably.

Total Marks: 50

<b>PART-A</b>			CO
Q1.	a) Explain the operation of a practical transformer under load condition and hence develop the phasor diagram of single phase transformer under load condition	12M	1
	b) A 5 KVA, 500/250V, 50Hz, 1- $\phi$ transformer gave the following readings: O.C. Test: 500V, 1 A, 50W (HV side). S.C. Test: 25V, 10A, 60W (LV side shorted) Determine: i) Circuit constants ii) The Efficiency on full load, 0.8 lagging p.f iii) The voltage regulation on full load, 0.8 leading p.f iv) Draw the equivalent circuit.	13M	1
Q2.	a) With a neat circuit diagram, discuss in detail how to perform OC and SC tests on single phase transformer.	12M	1
	b) Find the all day efficiency of a transformer having maximum efficiency of 98% at 15kVA at unity power factor and loaded as follows: 12 Hr 2kW at 0.5 power factor 6 Hr 12kW at 0.8 power factor 6 Hr no load	13M	1
<b>PART-B</b>			
Q3.	a) Explain with the help of connection and phasor diagram how Scott connections are used to obtain two phase supply from three –phase supply mains.	12M	1
	b) Explain with circuit diagram and phasor diagram how two transformers connected in open delta can supply the power successfully.	13M	1
Q4.	a) With the help of neat circuit diagram and phasor diagram explain the operation of 3-phase star –delta transformer.	12M	1
	b) A 3 phase, 1000 KVA, 6600/1100V, transformer is delta connected on the primary and star connected on the secondary, the primary resistance per phase 1.8 $\Omega$ and secondary resistance per phase is 0.025 $\Omega$ . Determine the efficiency when the secondary is supplying full load at 0.8 p.f. and the iron loss is 15kW.	13M	1

\*\*\*\*\*

<b>Course Outcomes (COs), Students will be able to,</b>	
1	Analyze the voltage regulation, commercial and all day efficiency of single phase transformer. Explain the operation of 3-Phase transformers, on-load tap-changers and Autotransformer.
2	Analyze the performance of transformers by Sumpner's Test, phase conversion, 3-phase connections, and parallel operation
3	Analyze the effect of excitation of non-salient pole synchronous generator and determine the ATD, ATC in DC Generators.
4	Analyze the regulation of Synchronous Generator by Slip test, EMF, MMF, and ZPF Methods.
5	Analyze the performance of the salient pole Synchronous Generators on infinite bus and parallel operation.

**RBT- Revised Blooms Taxonomy Learning Levels**

I. Remember, II. Understand, III. Apply, IV. Analyze, V. Evaluate, VI. Create