

**Roll No.....**  
**Total No. of Questions: [09]**

**Total No. of Printed Pages: [01]**

**B.Sc. (IT) (Semester – 2<sup>nd</sup>)**  
**FUNDAMENTAL DIGITAL ELECTRONICS**  
**Subject Code: BITE1-206**  
**Paper ID: [130409]**

**Time: 03 Hours**

**Maximum Marks: 60**

**Instruction for candidates:**

1. Section A is compulsory. It consists of 10 parts of two marks each.
2. Section B consist of 5 questions of 5 marks each. The student has to attempt any 4 questions out of it.
3. Section C consist of 3 questions of 10 marks each. The student has to attempt any 2 questions.

**Section – A** **(2 marks each)**

- Q1. Attempt the following:
- a. Perform  $(34)_{10} - (13)_{10}$  by using 2's complement method.
  - b. What is the function of Half- adder?
  - c. What are the first five decimal digits in base 4?
  - d. State De-Morgan's second Theorem.
  - e. Compare latch and flip flop.
  - f. Why don't care conditions are required?
  - g. How combinational circuits are different from sequential circuits?
  - h. What is the disadvantage of J-K flip flop?
  - i. What are the applications of counters?
  - j. Realize the NAND gate using NOR gates only.

**Section – B** **(5 marks each)**

- Q2. Draw the logic diagram of Master Slave J-K flip flop. Explain it in detail.
- Q3. What is gate? Discuss various elements and functions of logic gates by taking suitable examples.
- Q4. Implement the following Boolean function using 3:8 decoder and external gates.  
 $F(A,B,C) = \Sigma m(2,4,5,7)$
- Q5. Find the value of x in the following:
- (a)  $(111100011.0111)_2 = (x)_{10}$  (b)  $(275)_{10} = (x)_2$
  - (c)  $(706.23)_{10} = (x)_8$  (d)  $(6327.4051)_8 = (x)_{16}$
  - (e)  $(365)_x = (194)_{10}$
- Q6. Explain clock pulse generator using 555 Timer as Multivibrator.

**Section – C** **(10 marks each)**

- Q7. Implement the following Boolean function using 8:1 multiplexer  
 $F(A,B,C,D) = \Sigma m(2,4,5,7,10,14)$
- Q8. Design a Binary Adder/Subtractor circuit by using logic gates and explain it in detail.
- Q9. Design a 3-bit, Asynchronous down counter.