

Mastering Physics Solutions Chapter 24

Alternating Current Circuits

<https://www.aplustopper.com/mastering-physics-solutions-chapter-24-alternating-current-circuits/>
<http://bit.ly/2lhkgOU>
<https://drive.google.com/drive/u/0/folders/1KhQr9G59axJUslSSbE25Ldj4tdq8qnxU>
<http://bit.ly/2kQg1JE>
https://docs.google.com/presentation/d/e/2PACX-1vTuHlxTxAILwp-BovugSINyaGf8MVMltGTaxMxeyGYbwXpyQ1jAYufooT_vGlv6eNTE-UEpnTnoqMed/pub?start=false&loop=false&delayms=3000
<http://bit.ly/2MCsOwa>
https://docs.google.com/document/d/e/2PACX-1vQG4r_rHrM6v8EwjoutSNdcjwIQWNaRkHRloYNUpZfw3PSiHYVZOA1iY7sBpU02ZDNw_2tcJKT8Uzi/pub
<http://bit.ly/2JZPlnV>
<https://sites.google.com/site/aplustopperguide/mastering-physics-solutions-chapter-24-alternating-current-circuits>
<http://bit.ly/2t4fcl4>
<http://aplustoppernotes.blogspot.com/2018/06/mastering-physics-solutions-chapter-24.html>
<http://bit.ly/2HWMYgR>
<https://aplustoppernotes.wordpress.com/2018/06/18/mastering-physics-solutions-chapter-24-alternating-current-circuits/>
<http://bit.ly/2t6xwKc>

Chapter 24 Alternating Current Circuits Q.1CQ

How can the rms voltage of an ac circuit be nonzero when its average value is zero? Explain.

Solution:

For a complete cycle the voltage oscillates between positive and negative symmetrically.

Therefore the sum of symmetric positive and negative values will become zero and therefore the average value of ac - voltage is zero for a complete cycle.

But when we calculate the rms value of ac - voltage we first calculate the square of the voltage

Therefore whether the voltage is positive or negative its square is a positive Therefore the rms voltage of ac is always non zero.

Chapter 24 Alternating Current Circuits Q.1P

An ac generator produces a peak voltage of 55 V. What is the rms voltage of this generator?

Solution:

The peak voltage of ac generator $V_{\max} = 55\text{V}$

But rms voltage of ac is given by $V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}}$

$$\therefore V_{\text{rms}} = \frac{55\text{V}}{\sqrt{2}}$$

$$= \frac{55}{1.414} \text{V}$$

$$\boxed{V_{\text{rms}} = 39 \text{ V}}$$