 


Decoder

The combinational circuit that change the binary information into 2^N output lines is known as **Decoders**. The binary information is passed in the form of N input lines. The output lines define the 2^N -bit code for the binary information. In simple words, the **Decoder** performs the reverse operation of the **Encoder**. At a time, only one input line is activated for simplicity. The produced 2^N -bit output code is equivalent to the binary information.




There are various types of decoders which are as follows:

2 to 4 line decoder:

In the 2 to 4 line decoder, there is a total of three inputs, i.e., A_0 , and A_1 and E and four outputs, i.e., Y_0 , Y_1 , Y_2 , and Y_3 . For each combination of inputs, when the enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 2 to 4 line decoder are given below.

Block Diagram:

 

Truth Table:

Enable	INPUTS		OUTPUTS			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

The logical expression of the term Y₀, Y₁, Y₂, and Y₃ is as follows:


$$Y_3 = E \cdot A_1 \cdot A_0$$

$$Y_2 = E \cdot A_1 \cdot A_0'$$

$$Y_1 = E \cdot A_1' \cdot A_0$$

$$Y_0 = E \cdot A_1' \cdot A_0'$$

 
Logical circuit of the above expressions is given below:



3 to 8 line decoder:

The 3 to 8 line decoder is also known as **Binary to Octal Decoder**. In a 3 to 8 line decoder, there is a total of eight outputs, i.e., Y₀, Y₁, Y₂, Y₃, Y₄, Y₅, Y₆, and Y₇ and three outputs, i.e., A₀, A₁, and A₂. This circuit has an enable input 'E'. Just like 2 to 4 line decoder, when enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 3 to 8 line encoder are given below.

Block Diagram:

 

Truth Table:

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

The logical expression of the term Y₀, Y₁, Y₂, Y₃, Y₄, Y₅, Y₆, and Y₇ is as follows:

$$Y_0 = A_0 \cdot A_1 \cdot A_2'$$

$$Y_1 = A_0 \cdot A_1' \cdot A_2'$$

$$Y_2 = A_0 \cdot A_1 \cdot A_2$$

$$Y_3 = A_0 \cdot A_1' \cdot A_2$$


$$Y_4 = A_0' \cdot A_1 \cdot A_2$$

$$Y_5 = A_0 \cdot A_1' \cdot A_2$$

$$Y_6 = A_0' \cdot A_1 \cdot A_2$$

$$Y_7 = A_0 \cdot A_1 \cdot A_2$$

 Logical circuit of the above expressions is given below:



4 to 16 line Decoder

In the 4 to 16 line decoder, there is a total of 16 outputs, i.e., $Y_0, Y_1, Y_2, \dots, Y_{16}$ and four inputs, i.e., $A_0, A_1, A_2,$ and A_3 . The 3 to 16 line decoder can be constructed using either 2 to 4 decoder or 3 to 8 decoder. There is the following formula used to find the required number of lower-order decoders.

Required number of lower order decoders = m_2/m_1

$$m_1 = 8$$

$$m_2 = 16$$

$$\text{Required number of 3 to 8 decoders} = \frac{16}{8} = 2$$

Block Diagram:

The logical expression of the term $A_0, A_1, A_2, \dots, A_{15}$ are as follows:

$$\begin{aligned}
 Y_0 &= A_0' \cdot A_1' \cdot A_2' \cdot A_3' \\
 Y_1 &= A_0' \cdot A_1' \cdot A_2' \cdot A_3 \\
 Y_2 &= A_0' \cdot A_1' \cdot A_2 \cdot A_3' \\
 Y_3 &= A_0' \cdot A_1' \cdot A_2 \cdot A_3 \\
 Y_4 &= A_0' \cdot A_1 \cdot A_2' \cdot A_3' \\
 Y_5 &= A_0' \cdot A_1 \cdot A_2' \cdot A_3 \\
 Y_6 &= A_0' \cdot A_1 \cdot A_2 \cdot A_3' \\
 Y_7 &= A_0' \cdot A_1 \cdot A_2 \cdot A_3 \\
 Y_8 &= A_0 \cdot A_1' \cdot A_2' \cdot A_3' \\
 Y_9 &= A_0 \cdot A_1' \cdot A_2' \cdot A_3 \\
 Y_{10} &= A_0 \cdot A_1' \cdot A_2 \cdot A_3' \\
 Y_{11} &= A_0 \cdot A_1' \cdot A_2 \cdot A_3 \\
 Y_{12} &= A_0 \cdot A_1 \cdot A_2' \cdot A_3' \\
 Y_{13} &= A_0 \cdot A_1 \cdot A_2' \cdot A_3 \\
 Y_{14} &= A_0 \cdot A_1 \cdot A_2 \cdot A_3' \\
 Y_{15} &= A_0 \cdot A_1 \cdot A_2 \cdot A_3
 \end{aligned}$$

Logical circuit of the above expressions is given below:

