

Simulate the Circuit In Tinker cad for

1. LED
2. Touch Sensor
3. Ultrasonic Sensor
4. LDR
5. IR Sensor
6. DHT
7. Traffic Light Simulation using R,Y,G led and Transistor as a switch