

## EXPERIMENT NO. 2

**AIM:** Observe and plot the output Wave shape of Op-Amp R-C differentiating circuits, RC integrating circuits for square wave input.

### THEORY:

(a) **Differentiator:** It is an op-amp circuit which performs the mathematical operation of differentiation. That is the output waveform is the derivative or differential of the input voltage. That is  $V_o = -R_f C \frac{d(V_{in})}{dt}$ . The differentiator circuit is constructed from basic inverting amplifier by replacing the input resistance  $R_i$  with capacitor  $C$ . This circuit also works as high pass filter.

### Hints for Design of differentiator

Given  $f = 1 \text{ KHz}$

So  $T = 1/f = 1 \text{ mS}$

Design equation is  $T = 2\pi R_f C$

Let  $C = 0.01 \mu\text{F}$

Then  $R_f = 15 \text{ K}\Omega$

Let  $R_i = R_f/10 = 1.5 \text{ K}\Omega$

### CIRCUIT DIAGRAM:

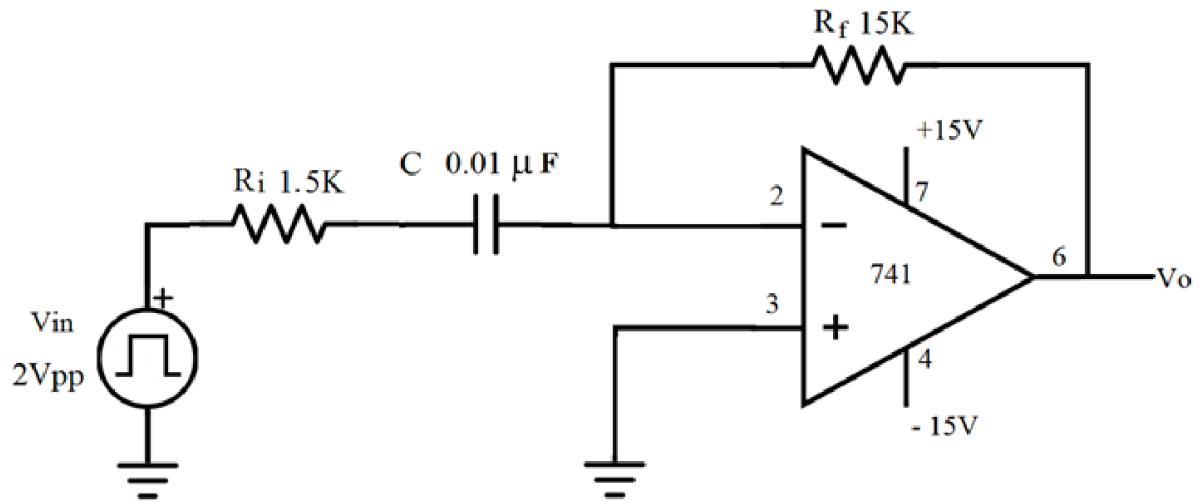


Figure 2.1: Circuit diagram of differentiator.

**Observation:**

Take  $V_{in} = 2V_{pp}$ , 1KHz square wave and observe output

**Graph:** draw the input and output waveforms on the graph.

(b) **Integrator:** It is a closed loop op-amp circuit which performs the mathematical operation of integration. That is the output waveform is the integral of the input voltage and is given by  $V_o = (-1/R_f C) \int V_{in} dt$ . The integrator circuit is constructed from basic inverting amplifier by replacing the feedback resistance  $R_f$  with capacitor  $C$ . This circuit also works as low pass filter.

**Hints for Design of integrator**

Given  $f = 1 \text{ KHz}$

So  $T = 1/f = 1 \text{ ms}$

Design equation is  $T = 2\pi R_i C$

Let  $C = 0.01\mu\text{F}$

Then  $R_i = 15\text{K}\Omega$

Take  $R_f = 10R_i = 150\text{K}\Omega$

### CIRCUIT DIAGRAM:

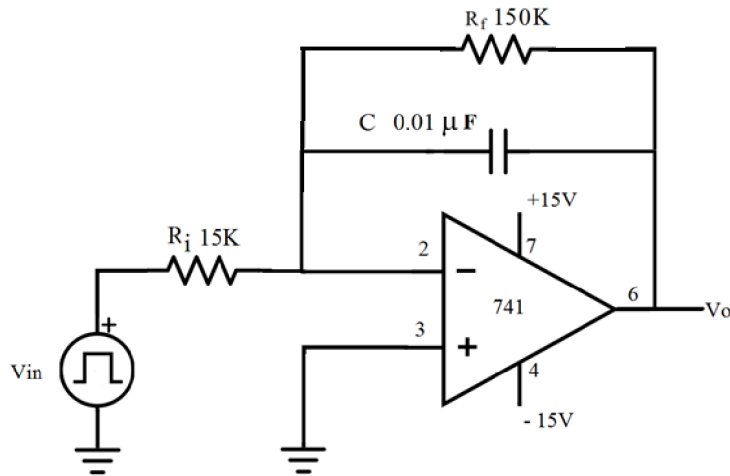


Figure 2.2: Circuit diagram of Integrator.

### Observation:

Take  $V_{in} = 2\text{V}_{pp}$ ,  $1\text{KHz}$  square wave and observe output

**Graph:** draw the input and output waveforms on the graph.

### CONCLUSION: