

**School Code: \_\_\_\_\_**  
**PRACTICAL EXAMINATION OF AISSCE 2026**  
**Physics (042)**

Class : XII

Date : \_\_\_\_\_

Max. Marks: 30

Time Allowed: \_\_\_\_\_

**Q1. Two experiments one from each section**

**(7+7 Marks)**

**Section A**

1. To determine resistivity of two / three wires by plotting a graph for potential difference versus current.
2. To find resistance of a given wire / standard resistor using metre bridge.
3. To verify the laws of combination (series) of resistances using a metre bridge.
4. To determine resistance of a galvanometer by half-deflection method and to find its figure of merit.

**Section B**

5. To find the focal length of a convex lens by plotting graphs between  $u$  and  $v$  or between  $1/u$  and  $1/v$ .
6. To find the focal length of a concave lens, using a convex lens.
7. To determine angle of minimum deviation for a given prism by plotting a graph between angle of incidence and angle of deviation.
8. To draw the I-V characteristic curve for a p-n junction in forward bias and reverse bias.

**Q2. Practical record [experiments and activities]**

**(5 Marks)**

**Q3. One activity**

**(3 Marks)**

1. To assemble the components of a given electrical circuit.
2. To identify a diode, an LED, a resistor and a capacitor from a mixed collection of such items.
3. To draw the diagram of a given open circuit comprising at least a battery, resistor/rheostat, key, ammeter and voltmeter. Mark the components that are not connected in proper order and correct the circuit and also the circuit diagram.

**Q4. Investigatory Project**

**(3 Marks)**

**Q5. Viva on experiments, activities and project**

**(5 Marks)**

**Internal Examiner**

xxxxxxxxxxxxxx

OASIS ID : \_\_\_\_\_

School Code: \_\_\_\_\_

**External Examiner**

xxxxxxxxxxxxxx

Examiner No: \_\_\_\_\_

School Code: \_\_\_\_\_