

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

- **D.C. Electricity**

- Current

Current is the rate of flow of charge

$$I = \Delta Q / \Delta t$$

I: Current (A)

Q or q: Charge (C)

T: time (s)

- Voltage

Voltage (Potential Difference) is the change in energy (work done) to each coulomb of charge between two points on a circuit, or two points across an electric field

$$V = \Delta E / Q$$

V: Voltage (V)

$\Delta E$  or W: Change in energy/Work (J)

Q or q: Charge (C)

- Resistance & Ohm's Law

Resists/limits the flow of current

Each ohm ( $\Omega$ ) of resistance measures how many volts are required for each amp of current to pass through a resistor

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$$V = IR$$

V: Voltage (V)

I: Current (A)

R: Resistance ( $\Omega$ )

- Power

The rate of work done in a circuit

$$P = IV$$

$$P = I^2R \leftarrow \text{Ohm's Law substitutions} \rightarrow P = V^2/R$$

P: Power (W)

V: Voltage (V)

I: Current (A)

R: Resistance ( $\Omega$ )

- Internal Resistance of a Battery

Batteries can be thought of as having an ideal voltage supply E.M.F. (Electromotive Force) in series with an internal resistance

$$V = \epsilon - Ir$$

V: Voltage across battery (V)

$\epsilon$ : E.M.F. of battery (V)

I: Current running through battery (A)

# Electrical Systems

## Structure

### [Level 3 Physics Formula Sheet](#)

r: Internal Resistance of battery ( $\Omega$ )

- [Kirchhoff's Laws](#)

- **Kirchhoff's Current Law**

- "At any junction in a circuit, the total current entering the junction equals the total current leaving the junction"*

- **Kirchhoff's Voltage Law**

- "Around any closed path of a circuit, the total of all the potential differences,  $V$ , is zero"*

### [D.C. Circuit Construction Kit - PhET](#)

### [D.C. Circuit Lab - PhET](#)

- [Capacitors](#)

Capacitors store energy in the form of an electric field

Capacitance is the amount of Charge stored per Volt on capacitor plates

$$C = Q/V$$

C: [Capacitance](#) (F: [Farad](#))

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

**NB:** the Farad is a very large unit and is therefore usually given in:

$$\mu\text{F} = 10^{-6} \text{ F}$$

$$\text{nF} = 10^{-9} \text{ F}$$

$$\text{pF} = 10^{-12} \text{ F}$$

Q or q: Charge stored on capacitor plates (C)

V: Voltage (Potential Difference) between capacitor plates (V)

Capacitance depends on:

- The area of the capacitor plates

$$C \propto A$$

- The distance between the plates

$$C \propto 1/d$$

- $\therefore C \propto A/d$

$$\therefore C = \epsilon_0 A/d$$

C: Capacitance (F: Farad)

A: Area of capacitor plates ( $\text{m}^2$ )

d: Distance between the plates (m)

$\epsilon_0$ : Permittivity of free space

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ Fm}^{-1}$$

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

- **Dielectric**

- An insulating material placed in between the capacitor plates to increase the Capacitance
- Dielectric,  $\epsilon_r$ , is a ratio that determines that factor that the Capacitance will increase by This is unique to each material used

$$C = \epsilon_r \epsilon_0 A/d$$

### PhET Application on Capacitors & Dielectrics

- **Networks of Capacitors**

- **Capacitors in Series**

$$1/C_t = 1/C_1 + 1/C_2 + 1/C_3 + \dots$$

$1/C_t$ : Inverse of Total Capacitance ( $C^{-1}$ )

$1/C_1$  etc: Inverse of each individual capacitor ( $C^{-1}$ )

- **Capacitors in Parallel**

$$C_t = C_1 + C_2 + C_3 + \dots$$

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$C_t$ : Total Capacitance (F)

$C_1$  etc: each individual capacitor (F)

- Energy Stored in a Capacitor

$$E_p = \frac{1}{2} QV$$

$$E_p = \frac{1}{2} CV^2 \leftarrow \text{Substituting } Q = CV$$

$$E_p = \frac{Q^2}{2C} \leftarrow \text{Substituting } Q/C = V$$

$E_p$ : Energy stored in a capacitor (J)

$C$ : Capacitance (F: Farad)

$Q$  or  $q$ : Charge stored on capacitor plates (C)

$V$ : Voltage (Potential Difference) between capacitor plates (V)

- Charging & Discharging a Capacitor  
(PhET App on Capacitors)

- **Time Constant**

The time it takes for a capacitor to charge up to 63% of the difference between the initial value and the final value.

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

The time it takes for a capacitor to discharge down to 37% of its initial value.

$$\tau = RC$$

$\tau$ : Time Constant (s)

R: Resistance in circuit ( $\Omega$ )

C: Capacitance (F)

Charging	Discharging
$V = V_b \times (1 - 0.37^n)$ <b>OR</b> $V = V_b \times (1 - e^{-t/\tau})$	$V = V_c \times 0.37^n$ <b>OR</b> $V = V_b \times e^{-t/\tau}$
Voltage increases from zero to battery voltage	Voltage decreases from initial voltage to zero
$V_b = V_C + V_R$	$V_C = V_R$
Current $\propto V_R$	Current $\propto V_R$
$I = I_i \times 0.37^n$ <b>OR</b> $I = I_i \times e^{-t/\tau}$	$I = I_i \times 0.37^n$ <b>OR</b> $I = I_i \times e^{-t/\tau}$
Current decreases from initial current to zero	

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

*These formulas are not given on the formula sheet*

V: Voltage across capacitor at a given time (V)

$V_b$ : Voltage of charging battery (V)

$V_c$ : Initial voltage across discharging capacitor (V)

$V_R$ : Voltage across Resistor (V)

I: Current at a given time (A)

$I_i$ : Initial Current (A)

n: Number of Time Constants that have passed

e: Euler's number is an irrational number

$e \approx 2.71828$

$e^{-1} \approx 0.367879$  close to 37%

**$n = t/\tau$**  ← (time in seconds  $\div$  Time Constant )

- **Inductors**

Inductors store energy in the form of a magnetic field



# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

#### ■ Magnetic Flux

The product of the magnetic field,  $B$ , penetrating an area,  $A$ , normal to the field

$$\phi = BA$$

$\phi$ : Magnetic Flux (weber:  $\text{Wb} = \text{Vs}$ )

$B$ : Magnetic Field (Tesla:  $\text{T}$ )

$A$ : Area normal to the field ( $\text{m}^2$ )

When the magnetic field,  $B$ , and area,  $A$ , are not at right angles, then

$$\phi = BA\sin(\theta)$$

$\theta$ : Angle between magnetic field,  $B$ , and area,  $A$

**NB:** Weber Unit

$$\text{Wb} = \text{Tm}^2 = \text{Vs} = \text{J/A} = (\text{kgm}^2)/(\text{s}^2\text{A})$$

#### ● Lenz's Law

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

*“An induced current will always flow in the direction that will oppose the changing flux that caused it”*

This is an extension of the conservation of energy law

- Faraday's Law

The induced voltage, e.m.f., is directly proportional to the rate of change of flux

$$V = - \Delta\phi / \Delta t$$

OR

$$\varepsilon = - \Delta\phi / \Delta t$$

V OR  $\varepsilon$ : Induced e.m.f. (V)

$\Delta\phi$ : Change in Magnetic Flux (Wb)

$\Delta t$ : Change in time (s)

- : to remind you that the induced e.m.f. always opposes the change in flux - Lenz's Law

### Faraday's Law PhET Application

- Transformers

The ratio of the secondary to primary voltage is equal to the ratio of the secondary to primary turns

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$$V_s/V_p = N_s/N_p$$

$V_s$ : Secondary Voltage (V)

$V_p$ : Primary Voltage (V)

$N_s$ : Secondary Turns

$N_p$ : Primary Turns

In an ideal transformer:

**Secondary Power = Primary Power**

In reality, energy is lost through heat from eddy currents generated in the soft iron core from the changing flux.

- Inductance

Mutual Inductance	<u>Self Inductance</u>
$V = -m\Delta I/\Delta t$	$V = -L\Delta I/\Delta t$
m: Mutual Inductance (H: Henrys)	L: Self Inductance (H: Henrys)
-: to remind you of Lenz's Law (inductor will react against	

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

any change in flux)
$V$ or e.m.f. : Induced Voltage or back e.m.f. (V)
$\Delta I$ : Change in Current (A)
$\Delta t$ : Change in Time (s)

- **Charging & Discharging an Inductor**  
(PhET App on Inductors)
  - **Time Constant**

The time it takes for an inductor to discharge down to 37% of its initial value.

$$\tau = L/R$$

$\tau$ : Time Constant (s)

R: Resistance in circuit ( $\Omega$ )

L: Inductance (H)

Powering Up	Powering Down
$V = V_L \times 0.37^n$ <b>OR</b> $V = V_L \times e^{-t/\tau}$	$V = V_L \times 0.37^n$ <b>OR</b> $V = V_L \times e^{-t/\tau}$

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

Voltage decreases from initial voltage ( $V_L = -V_b$ ) to zero	Voltage decreases from initial voltage ( $V_L = V_b$ ) to zero
$V_b = V_L + V_R$	$V_L = V_R$
Current $\propto V_R$	Current $\propto V_R$
$I = I_i (1 - 0.37^n)$ <b>OR</b> $I = I_i (1 - e^{-t/\tau})$	$I = I_i \times 0.37^n$ <b>OR</b> $I = I_i \times e^{-t/\tau}$
<b>Current increases from zero current to a max</b>	<b>Current decreases from initial current to zero</b>
<b><i>These formulas are not given on the formula sheet</i></b>	

V: Voltage across inductor at a given time (V)

$V_b$ : Voltage of charging battery (V)

$V_L$ : Initial voltage across inductor (V)

$V_R$ : Voltage across Resistor (V)

I: Current at a given time (A)

$I_i$ : Initial Current (A)

n: Number of Time Constants that have passed

e: Euler's number is an irrational number

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$$e \approx 2.71828$$

$$e^{-1} \approx 0.367879 \text{ close to } 37\%$$

$$n = t/\tau \leftarrow (\text{time in seconds} \div \text{Time Constant})$$

- **A.C. Electricity**

- **A.C. Power & Root Mean Squared (r.m.s.) Current and Voltage**

The average power in an a.c. circuits is half the maximum power

$$\text{Power}_{av} = \frac{1}{2} \text{Power}_{max}$$

$I_{r.m.s.} \text{ to } I_{max}$	$V_{r.m.s.} \text{ to } V_{max}$
$I_{av} \times V_{av} = (I_{max} \times V_{max})/2$ $I_{av}^2 \times R = (I_{max}^2 \times R)/2$ $\therefore I_{av}^2 = (I_{max}^2)/2$ $I_{av} = I_{max}/\sqrt{2}$ $\sqrt{2} \times I_{av} = I_{max}$ $\therefore \sqrt{2} \times I_{r.m.s.} = I_{max}$	$I_{av} \times V_{av} = (I_{max} \times V_{max})/2$ $V_{av}^2/R = (V_{max}^2/R)/2$ $\therefore V_{av}^2 = (V_{max}^2)/2$ $V_{av} = V_{max}/\sqrt{2}$ $\sqrt{2} \times V_{av} = V_{max}$ $\therefore \sqrt{2} \times V_{r.m.s.} = V_{max}$

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

∴ The average Current is equal to the maximum Current  $\times 1/\sqrt{2}$

∴ The average Voltage is equal to the maximum Voltage  $\times 1/\sqrt{2}$

$1/\sqrt{2} = 0.707$  (3s.f.) So  $I_{\text{r.m.s.}}$  &  $V_{\text{r.m.s.}}$  Are roughly 71% of their maximum values

- **A.C. Resistors**

$$V_{\text{max}} = I_{\text{max}} \times R$$

$$V_{\text{r.m.s.}} = I_{\text{r.m.s.}} \times R$$

Work in r.m.s. Or max but **not** both together

The voltage drop across a resistor is **always in phase** with the current running through the resistor

$$V \propto I$$

- **A.C. Capacitors**

$$V_c = I \times X_c$$

$V_c$ : Voltage drop across the capacitor (V)

$I$ : Current (A)

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$X_c$ : [Reactance of the capacitor](#) ( $\Omega$ )

*NB: Again work in either r.m.s. Or max*

$$X_c = 1/(\omega C) \quad \text{OR} \quad X_c = 1/(2\pi f C)$$

$X_c$ : Reactance of the capacitor ( $\Omega$ )

$\omega$ : Angular velocity of a.c. current ( $\text{rads}^{-1}$ )

$$\omega = 2\pi f$$

$f$ : frequency of a.c. current (Hz)

$C$ : Capacitance (F)

$V_c$  is always  $90^\circ$  behind the current

( $V_c$  lags  $I$  by  $\pi$  rad) - This is because  $V_c \propto Q$  and it takes time for the charge to run on and off the plates

#### ○ **A.C. Inductors**

$$V_L = I \times X_L$$

$V_L$ : Voltage drop across the inductor (V)

$I$ : Current (A)

$X_L$ : [Reactance of the inductor](#) ( $\Omega$ )

*NB: Again work in either r.m.s. Or max*



# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$$X_L = \omega L \quad \text{OR} \quad X_L = 2\pi fL$$

$X_L$ : Reactance of the inductor ( $\Omega$ )

$\omega$ : Angular velocity of a.c. current ( $\text{rads}^{-1}$ )

$$\omega = 2\pi f$$

$f$ : frequency of a.c. current (Hz)

$L$ : Inductance (H)

$V_L$  is always  $90^\circ$  ahead of the current

( $V_L$  leads  $I$  by  $\pi$  rad) - This is because  $V_L \propto -\Delta I/\Delta t$ ,

Faraday's Law, and the induced voltage reacts

against any change in current. The rate of change of current is maximum when the current is zero (see a.c. current graph)

- LCR Circuits and Resonance

$$V_s = I \times Z$$

$V_s$ : Voltage of the a.c. supply (V)

$I$ : Current (A)

$Z$ : Impedance of the whole circuit ( $\Omega$ )

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

$$V_s = \sqrt{((V_L - V_C)^2 + V_R^2)}$$

$$Z = \sqrt{((X_L - X_C)^2 + R^2)}$$

$$V_s = IZ$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$V_R = IR$$

A phasor diagram is a way to relate the phase relationships between the supply, inductor, capacitor and resistor in voltage drops or impedances, reactances and resistances

*NB: Again work in either r.m.s. Or max*

**Angle of the Impedance, Z, or Source Voltage, Vs, to the current**

$$\tan(\theta) = (X_L - X_C)/R = (V_L - V_C)/V_R$$

$$\theta = \tan^{-1}((X_L - X_C)/R) = \tan^{-1}((V_L - V_C)/V_R)$$

### MIT Applet on RCL Phase Relationships of XL, XC & R

**Resonance in the LCR Circuit**

# Electrical Systems

## Structure

### Level 3 Physics Formula Sheet

Because  $X_L$  and  $X_C$  are  $180^\circ$  apart, they directly oppose one another. Resonance will occur when  $X_L = X_C$  and resonant frequency,  $f_o$ , can be found

$$X_L = X_C$$

$$2\pi fL = 1/(2\pi fC)$$

$$f_o = 1/(2\pi\sqrt{LC})$$

NB: that  $Z$  and  $V_s$  will be in phase with the current