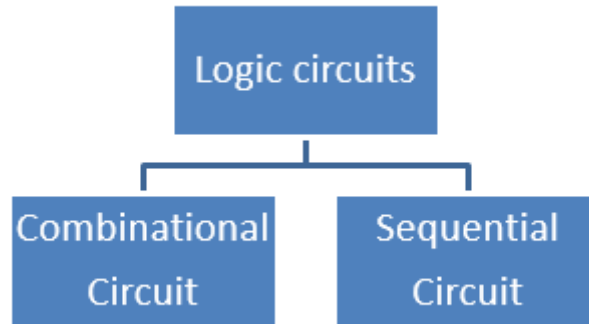


Combinational Logic Circuit




Combinational Logic circuits

The combinational logic circuits are the circuits that contain different types of logic gates. Simply, a circuit in which different types of logic gates are combined is known as a **combinational logic circuit**. The output of the combinational circuit is determined from the present combination of inputs, regardless of the previous input. The input variables, logic gates, and output variables are the basic components of the combinational logic circuit. There are different types of combinational logic circuits, such as Adder, Subtractor, Decoder, Encoder, Multiplexer, and De-multiplexer.


A combinational circuit is a combination of three things.

 1. **Input variables**
2. **Logic gates**
3. **Output variables**



There are the following characteristics of the combinational logic circuit:

 - At any instant of time, the output of the combinational circuits depends only on the present input terminals.
- The combinational circuit doesn't have any backup or previous memory. The present state of the circuit is not affected by the previous state of the input.
- The n number of inputs and m number of outputs are possible in combinational logic circuits.




The ' n ' input variable comes from the external source while the ' m ' output variable goes to the external destination. In many applications, the source or destinations are storage registers.

Half Adder

The Half-Adder is a basic building block of adding two numbers as two inputs and produce out two outputs. The adder is used to perform OR operation of two single bit binary numbers. The **augend** and **addend** bits are two input states, and '**carry**' and '**sum**' are two output states of the half adder.

Block diagram

 

Truth Table

Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

In the above table,

1. 'A' and 'B' are the input states, and 'sum' and 'carry' are the output states.
2. The carry output is 0 in case where both the inputs are not 1.
3. The least significant bit of the sum is defined by the 'sum' bit.

The SOP form of the sum and carry are as follows:

$$\text{Sum} = x'y + xy'$$

$$\text{Carry} = xy$$


Construction of Half Adder Circuit:

In the block diagram, we have seen that it contains two inputs and two outputs. The **augend** and **addend** bits are the input states, and **carry** and **sum** are the output states of the half adder. The half adder is designed with the help of the following two logic gates:

1. 2-input AND Gate.
2. 2-input Exclusive-OR Gate or Ex-OR Gate

 1. 2-input Exclusive-OR Gate or Ex-OR Gate

The **Sum** bit is generated with the help of the **Exclusive-OR** or **Ex-OR** Gate.



The above is the symbol of the **EX-OR** gate. In the above diagram, 'A' and 'B' are the inputs, and the 'SUMOUT' is the final outcome after performing the XOR operation of both numbers.


The truth table of the EX-OR gate is as follows:

Input		Output
A	B	SUMOUT
0	0	0
0	1	1
1	0	1
1	1	0

From the above table, it is clear that the XOR gate gives the result 1 when both of the inputs are different. When both of the inputs are the same, the XOR gives the result 0. To learn more about the XOR gate, [click here](#).

 2. 2-input AND Gate:

The XOR gate is unable to generate the carry bit. For this purpose, we use another gate called AND Gate. The AND gate gives the correct result of the carry.



The above is the symbol of the **AND** gate. In the above diagram, 'A' and 'B' are the inputs, and 'OUT' is the final outcome after performing AND operation of both numbers.


There is the following truth table of AND Gate:

Input		Output
A	B	OUT
0	0	0
0	1	0
1	0	0
1	1	1

From the above table, it is clear that the AND gate gives the result 1 when both of the inputs are 1. When both of the inputs are different and 0, the AND gates gives the result 0. To learn more about the AND gate

Half-Adder logical circuit:

 So, the Half Adder is designed by combining the 'XOR' and 'AND' gates and provide the sum and carry.



There is the following **Boolean expression** of Half Adder circuit:



$$\text{Sum} = A \text{ XOR } B \text{ (A+B)}$$

$$\text{Carry} = A \text{ AND } B \text{ (A.B)}$$

Full Adder

The half adder is used to add only two numbers. To overcome this problem, the full adder was developed. The full adder is used to add three 1-bit binary numbers A, B, and carry C. The full adder has three input states and two output states i.e., sum and carry.

Block diagram

  

Truth Table


Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

In the above table,

- 'A' and 'B' are the input variables. These variables represent the two significant bits which are going to be added
- 'C_{in}' is the third input which represents the carry. From the previous lower significant position, the carry bit is fetched.
- The 'Sum' and 'Carry' are the output variables that define the output values.
- The eight rows under the input variable designate all possible combinations of 0 and 1 that can occur in these variables.

Note: We can simplify each of the output 'Boolean function' with the help of the unique map method.

 
The SOP form can be obtained with the help of K-map as:




$$\text{Sum} = x'y'z + x'yz' + xy'z' + xyz$$

$$\text{Carry} = xy + xz + yz$$

Construction of Half Adder Circuit:

 


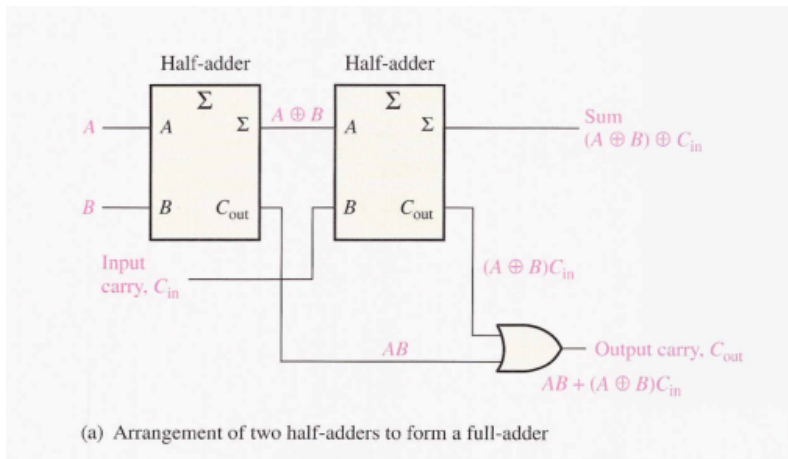

The above block diagram describes the construction of the Full adder circuit. In the above circuit, there are two half adder circuits that are combined using the OR gate. The first half adder has two single-bit binary inputs A and B. As we know that, the half adder produces two outputs, i.e., Sum and Carry. The 'Sum' output of the first adder will be the first input of the second half adder, and the 'Carry' output of the first adder will be the second input of the second half adder. The second half adder will again provide 'Sum' and 'Carry'. The final outcome of the Full adder circuit is the 'Sum' bit. In order to find the final output of the 'Carry', we provide the 'Carry' output of the first and the second adder into the OR gate. The outcome of the OR gate will be the final carry out of the full adder circuit.

The MSB is represented by the final 'Carry' bit.

 The full adder logic circuit can be constructed using the 'AND' and the 'XOR' gate with an OR gate.



The actual logic circuit of the full adder is shown in the above diagram. The full adder circuit construction can also be represented in a Boolean expression.

Sum:

- Perform the XOR operation of input A and B.
- Perform the XOR operation of the outcome with carry. So, the sum is $(A \text{ XOR } B) \text{ XOR } C_{in}$ which is also represented as:
 $(A \oplus B) \oplus C_{in}$

Carry:

1. Perform the 'AND' operation of input A and B.
2. Perform the 'XOR' operation of input A and B.
3. Perform the 'OR' operations of both the outputs that come from the previous two steps. So the 'Carry' can be represented as:
 $A.B + (A \oplus B)$