
## Primeira Avaliação - Circuitos Elétricos - Professor: André E. Lazzaretti

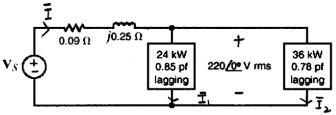1) Encontre  $\mathbf{V}_{\epsilon}$  no circuito a seguir, considerando f=60Hz. (Valor 2,5 pontos - somente acerto integral).



$$P_1 = V_L I_1 P F_1$$
 $I_1 = \frac{24k}{220(0.85)}$ 
 $I_1 = 128.34 A 2ms$ 
 $I_2 = 128.34 L-col^{-1}(0.85)$ 
 $I_3 = 128.34 L-31.79^{\circ} A 2ms$ 
 $I_4 = \frac{P_2}{V_L P F_2} = \frac{36k}{(220)(0.78)}$ 
 $I_4 = 209.8 A 2ms$ 
 $I_4 = 209.8 L-col^{-1}(0.78)$ 
 $I_5 = 209.8 L-38.74^{\circ} A 2ms$ 
 $I_7 = I_1 + I_9$ 

$$\bar{I} = 198.34 \angle -31.79^{\circ} + 209.8 \angle -38.74^{\circ}$$


$$\bar{I} = 337.55 \angle -36.10^{\circ} \text{ A rms}$$

$$\bar{V}_{S} = \bar{I} (0.09 + j0.25) + 220 \angle 0^{\circ}$$

$$\bar{V}_{S} = (337.55 \angle -36.10^{\circ})(0.09 + j0.25) + 220 \angle 0^{\circ}$$

$$\bar{V}_{S} = 298.54 \angle 9.7^{\circ} \vee_{SMS}$$

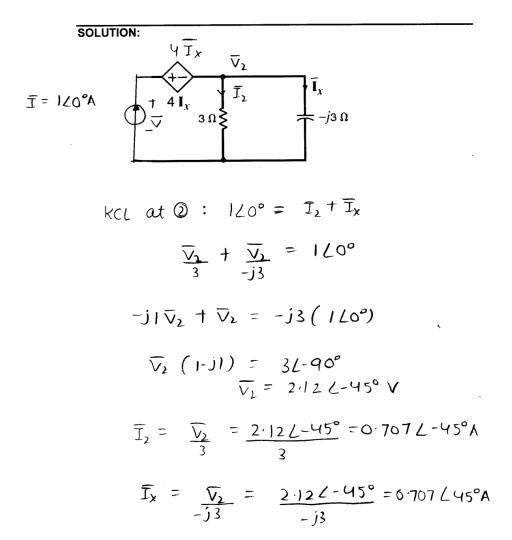2) Encontre  $\mathbf{Z}_{TH}$  no circuito a seguir. (Valor 2,5 pontos - somente acerto integral).



KVL: 
$$\nabla = 4T_x + 3T_2$$


$$\nabla = 4(0.707 \angle 45^\circ) + 3(7.07 \angle -45^\circ)$$

$$\nabla = 3.54 \angle 8.13^\circ V$$

$$\overline{Z}_{TH} = \frac{\overline{V}}{\overline{I}} = \frac{3.54 \angle 8.13^\circ}{120^\circ}$$

$$\overline{Z}_{TH} = 3.54 \angle 8.13^\circ - 2$$

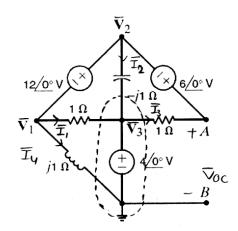3) Determine  $V_{TH}$  no circuito a seguir. (Valor 2,5 pontos).



KCL at supermode: 
$$\overline{I}_1 + \overline{I}_2 + \overline{I}_4 = \overline{I}_3$$

$$\frac{\overline{\nabla}_1 - \overline{\nabla}_2}{1} + \frac{\overline{\nabla}_2 - \overline{\nabla}_3}{j1} + \frac{\overline{\nabla}_1}{j1} = \frac{\overline{\nabla}_3 - \overline{\nabla}_{OC}}{1}$$

$$j1(\overline{\nabla}_1 - \overline{\nabla}_3) - (\overline{\nabla}_2 - \overline{\nabla}_3) + \overline{\nabla}_1 = j1(\overline{\nabla}_3 - \overline{\nabla}_{OC})$$

$$(1+j1)\overline{\nabla}_1 - \overline{\nabla}_2 + (1-j2)\overline{\nabla}_3 + \overline{\nabla}_{OC} = 0$$

$$\nabla_{3} = 420^{\circ} V$$

$$\nabla_{0}c - \nabla_{2} = 620^{\circ}$$

$$-\nabla_{1} + \nabla_{2} = 1220^{\circ}$$

$$(1+j1) \nabla_{1} - \nabla_{2} + \nabla_{0}c = -420^{\circ} (1-j2)$$

$$(1+j1) \nabla_{1} - \nabla_{2} + \nabla_{0}c = 8.942116.57^{\circ}$$

$$-\nabla_{2} + \nabla_{0}c = 620^{\circ}$$

$$-\nabla_{1} + \nabla_{2} = 1220^{\circ}$$


$$(1+j1) \nabla_{1} - \nabla_{2} + \nabla_{0}c = 8.942116.57^{\circ}$$

$$\nabla_{1} = 9.0529626.35^{\circ} V$$

$$\nabla_{2} = 14.21239.28^{\circ} V$$

$$\nabla_{0}c = 19.23227.9^{\circ}$$

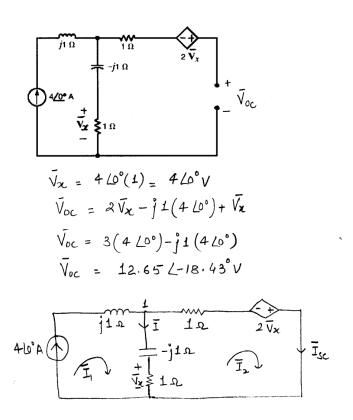4) Encontre  $\mathbf{Z}_L$  para máxima transferência de potência. (Valor: 1,0 ponto pro  $\mathbf{V}_{TH}$ , 1,0 ponto pro  $\mathbf{I}_N$  e 0,5 ponto pro  $\mathbf{Z}_L$ ).



KCL: 
$$\bar{I}_{1} = \bar{I} + \bar{I}_{2}$$
  
 $\bar{I} = \bar{I}_{1} - \bar{I}_{2}$   
KVL  $\Lambda^{0}_{1}$ ght  $loop$ :  
 $1(\bar{I}_{2}) + (1 - \dot{j}_{1})(-\bar{I}_{1}) = 2\bar{V}_{X}$   
 $\bar{I}_{2} + (1 - \dot{j}_{1})(-\bar{I}_{1} + \bar{I}_{2}) = 2\bar{V}_{X}$   
 $\bar{V}_{X} = \bar{I}(1) = \bar{I}_{1} - \bar{I}_{2}$   
 $\bar{I}_{2} + (1 - \dot{j}_{1})(-\bar{I}_{1} + \bar{I}_{2}) = 2(\bar{I}_{1} - \bar{I}_{2})$   
 $(-3 + \dot{j}_{1})\bar{I}_{1} + (4 - \dot{j}_{1})\bar{I}_{2} = 0$   
 $\bar{I}_{1} = A L 0^{\circ} A$   
 $(4 - \dot{j}_{1})\bar{I}_{2} = (-4 L 0^{\circ})(-3 + \dot{j}_{1})$   
 $\bar{I}_{2} = 3.0 + (-4.4^{\circ} A)$   
 $\bar{I}_{3} = 3.0 + (-4.4^{\circ} A)$   
 $\bar{I}_{3} = 3.0 + (-4.4^{\circ} A)$   
 $\bar{I}_{3} = 3.0 + (-4.4^{\circ} A)$   
 $\bar{I}_{4} = -4.4^{\circ} A$   
 $\bar{I}_{5} = \bar{I}_{2} = 3.0 + (-4.4^{\circ} A)$   
 $\bar{I}_{5} = \bar{I}_{5} = -18.43^{\circ}$   
 $\bar{I}_{7} = 4 - \dot{j}_{1} \Omega$   
 $\bar{I}_{7} = \bar{I}_{7} = -1.4 + \dot{i}_{1} \Omega$