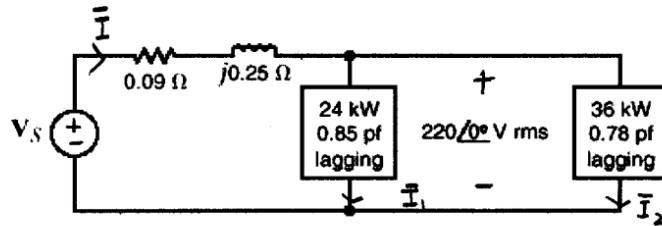


Primeira Avaliação - Circuitos Elétricos - Professor: André E. Lazzaretti

1) Encontre V_s no circuito a seguir, considerando $f=60\text{Hz}$. (Valor 2,5 pontos - somente acerto integral).



$$P_1 = V_L I_1 \text{ PF}_1$$

$$I_1 = \frac{24 \text{ k}}{220 (0.85)}$$

$$I_1 = 128.34 \text{ A rms}$$

$$\bar{I}_1 = 128.34 \angle -\cos^{-1}(0.85)$$

$$\bar{I}_1 = 128.34 \angle -31.79^\circ \text{ A rms}$$

$$I_2 = \frac{P_2}{V_L \text{ PF}_2} = \frac{36 \text{ k}}{(220)(0.78)}$$

$$I_2 = 209.8 \text{ A rms}$$

$$\bar{I}_2 = 209.8 \angle -\cos^{-1}(0.78)$$

$$\bar{I}_2 = 209.8 \angle -38.74^\circ \text{ A rms}$$

$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

$$\bar{I} = 128.34 \angle -31.79^\circ + 209.8 \angle -38.74^\circ$$

$$\bar{I} = 337.55 \angle -36.10^\circ \text{ A rms}$$


$$\bar{V}_s = \bar{I} (0.09 + j0.25) + 220 \angle 0^\circ$$

$$\bar{V}_s = (337.55 \angle -36.10^\circ)(0.09 + j0.25) + 220 \angle 0^\circ$$

$$\bar{V}_s = 298.54 \angle 9.7^\circ \text{ V rms}$$

2) Encontre Z_{TH} no circuito a seguir. (Valor 2,5 pontos - somente acerto integral).

SOLUTION:

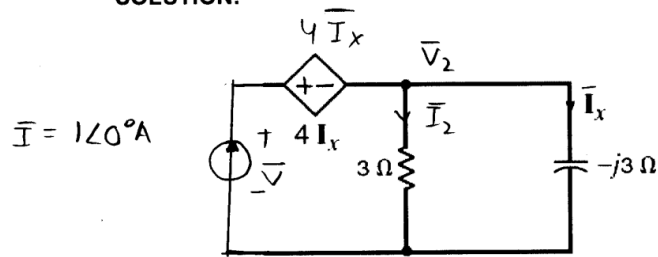

$$\text{KCL at } \textcircled{2} : 120^\circ = \bar{I}_2 + \bar{I}_x$$

$$\frac{\bar{V}_2}{3} + \frac{\bar{V}_2}{-j3} = 120^\circ$$

$$-j1\bar{V}_2 + \bar{V}_2 = -j3(120^\circ)$$

$$\bar{V}_2 (1 - j1) = 3 \angle -90^\circ$$

$$\bar{V}_2 = 2.12 \angle -45^\circ \text{ V}$$

$$\bar{I}_2 = \frac{\bar{V}_2}{3} = \frac{2.12 \angle -45^\circ}{3} = 0.707 \angle -45^\circ \text{ A}$$

$$\bar{I}_x = \frac{\bar{V}_2}{-j3} = \frac{2.12 \angle -45^\circ}{-j3} = 0.707 \angle 45^\circ \text{ A}$$

$$\text{KVL: } \bar{V} = 4\bar{I}_x + 3\bar{I}_2$$


$$\bar{V} = 4(0.707 \angle 45^\circ) + 3(7.07 \angle -45^\circ)$$

$$\bar{V} = 3.54 \angle 8.13^\circ \text{ V}$$

$$\bar{Z}_{TH} = \frac{\bar{V}}{\bar{I}} = \frac{3.54 \angle 8.13^\circ}{1 \angle 0^\circ}$$

$$\bar{Z}_{TH} = 3.54 \angle 8.13^\circ \Omega$$

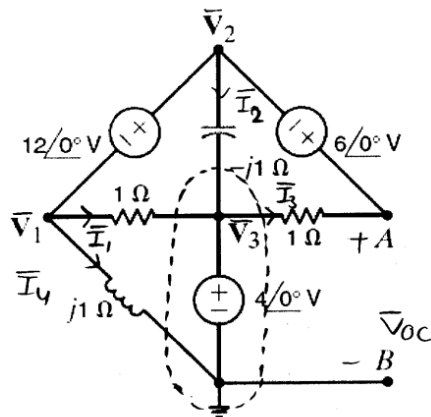3) Determine $\mathbf{V_{TH}}$ no circuito a seguir. (Valor 2,5 pontos).



$$\text{KCL at supernode: } \bar{I}_1 + \bar{I}_2 + \bar{I}_4 = \bar{I}_3$$

$$\frac{\bar{V}_1 - \bar{V}_2}{1} + \frac{\bar{V}_2 - \bar{V}_3}{-j1} + \frac{\bar{V}_1}{j1} = \frac{\bar{V}_3 - \bar{V}_{OC}}{1}$$

$$j1(\bar{V}_1 - \bar{V}_3) - (\bar{V}_2 - \bar{V}_3) + \bar{V}_1 = j1(\bar{V}_3 - \bar{V}_{OC})$$

$$(1 + j1)\bar{V}_1 - \bar{V}_2 + (1 - j2)\bar{V}_3 + \bar{V}_{OC} = 0$$

$$\bar{V}_3 = 4\angle 0^\circ \text{ V}$$

$$\bar{V}_{oc} - \bar{V}_2 = 6\angle 0^\circ$$

$$-\bar{V}_1 + \bar{V}_2 = 12\angle 0^\circ$$

$$(1+j1)\bar{V}_1 - \bar{V}_2 + \bar{V}_{oc} = -4\angle 0^\circ (1-j2)$$

$$(1+j1)\bar{V}_1 - \bar{V}_2 + \bar{V}_{oc} = 8.94\angle 116.57^\circ$$

$$-\bar{V}_2 + \bar{V}_{oc} = 6\angle 0^\circ$$

$$-\bar{V}_1 + \bar{V}_2 = 12\angle 0^\circ$$


$$(1+j1)\bar{V}_1 - \bar{V}_2 + \bar{V}_{oc} = 8.94\angle 116.57^\circ$$

$$\bar{V}_1 = 9.05\angle 96.35^\circ \text{ V}$$

$$\bar{V}_2 = 14.21\angle 39.28^\circ \text{ V}$$

$$\bar{V}_{oc} = 19.23\angle 27.9^\circ$$

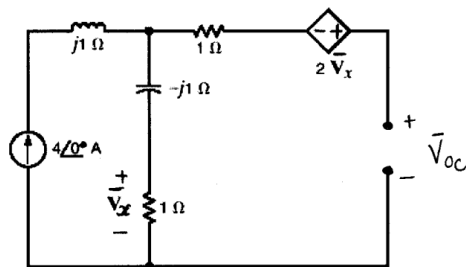4) Encontre Z_L para máxima transferência de potência. (Valor: 1,0 ponto pro V_{TH} , 1,0 ponto pro I_N e 0,5 ponto pro Z_L).




$$\bar{V}_x = 4\angle 0^\circ (1) = 4\angle 0^\circ \text{ V}$$

$$\bar{V}_{oc} = 2\bar{V}_x - j1(4\angle 0^\circ) + \bar{V}_x$$

$$\bar{V}_{oc} = 3(4\angle 0^\circ) - j1(4\angle 0^\circ)$$
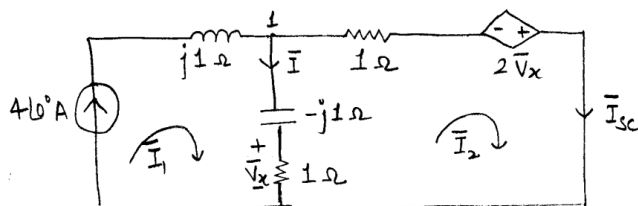
$$\bar{V}_{oc} = 12.65\angle -18.43^\circ \text{ V}$$



$$\text{KCL: } \bar{I}_1 = \bar{I} + \bar{I}_2$$

$$\bar{I} = \bar{I}_1 - \bar{I}_2$$

KVL right loop:

$$1(\bar{I}_2) + (1-j1)(-\bar{I}) = 2\bar{V}_x$$

$$\bar{I}_2 + (1-j1)(-\bar{I}_1 + \bar{I}_2) = 2\bar{V}_x$$

$$\bar{V}_x = \bar{I}(1) = \bar{I}_1 - \bar{I}_2$$

$$\bar{I}_2 + (1-j1)(-\bar{I}_1 + \bar{I}_2) = 2(\bar{I}_1 - \bar{I}_2)$$

$$(-3+j1)\bar{I}_1 + (4-j1)\bar{I}_2 = 0$$

$$\bar{I}_1 = 4\angle 0^\circ \text{ A}$$

$$(4-j1)\bar{I}_2 = (-4\angle 0^\circ)(-3+j1)$$

$$\bar{I}_2 = 3.07\angle -4.4^\circ \text{ A}$$

$$\bar{I}_{sc} = \bar{I}_2 = 3.07\angle -4.4^\circ \text{ A}$$

$$\bar{Z}_{TH} = \frac{\bar{V}_{oc}}{\bar{I}_{sc}} = \frac{12.65\angle -18.43^\circ}{3.07\angle -4.4^\circ}$$

$$\bar{Z}_{TH} = 4-j1\Omega$$

$$\bar{Z}_L = \bar{Z}_{TH}^* = 4+j1\Omega$$