

FPGA Assignment: UP–DOWN Counter + TIMER Circuit

Platform: Altera DE2-70 FPGA board

Project Goal

Design and implement a digital **UP–DOWN counter with a timer function** on the DE2-70 FPGA board, Fig. 1. Use the board's **switches (SW)** and **keys (KEY)** to control the operation according to the following specifications.

Functional Description

1. Timer Duration Control

o **Switch group A (SW A):**

Sets the **duration** of the timer signal — this represents either:

- Whole seconds, or
- Tenths of a second (0.1 s)

o **Switch B (SW B):**

Selects the **time unit** for the duration set by SW A:

- 0 → duration in **seconds**
- 1 → duration in **seconds / 10**

2. Counting Direction

o **Switch C (SW C):**

Determines counting direction:

- 0 → **Up-counting**
- 1 → **Down-counting**

3. Counter Enable

o **Switch D (SW D):**

Acts as the **enable (gate)** control for the counter:

- 1 → Counter active
- 0 → Counter stopped

4. Timer Trigger and Reset

o **KEY A:**

One-shot trigger — starts the timer once when pressed.

o **KEY B:**

Reset — clears the counter and timer, returning the circuit to its initial state.

5. Output Display

- o The **current counted value** (in seconds or tenths of seconds, based on SW B) must be displayed on the **7-segment displays** of the FPGA board.
-

Implementation Groups

- **Group 1:** Implement the “**blue modules**” (as shown in your project diagram or design document).
 - **Group 2:** Implement the “**orange modules.**”
-

Deliverables

Each group must submit:

1. **Project materials**
 - o Quartus project files (.qpf, .bdf/.v/.vhd, pin assignments)
 - o Timing and block diagrams (if applicable)
 2. **Short Description**
 - o Explain how each switch and key controls the system.
 - o Describe the functionality of the timer and counter modules.
 - o Mention how the display output is generated.
 3. **Video Demonstration**
 - o Show the FPGA in operation:
 - Demonstrate both UP and DOWN counting.
 - Show switching between seconds and seconds/10 mode.
 - Demonstrate timer triggering and reset functions.
-

Learning outcomes

- Use a **clock divider** to create 1-second and 0.1-second timing signals.
- Implement the **counter** and **timer** as separate modules for clarity.
- Use **state machines** for precise control of timer start/stop.
- Test each part separately before integrating everything.

 


Figure 1: Architecture of FPGA UP/Down counter with Timer logic