

CMSC389E:

Digital Logic Design Through Minecraft

Adders, Encoders, Decoders

Fall 2020
Akilesh Praveen

Administrivia

- Project Submission via ELMS
 - CS Department Bureaucracy :(
- Keep checking the course website! (will be updated tonight)
(<http://www.cs.umd.edu/class/fall2020/cmsc389E/>)

Announcements

- Project 2
 - Conceptual knowledge in today's lecture + online textbook
 - Project spec will be released on ELMS and course website **tonight / Saturday**

Numbers and Computers

Numbers & Computers

- Let's talk about numbers and computers
- How do they deal with them?

Numbers & Computers

- Let's talk about numbers and computers
- How do they deal with them?
 - In binary

Numbers & Computers

- Let's talk about numbers and computers
- How do they deal with them?
 - In binary
- How do **we** deal with them?

Numbers & Computers

- Let's talk about numbers and computers
- How do they deal with them?
 - In binary
- How do **we** deal with them?
 - In decimal

Numbers & Computers

- We're going to work through creating circuits that let us
 - **Manipulate** binary numbers on a computer
 - **Convert** binary numbers to decimal (for us to work with) and vice versa
- *READ: Digital Logic & Comp Arch in Minecraft, C3*

Adders

Adders

- We all know how to add numbers

Adders

- We all know how to add numbers
 - Hopefully

Adders

- We all know how to add numbers
 - Hopefully
- How do computers add them?

Adders

- We all know how to add numbers
 - Hopefully
- How do computers add them?
 - First, think about number representation in **digital logic circuits**

Adders

- We all know how to add numbers
 - Hopefully
- How do computers add them?
 - First, think about number representation in **digital logic circuits**
- Let's work through an example

Adders

- How would you, **as a human**, add the following numbers
 - `0b11101`
 - `0b11011`

Adders

- How would you, **as a human**, add the following numbers
 - `0b111101`
 - `0b111011`
- Let's take it back to elementary school

Adders

- Remember, we're working with binary

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline \end{array}$$

Adders

- Let's add the first 'column' here

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Adders

- We seem to have a 'carry-over' happening here

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Adders

- This happens when we exceed the a number system's limit with an 'add'
- Where else during this computation would this occur?
 - Keep this one in mind

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 11101 \\ 11011 \\ \hline 0 \end{array}$$

Half Adders

Half Adders

- Now, think about how a computer would do this operation

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Half Adders

- Now, think about how a computer would do this operation
 - Let's make it into a smaller problem

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Half Adders

- We want **two** bits input
- We want **two** bits output

$$\begin{array}{r} 1 \\ 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Half Adders

- We want **two** bits input
 - Input number 1 (one digit)
 - Input number 2 (one digit)
- We want **two** bits output
 - One for the sum
 - One for the 'carry'

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 11011 \\ 1 \end{array}$$


Half Adders

- Turns out, **generating** those two output bits given our two inputs is pretty easy!
- *READ: Digital Logic & Comp Arch in Minecraft, C3.1*

Half Adders

- Here's our truth table and logic circuit

Half Adder		
In	Sum	Carry
0 0	0	0
0 1	1	0
1 0	1	0
1 1	0	1

 

Full Adder

Full Adders

- The Half Adder is great, but limited in functionality
- Let's work on scaling it up
 - From adding **two one digit numbers**
 - To adding **two n digit numbers**
- How can we accomplish this?
 - Think back to our addition example

Full Adders

- In other words, our **half-adder** takes care of this one...

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 11011 \\ 0 \end{array}$$

Full Adders

- But our new circuit needs to handle all of these as well


$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

The diagram illustrates a binary addition problem. The top number is 11101, and the bottom number is 11011. A plus sign is to the left of the bottom number. A horizontal line is drawn below the bottom number. Below the line, the result is 0. A red '1' is positioned above the second digit from the right of the top number. Green ovals encircle the first four digits of both numbers and the result. A red oval encircles the last digit of both numbers and the result.


Full Adders

- Our solution?
 - Just handle a ‘carry in’ bit!
 - It turns out, that’s all we need
- *READ: Digital Logic & Comp Arch in Minecraft, C3.2*

Full Adders

 

Full Adders

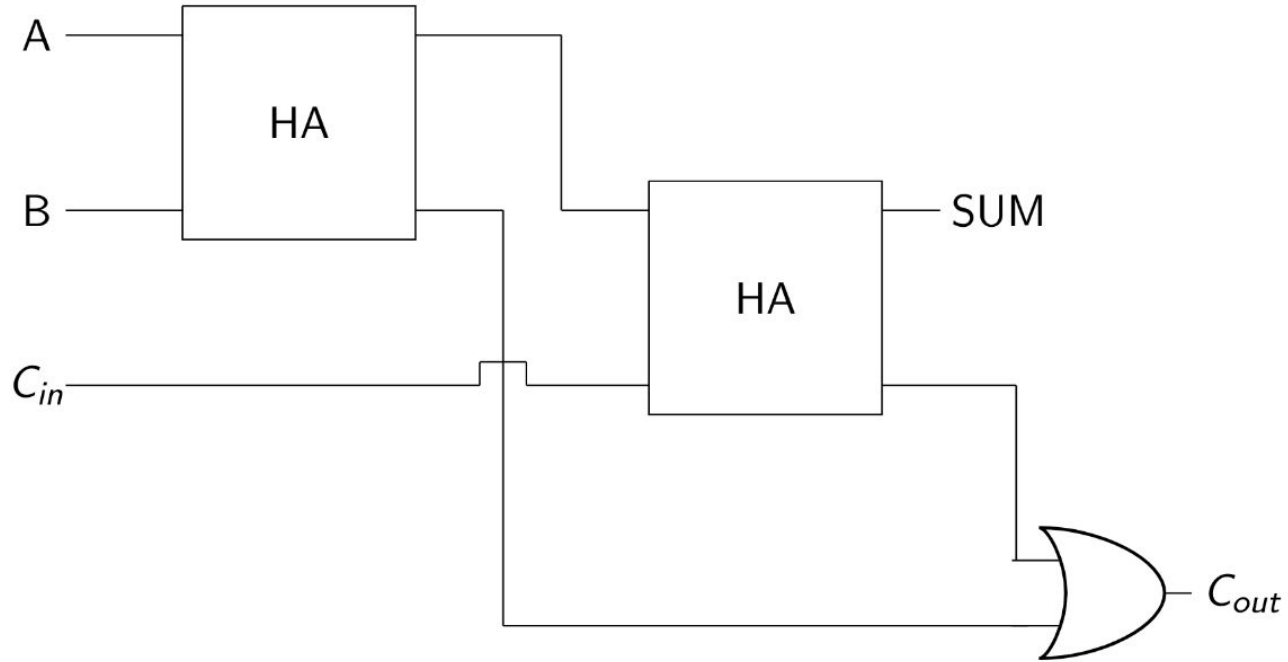

Full Adders

- Q: How would doing all this sequential math actually look in terms of a circuit?

A binary addition diagram showing the sum of 11011 and 11101. The numbers are aligned vertically with a plus sign to the left. A horizontal line is drawn below the second number. The result 0 is shown below the line. A red '1' is written above the fourth column. Green ovals encircle the first four columns of the numbers and the result. A red oval encircles the fifth column of the numbers and the result.

$$\begin{array}{r} 11101 \\ + 11011 \\ \hline 0 \end{array}$$

Full Adders

- A: Like this
 - Note that the adder determining S_0 can also be a HA

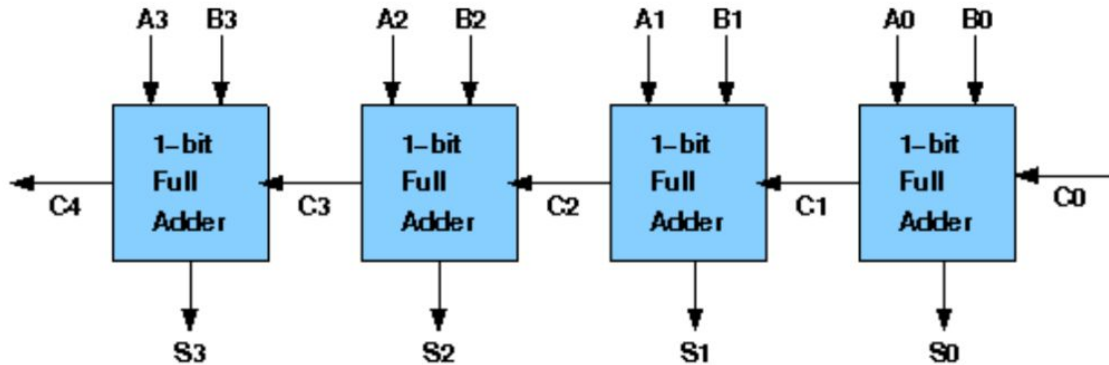


Image courtesy of IIT

Full Adders

- In terms of Minecraft, we really only **need** to know how to make a Full adder
 - A half adder is the same thing, without a carry bit
- Luckily, there's a pretty simple way to put together a full adder leveraging Minecraft's odd nuances
 - Full adder demo by Ashwath

Decoders & Encoders

Decoders & Encoders

- How will we get this data out of our computer and into an interpretable form?
- I.e. how can we convert this binary representation into decimal representation easily?

Decoders & Encoders

- This is an essential problem in digital logic
 - Pertaining to computer design
- Engineers have designed two logical circuits help us interface with different number systems
 - Decoder
 - Encoder

Decoders & Encoders

- **Decoders** convert binary signals into decimal representations of those signals
- **Encoders** convert decimal representations of signals back into binary
- These circuits can be generalized to different number systems as well

Decoders & Encoders

- **Decoders:** Binary to decimal
- **Encoders:** Decimal to binary

Decoders & Encoders

- Let's first talk about decoders
- What would you do (as a human) if I asked you to convert the following binary number to decimal form?
 - 0b110

Decoders & Encoders

- Let's first talk about decoders
- What would you do (as a human) if I asked you to convert the following binary number to decimal form?
 - 0b110
- Now think in terms of three wires coming in, each representing a digit

Decoders & Encoders

- A solution: assign a wire for each possible output
 - If the binary input is 0, turn only a certain wire on
 - If the binary input is 1, turn only another wire on
 - If the binary input is 2, turn only another wire on
 - etc.

Decoders & Encoders

- We will need more output wires than input wires

Decoders & Encoders

- We will need more output wires than input wires
- Given 3 inputs

Decoders & Encoders

- We will need more output wires than input wires
- Given 3 inputs
 - We will need 8 outputs

Decoders & Encoders

- We will need more output wires than input wires
- Given 3 inputs
 - We will need 8 outputs
- Given n inputs?

Decoders & Encoders

- We will need more output wires than input wires
- Given 3 inputs
 - We will need 8 outputs
- Given n inputs
 - We will need 2^n outputs

Decoders & Encoders

- Let's figure out our smaller example first
 - How will we take 3 input binary values and select one of 8 outputs for them?
 - It turns out, the answer is fairly straightforward once you create a truth table

Decoders & Encoders

- Let's figure out our smaller example first
 - How will we take 3 input binary values and select one of 8 outputs for them?
 - It turns out, the answer is fairly straightforward once you create a truth table

Decoders & Encoders

Table I Truth table for 3 to 8 decoder

Enable pin	Input lines			Output lines							
E	I ₂	I ₁	I ₀	O ₇	O ₆	O ₅	O ₄	O ₃	O ₂	O ₁	O ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0


Note: 'x' denotes don't care condition

Decoders & Encoders

- Once we've made our truth table, it becomes much easier to create a logical circuit
- Notice the clever use of input buses (we will put up another video about those in the near future)

READ: Digital Logic & Comp Arch in Minecraft, C3.3

Decoders & Encoders

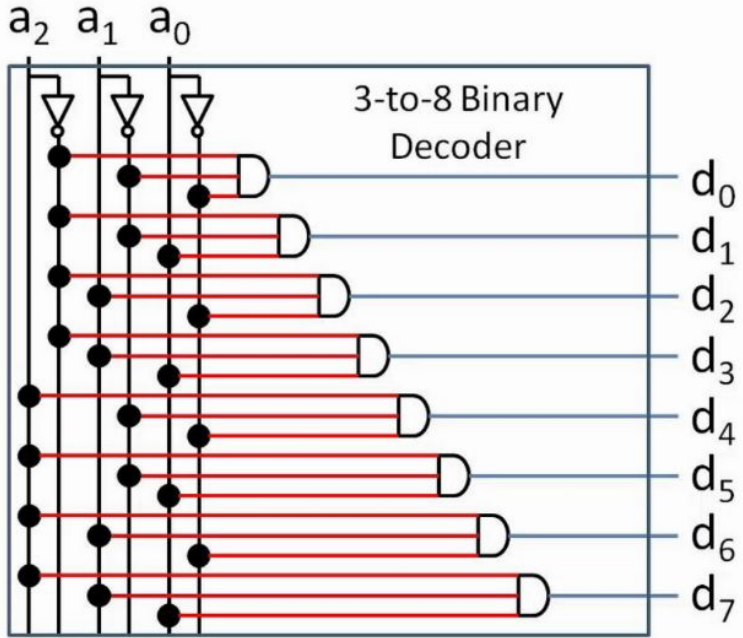

Decoders & Encoders

- Suppose we wanted to go the other way around
- From decimal to binary
 - Why?
- *READ: Digital Logic & Comp Arch in Minecraft, C3.5*

Decoders & Encoders

- Encoders are essentially the complement to decoders
 - Suppose this time that we had 8 input wires, each signifying numbers from 0-7
 - Our goal now is to decide binary output based on which wire out of the 8 is 'on'

Decoders & Encoders

- The logical circuit is strikingly similar to the decoder
- First, let's look at the truth table

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1


Decoders & Encoders

- Now, the circuit

READ: Digital Logic

& Comp Arch in

Minecraft, C3.4

 

Buses Demo

Project 2