

Current

Electricity:

Voltage and Resistance

March 8, 2022

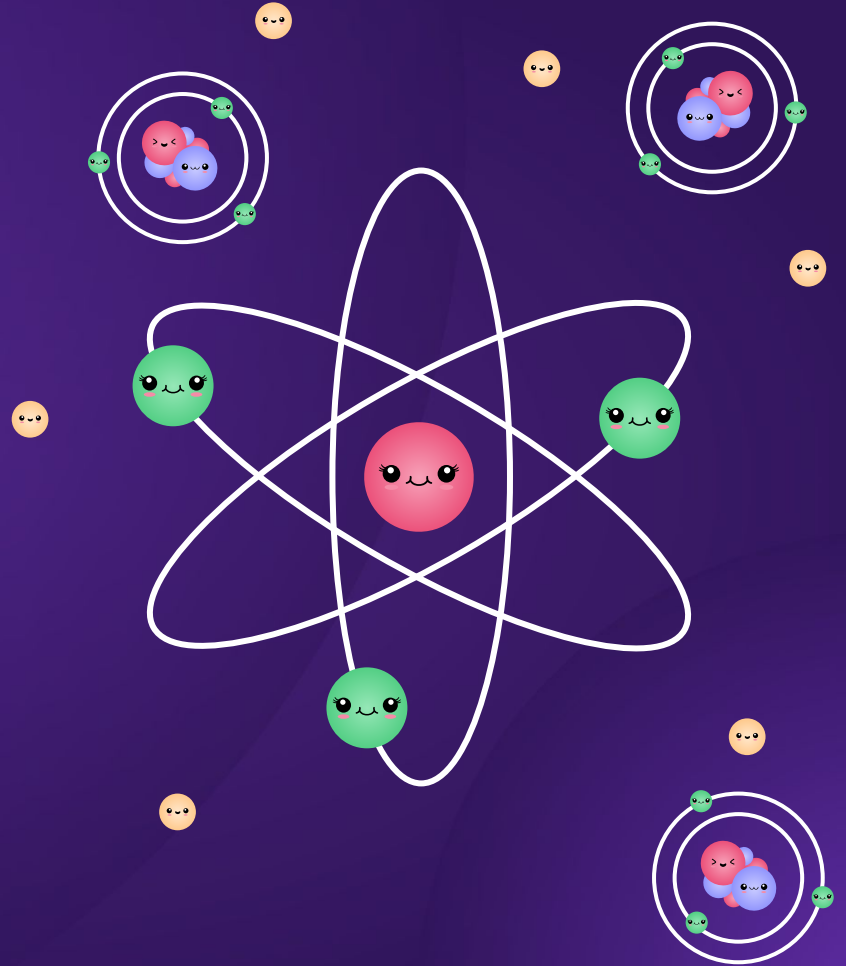


Table of contents



01

Defining Voltage

02

**Measuring
Voltage**

03



Defining Resistance

04

Resistance Values

01

Voltage

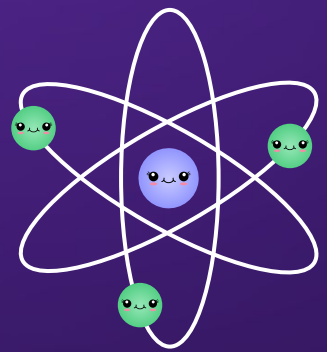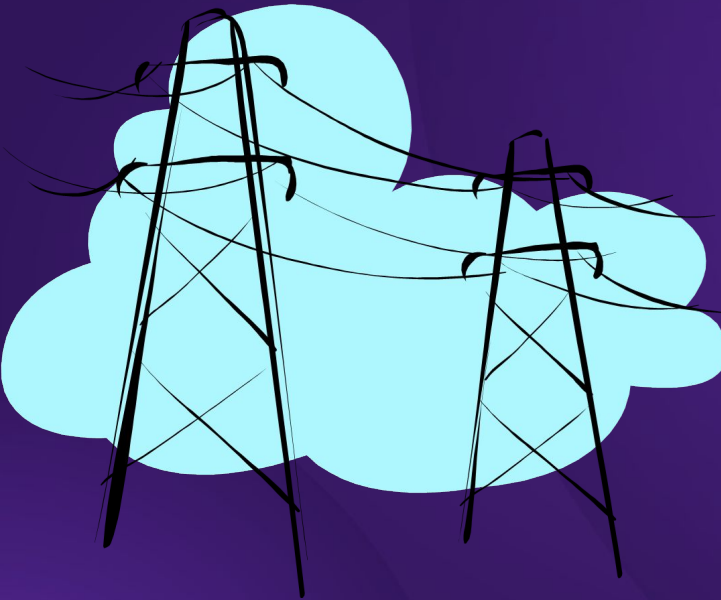

What is Voltage (V)?



- Electrical energy is carried through a circuit by electrons.
- The change in electrical energy per coulomb of charge is called potential difference





Potential Difference



- When we hear difference what comes to mind?

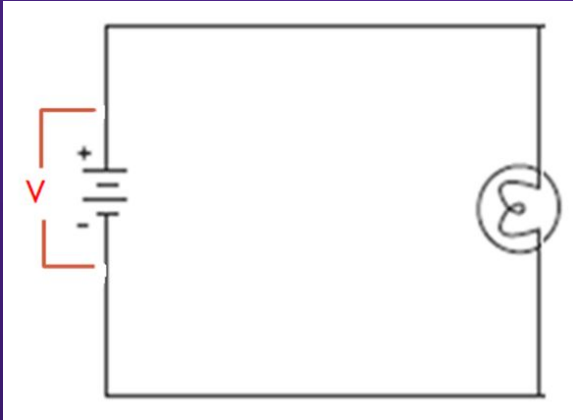
In a circuit, we can measure the change in potential energy between two different points on the circuit, and we call this potential difference, or voltage (V).



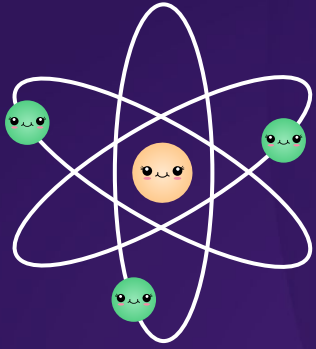

02

Measuring Voltage

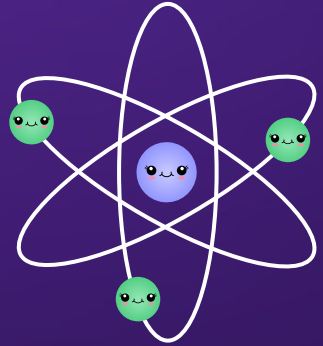


Units of Voltage



- Potential difference is measured in Volts (named after the guy above)
- Because of its units Potential Difference is often just referred to as voltage (V)

Measuring the Voltage


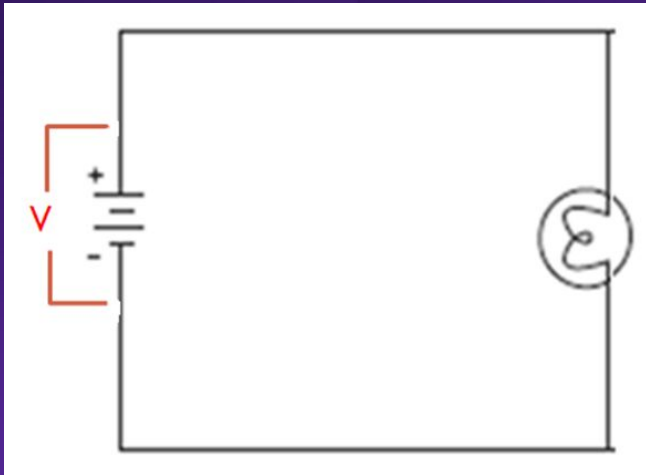
- Voltage is measured by a device called a voltmeter




The voltmeter is always connected across the device
Reminder: this is to measure the difference between 2 points

Check Your Understanding

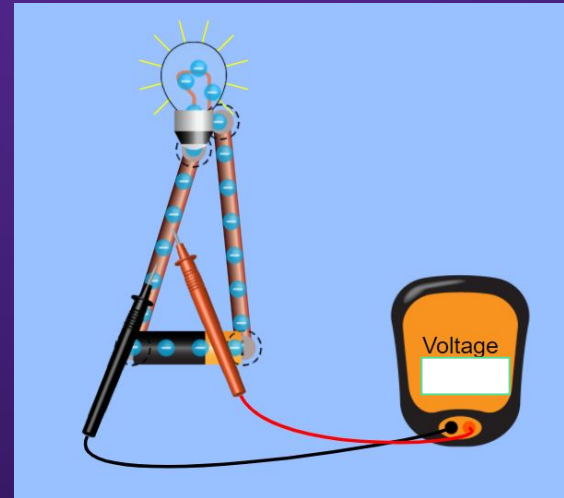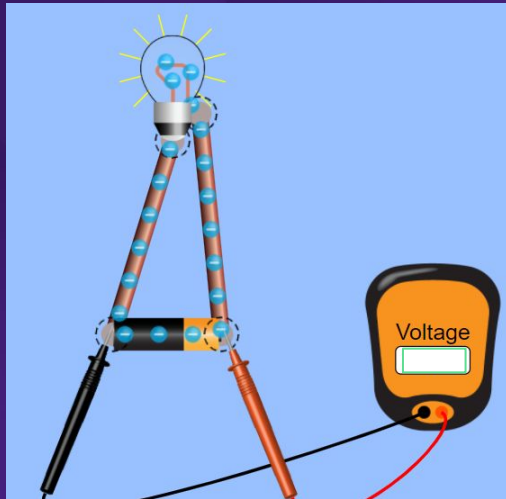Which of following will give a non-zero potential difference reading?




Examples...

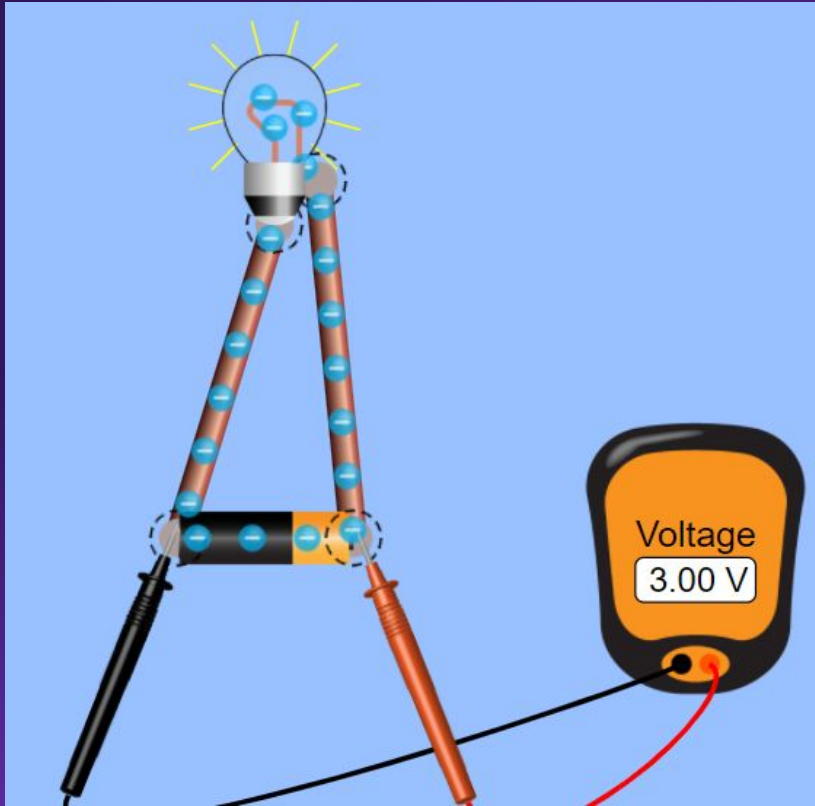


- When the Voltmeter hugs the battery we can measure the change in energy from the start to the end of the circuit

Examples...

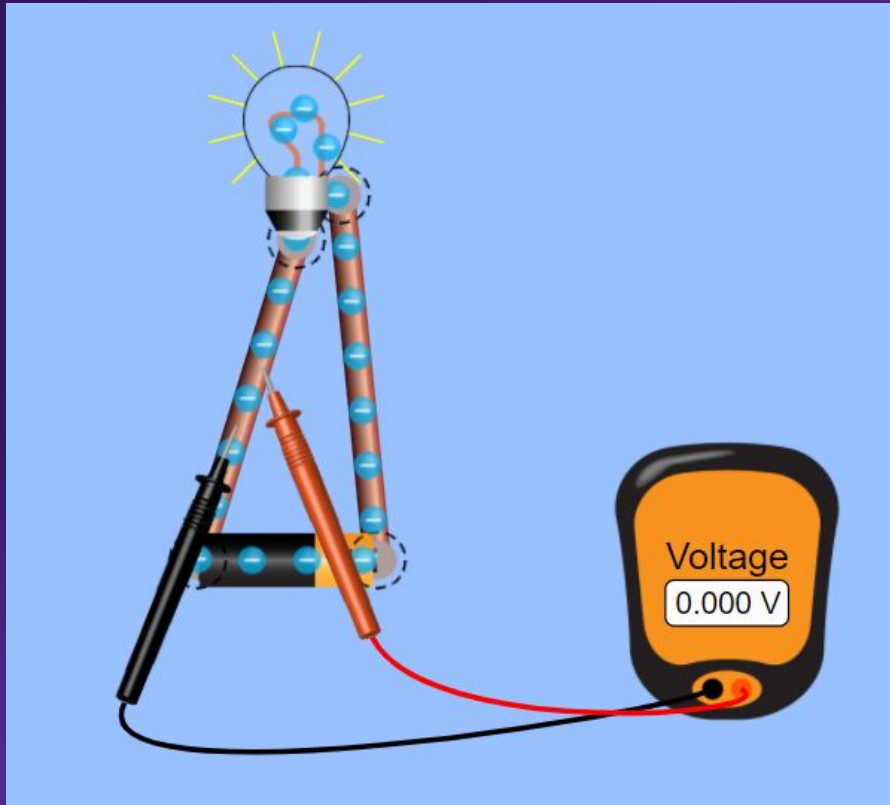


- When the Voltmeter is placed into a single point in the circuit no change in energy is detected

Examples...

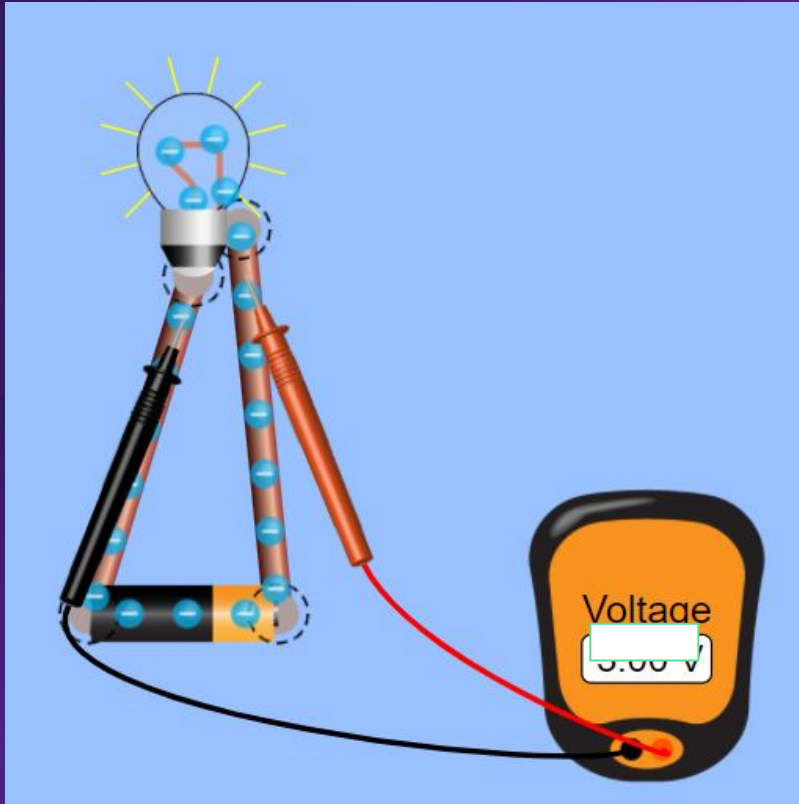

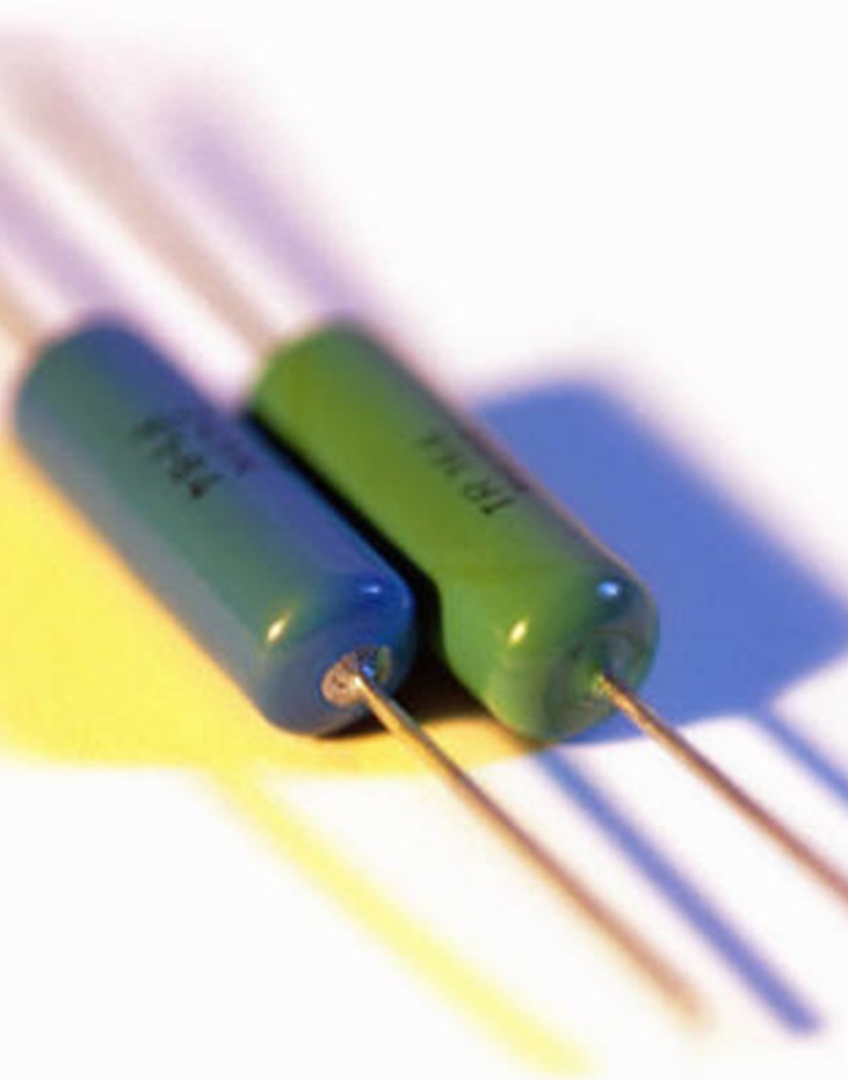- When the Voltmeter hugs the bulb we can measure the energy dissipated by the bulb




03

Defining Resistance


The Resistor

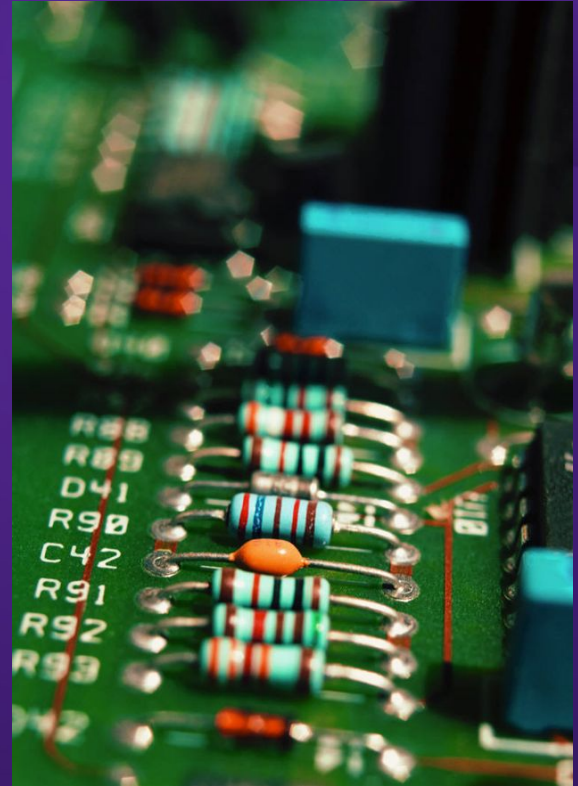- A resistor is part of an electric circuit that resists the flow of electric current.
- As current flows through a resistor, some of the electrical energy is transformed into another form, such as light or heat energy.



Resistors in a circuit


The symbol for a simple resistor is:

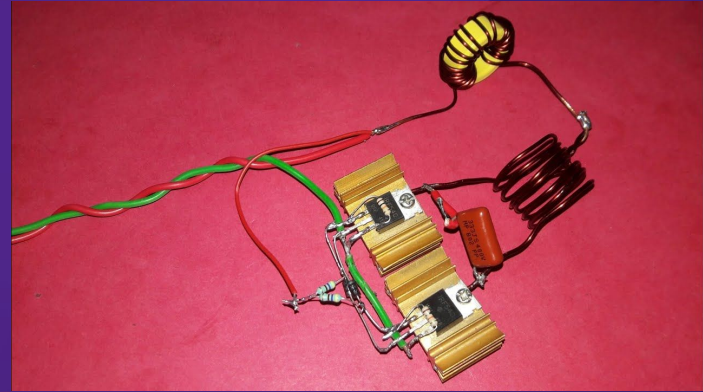


But... Many other components of circuits such as bulbs or heaters are also resistors and they get their own special symbols

Resistors Resist Current

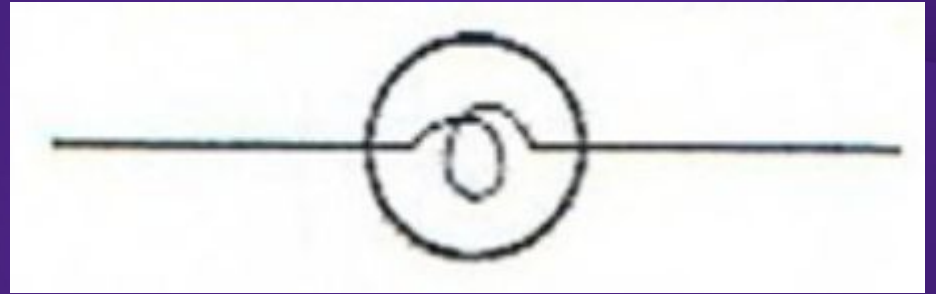When a resistor is connected to an electric cell, the amount of **current** that flows through the circuit depends on **the amount of resistance**




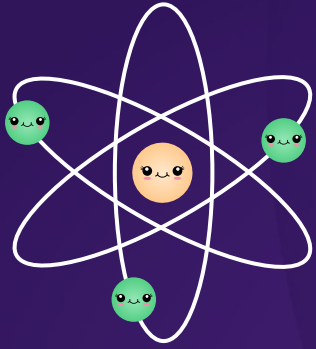A bulb is a special type of resistor where some of the current gets converted/used as “light” energy!



04

Resistance Values

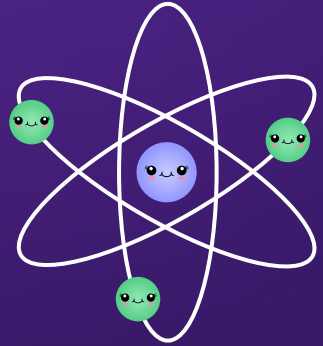

Units


Resistance is measured by an ohmmeter in units called Ohms with the symbol Ω (it's a greek letter called Omega)



Resistors are colour coded

black	0
brown	1
red	2
orange	3
yellow	4
green	5
blue	6
violet	7
grey	8
white	9

From p. 316

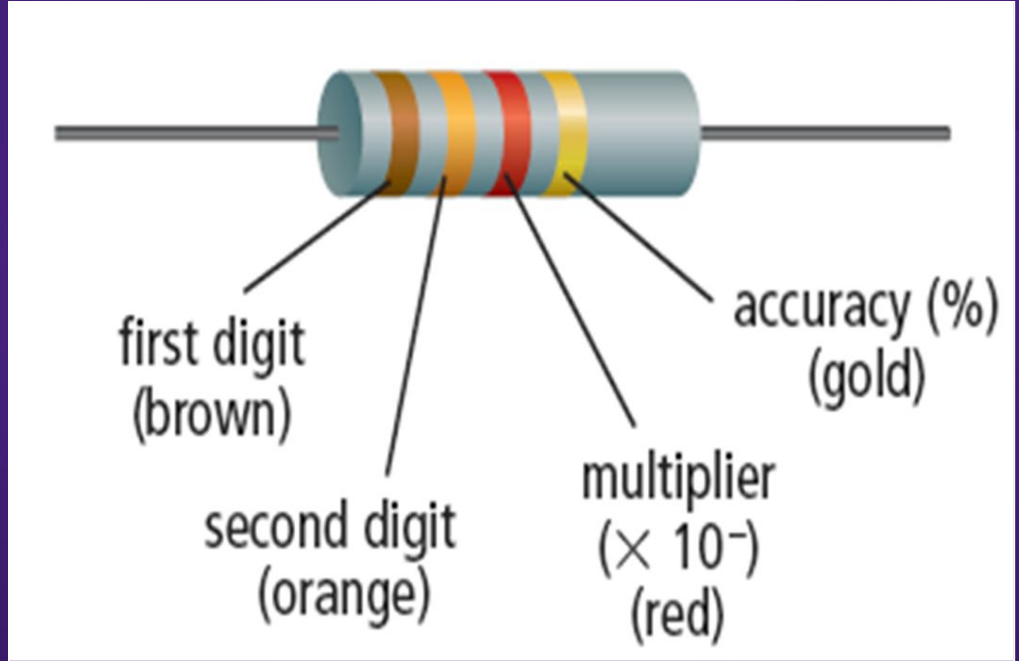

This example has a value of
 $13 \times 10^2 \Omega = 1300 \Omega$

Check your Understanding

Which of the following describes resistance?


I.	It resists the flow of electrons.
II.	It speeds up the current flow in a circuit.
III.	It causes the electron's electrical energy to be converted to heat and light energy.

- A.** I and II only
- B.** I and III only
- C.** II and III only
- D.** I, II, and III

Check your Understanding

Which of the following correctly matches the devices with what they measure?

	Ammeter	Ohmmeter	Voltmeter
A.	current	voltage	resistance
B.	resistance	current	voltage
C.	voltage	resistance	current
D.	current	resistance	voltage

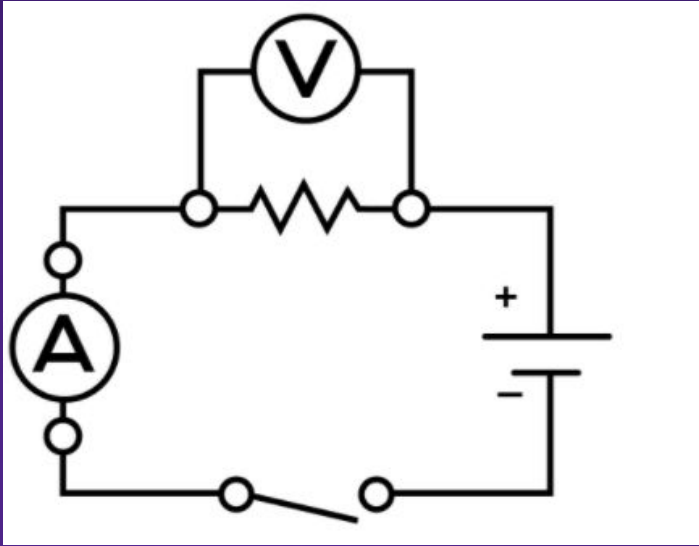

Lab Time