Roll No……..….. **Total No. of Printed Pages: [01]**
Total No. of Questions: [11]

MCA (Semester –1st)
DIGITAL CIRCUITS & LOGIC DESIGN
Subject Code: MECE0F95
Paper ID: [OE1270124]

Time: 03 Hours **Maximum Marks: 60**

Instruction for candidates:

1. Section A is compulsory. It carries 16 marks. It consists of 4 questions of 4 marks each.
2. Section B consist of 4 questions of 8 marks each. The student has to attempt any 3 questions out of it.
3. Section C consist of 3 questions of 10 marks each. The student has to attempt any 2 questions.

Section – A **(4 marks each)**

Q1. What are the Digital signals, Logic Levels, PLAs explain with suitable example?

Q2. Realize 2 input Ex-OR and Ex-NOR gate using NAND gate only.

Q3. Minimize the function using K-map method & Implement the same using NAND gate only.
F(A,B,C,D)= ∑m (1,2,3,8,9,10,11,14)+d(7,15)

Q4. Convert (110101101)2 = ( ) 10
(11011010.110101)2 = ( )16

Section – B **(8 marks each)**

Q5. Draw & explain 16×1 Mux using two 8×1 Mux and one OR Gate.

Q6. Draw the Circuit diagram of Full adder & half subtractor.

Q7. Draw & Explain the JK Flip-Flop. Convert the S-R Flip-Flop to J_K flip flop.

Q8. Draw the circuit of BCD adder & perform the function (9+6) & (8+5).

Section – C **(10 marks each)**

Q9. Explain R-2R ladder network with suitable diagram.

Q10. Design a 3 Bit up counter using J-K-Flip flop.

Q11. Discuss the Modelling and Simulation of Moore and Mealy machines.